

INTERNATIONAL CENTRE FOR APPLIED SCIENCES
 (Manipal University)
II SEMESTER B.S. DEGREE EXAMINATION – JUNE 2016
SUBJECT: LINEAR NETWORKS IN STEADY STATE ANALYSIS (EE 121)
 (BRANCH: CE /E&C/ E&E / BIO-MED)
MONDAY, 13TH JUNE, 2016

Time: 3 Hours

Max. Marks: 100

✓ **Answer ANY FIVE FULL Questions.**

1. A) In the circuit shown in Fig. Q1A, find the equivalent resistance between A and B.
 B) In the network of Fig. Q1B, find the current in $10\ \Omega$ resistor using source transformation technique.

(10+10 Marks)
2. A) In the network shown in Fig. Q2A, find the current in 8V battery using mesh current analysis.
 B) In the circuit of Fig. Q2B, find the current in $5\ \Omega$ resistor using node voltage method.

(10+10 Marks)
3. A) A series circuit takes a current of 3.5A at a power factor of 0.8 leading when connected to a 100V, 50Hz, single phase AC supply. Determine the values of circuit elements.
 B) A coil of resistance r and inductance L is connected in series with a capacitor of $100\ \mu\text{F}$. The voltage across the coil is half of the voltage across the capacitor. The power consumed in the coil is 200W when drawing a current of 5A. Find the values of r and L if the supply frequency is 50Hz.
 C) In the circuit of Fig. Q3C, determine the current through capacitor using mesh current analysis.

(5+5+10 Marks)
4. A) In the network of Fig. Q4A, find (i) current supplied by the battery (ii) power consumed in the circuit (iii) Power factor. Also, draw the power triangle.
 B) A coil of resistance $15\ \Omega$ and inductance 0.05H is connected in parallel with a non-inductive resistance of $15\ \Omega$. The combination is connected across a single phase, 250V, 50Hz, AC supply. Determine (i) the current drawn from the supply (ii) Power Consumed (iv) draw the phasor diagram.

(10+10 Marks)
5. A) In the network of Fig. Q5A, find the current through $8\ \Omega$ resistor using superposition theorem.
 B) In the circuit shown in Fig. Q5B, find the value of load impedance to be connected for maximum power transfer if the load consists of variable resistance in series with variable reactance. Also, find the value of maximum power.

(10+10 Marks)

6. A) In the circuit shown in Fig. Q6A, find the current through 5Ω resistor using Norton's theorem.
- B) Three impedances $Z_1 = (4 + j3)\Omega$, $Z_2 = (8 - j2)\Omega$ and $Z_3 = (R - j5)\Omega$ are connected in parallel across a 100V, single phase AC supply. If R is variable from zero to infinity, draw the locus of total current. Hence, determine (i) minimum current (ii) maximum current in the circuit.
- (10+10 Marks)**
7. A) For the locus diagram shown in Fig. Q7A, draw the circuit configuration and insert the values of all the elements. Also, find the currents at unity power factor.
- B) Three similar impedances, each of $(12 - j8)\Omega$ are connected in star across a 200V, 50 Hz, 3 phase, RYB supply. Determine the line currents, total power consumed and the readings of the two wattmeters connected to measure the power.
- (10+10 Marks)**
8. A) Starting from the fundamentals, determine the readings of the two wattmeters connected to measure the total power in a balanced star connected, lagging power factor load. Hence, show that two wattmeters are sufficient to measure the total power in the balanced 3 phase load.
- B) Three similar load impedances of lagging power factor are connected in delta across a 400V, 3 phase AC supply. The readings of the two wattmeters connected to measure the total power are 8KW and 1KW respectively. Find the values of the elements in the load impedance per phase.
- (10+10 Marks)**

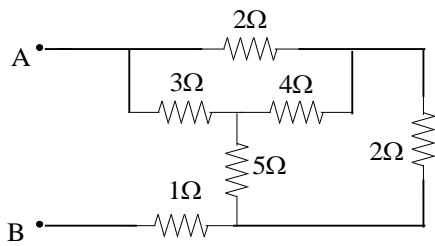


Fig. Q1A

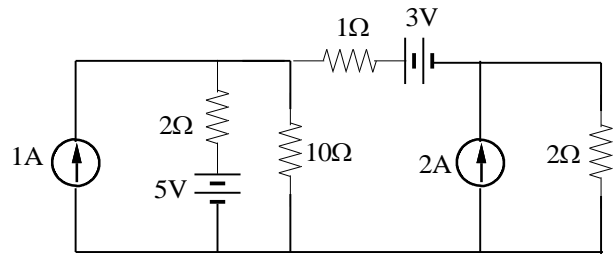


Fig. Q1B

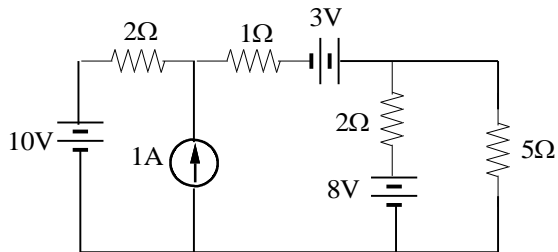


Fig. Q2A

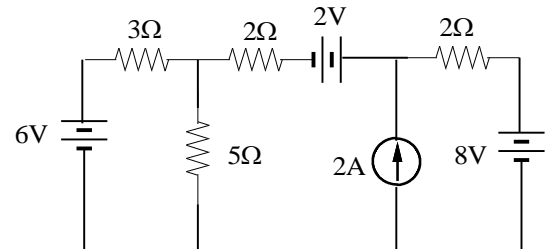


Fig. Q2B

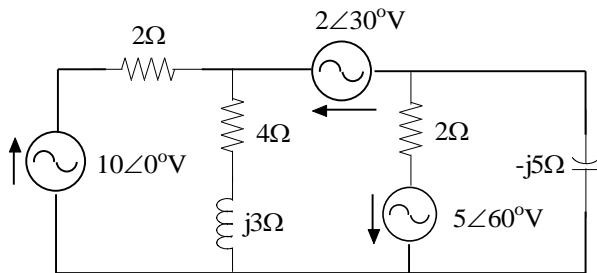


Fig. Q3C

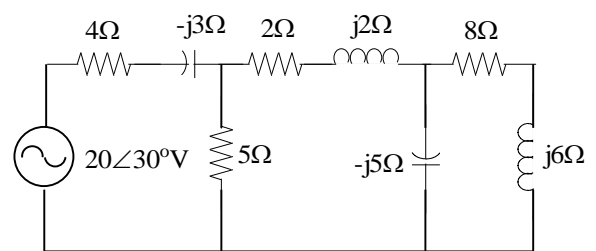


Fig. Q4A

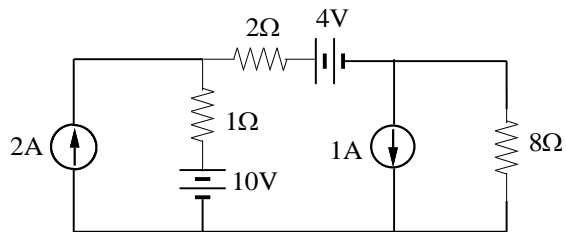


Fig. Q5A

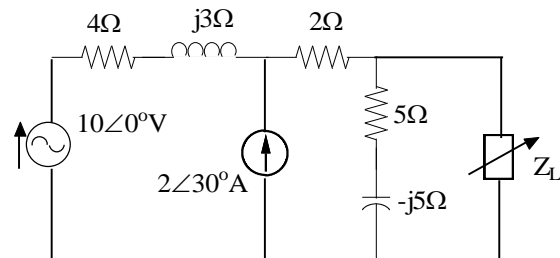


Fig. Q5B

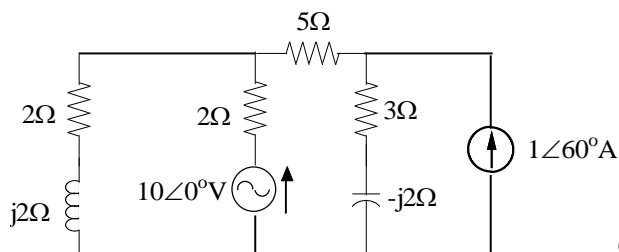


Fig. Q6A

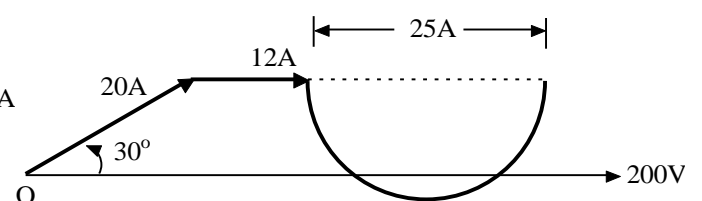


Fig. Q7A