



Reg. No.

--	--	--	--	--	--	--	--	--	--

**INTERNATIONAL CENTRE FOR APPLIED SCIENCES**  
(Manipal University)  
**III SEMESTER B.S. DEGREE EXAMINATION – MAY 2016**  
**SUBJECT: COMBINATIONAL AND SEQUENTIAL LOGIC (EC 231)**  
(BRANCH: COMP SCIENCE/COMP ENGG/E&C/E&E)  
**26<sup>TH</sup> MAY, 2016**

**Time: 3 Hours**

**Max. Marks: 100**

✓ **Answer ANY FIVE full Questions.**

1A. Solve the following:

- Convert  $(9786.3247)_{10}$  to hexadecimal.
- Convert  $(324.213)_5$  to decimal number.
- Convert  $(-27)_{10}$  to an 8-bit binary number.

1B. Given the Boolean function  $f(abcd) = a + \bar{a}\bar{b}c + \bar{b}\bar{d}$ . Without minimizing, realize using

- Two input NAND gates
- Two input NOR gates.

1C. Solve the following:

- $(418.59)_{BCD} - (378.28)_{BCD}$ , using 10's complement addition.
- $(1011.0101)_2 - (110.101)_2$ , using 2's complement addition.

((2+2+2) + (3+3) + (5+3)=20 marks)

2A. Simplify the following expressions using Boolean algebra:

- $F(abc) = \bar{a}\bar{b}\bar{c} + \bar{a}\bar{b}c + \bar{a}b\bar{c} + \bar{a}bc + a\bar{b}\bar{c} + a\bar{b}c + abc + ab\bar{c}$
- $F(ABC) = (A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + \bar{C})$
- $F(xyz) = \bar{x}\bar{y}\bar{z} + xz + \bar{y}z + xyz$

2B. Convert the following Boolean function  $F(A, B, C) = (A + B)(\bar{B} + AC)(A + \bar{C})$  into SOP form, Canonical SOP form, POS form and canonical POS form.

2C. Explain features of 2 out of 5, 2421 and 24-2-1 BCD codes.

((2+2+2)+8+6=20 marks)

3A. Design BCD to Excess 3 converter using minimum logic gates.

3B. Design full subtractor using two input NOR gates.

3C. Realize the function  $f(abcd) = \sum(0,2,5,7,8,9,13,14,15)$  using 8x1 multiplexer using least significant inputs as select lines.

(12+4+4=20 marks)

4A. Realize 16 to 1 multiplexer using 2 to 1 multiplexers. Also write the truth table.

4B. Using k-map, simplify the following Boolean functions in product of sum form and realize using logic gates.

(i)  $f(wxyz) = \sum m(1,2,3,4,6,8,9,10,11).$

(ii)  $f(abcd) = \prod M(1,5,6,7,11,12,13,15)$

4C. Using 1 to 4 demultiplexer, implement 4 to 16 decoder as a max term generator.

(6+(4+4)+6=20 marks)

5A. Define the following terms with syntax, with respect to VHDL.

- i. Process
- ii. Variable
- iii. Entity

5B. Explain OTPROM, EEROM, Flash, SRAM, DRAM, PSRAM, briefly.

5C. Write a VHDL code for four bit parallel adder using full adder as a component.

(6+6+8=20 marks)

6A. Derive characteristic equations for SR, JK, T and D flipflops.

6B. Using D-flipflops, design a mealy synchronous sequential circuit to detect an overlapping sequence 1010.

(10+10=20 marks)

7A. Design the four bit universal shift register using D flipflops and explain its operations.

7B. Using positive edge triggered JK flipflops, design mod 16 ripple counter which can be controlled to count up or down.

7C. Sketch a four bit Johnson's counter using D-flipflops. Draw the timing diagram.

(6+8+6=20 marks)

8A. Design Mod 8 synchronous up counter using JK flipflops. Also draw the timing diagram.

8B. Implement following Boolean functions using 3X 2 ROM:

$$f1(a, b, c) = \sum (1,2,4,6,7), \quad f2(a, b, c) = \sum (1,3,4,5)$$

(12+8=20 marks)

