

INTERNATIONAL CENTRE FOR APPLIED SCIENCES

(Manipal University)

III SEMESTER B.S. DEGREE EXAMINATION – MAY 2016

SUBJECT: D.C & A.C CIRCUIT ANALYSIS (EE 232)

(BRANCH: IP/ MECH)

24TH MAY, 2014

Time: 3 Hours

Max. Marks: 100

✓ **Answer ANY FIVE full Questions.**

1. (A) For the circuit shown in Fig. 1(A), find the equivalent resistance as seen from the terminals A and B using star-delta transformation (7 mark)
- (B) For the circuit shown in Fig. 1(B), find the current through $6\ \Omega$ resistor using mesh current analysis. (7 mark)
- (C) For the circuit shown in Fig. 1(C), determine the voltage across the terminals A and B using source transformation (6 mark)

2. (A) An alternating current varying sinusoidally with a frequency of 50Hz has an rms value of 20A. Write down the equation for the instantaneous value and find the corresponding value:
 - i. 0.0025 sec
 - ii. 0.0125 sec after passing through a positive maximum value
 - iii. At what time, measured from positive maximum value, will the instantaneous current be 14.14A? (10 mark)
- (B) Prove that the power absorbed by a pure capacitor and an inductor connected an AC source is zero. (10 mark)

3. (A) Find the value of RL which receives maximum power of the circuit shown in Fig. 3(A) and hence find the power. (10 mark)
- (B) State Norton's theorem. For the circuit shown in Fig. 3(B), find the value of I_b using Norton's equivalent circuit. Take $R = 667\ \Omega$. (10 mark)

4. (A) A 200V, 50Hz sinusoidal supply is connected to a parallel network comprising three branches A, B and C as follows:

Branch A – A coil of resistance $3\ \Omega$ and inductive reactance $4\ \Omega$

Branch B – A series circuit of resistance $4\ \Omega$ and capacitive reactance $3\ \Omega$

Branch C – A capacitor

Given that the power factor of the combined circuit is unity; find:

- i. The capacitance of capacitor
- ii. The current taken from the supply (10 mark)

(B) A coil of resistance $10\ \Omega$ and inductance 0.1H is connected in series with a capacitor $150\ \mu\text{F}$ across 200V , 50Hz supply. Calculate:

- i. Inductive Reactance
- ii. Capacitive Reactance
- iii. Impedance
- iv. Current
- v. Power Factor
- vi. Voltage across the coil and capacitor (10 mark)

5. (A) Explain current resonance. Obtain the expression for resonant frequency f_0 and current magnification for the circuit shown in Fig 5(A). (10 mark)

(B) A circuit having a resistance of $50\ \Omega$ and inductance $0.4\ \text{H}$ and a variable capacitance in series is connected across 110V , $50\ \text{Hz}$ supply. Calculate:

- i. The value of capacitance to give resonance
- ii. Current
- iii. Voltage across the inductance
- iv. Voltage across the capacitance
- v. Q-factor of the circuit (10 mark)

6. (A) Find the current through the galvanometer G of resistance $50\ \Omega$ in the circuit shown in Fig. 6(A) using Thevenin's theorem. (10 mark)

(B) Obtain the conditions for maximum power transfer across load terminals when:

- i. Load resistance is equal to source resistance
- ii. Load resistance is equal to magnitude of source impedance
- iii. Load impedance is equal to complex conjugate of source impedance.

(10 mark)

7. (A) Calculate the Z_{eq} and Y_{eq} of the circuit shown in Fig. 7(A) and the power consumed in the impedance $2+5j$. (10 mark)

(B) A choke coil is connected to 240V ac supply. When the frequency of the supply is 50Hz , an ammeter connected in series with the choke coil reads 60A . On increasing the frequency to 100Hz , the same ammeter reads 40A . Calculate the resistance and Inductance of the choke coil. (10 mark)

8. (A) While measuring three phase power by two wattmeter method, the following observations were made. Indicate the load power factor in each case.

- i. When both the meters show same reading
- ii. One of the wattmeter shows zero reading
- iii. One wattmeter shows double the reading than the other. (03 mark)

(B) A balanced load of $8 + 6j$ ohms per phase is connected to a 3 phase 400V supply. Find the line current, power factor, real power, reactive power and total apparent power when the system is connected in:

- i. Star
- ii. Delta (10 mark)

(C) Show that in a three phase system with balanced load, two wattmeters are sufficient to measure the power. (7 mark)

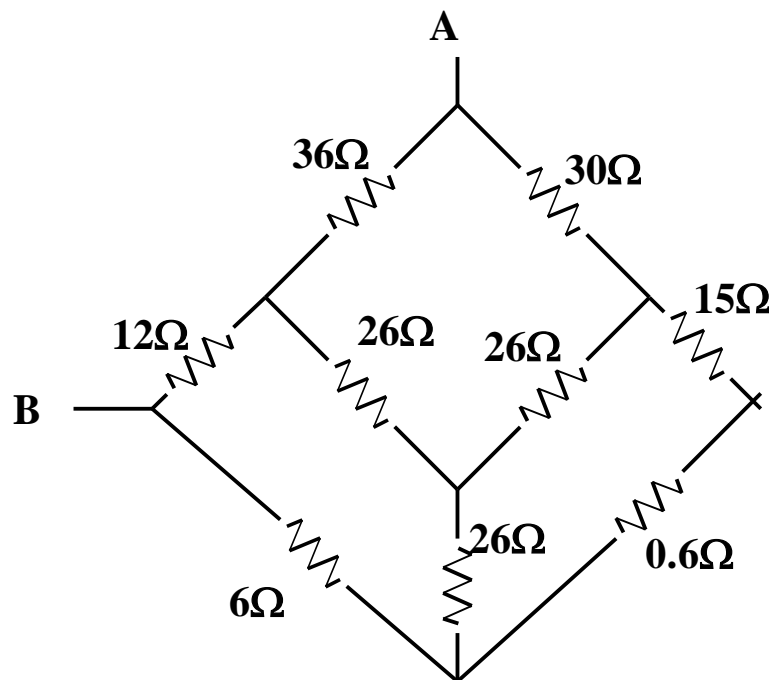


Fig. 1(A)

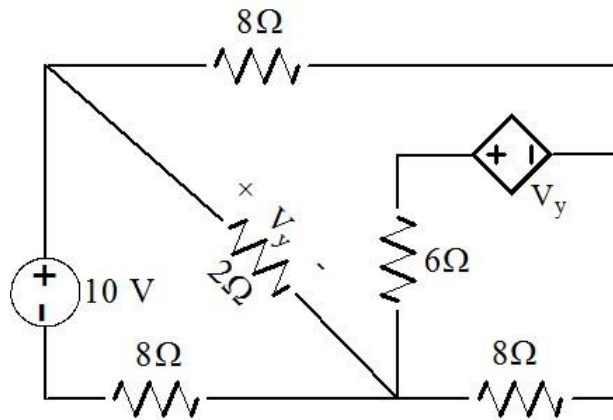


Fig. 1(B)

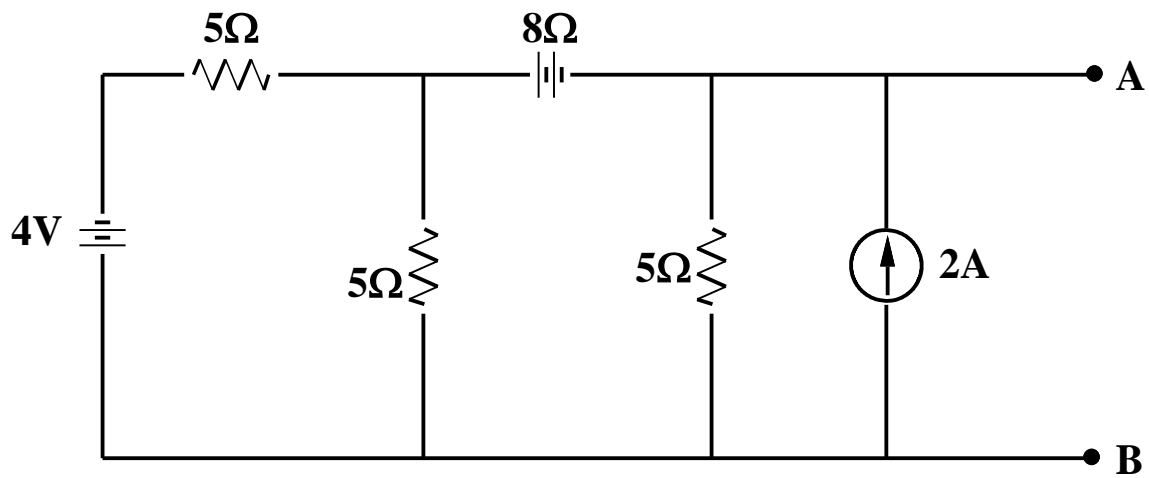


Fig. 1(C)

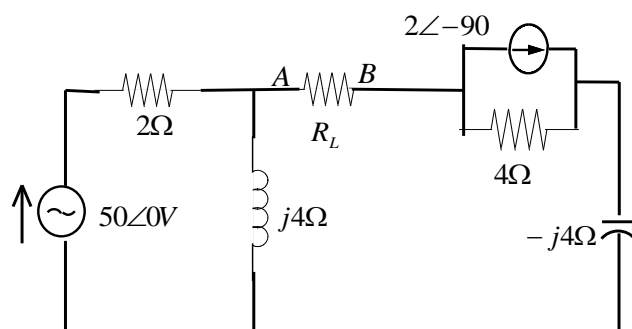


Fig. 3(A)

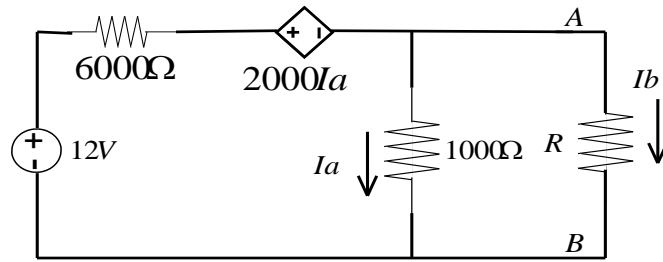


Fig. 3(B)

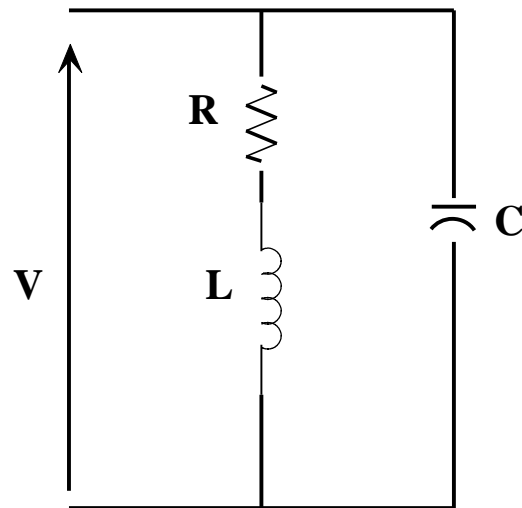


Fig. 5(A)

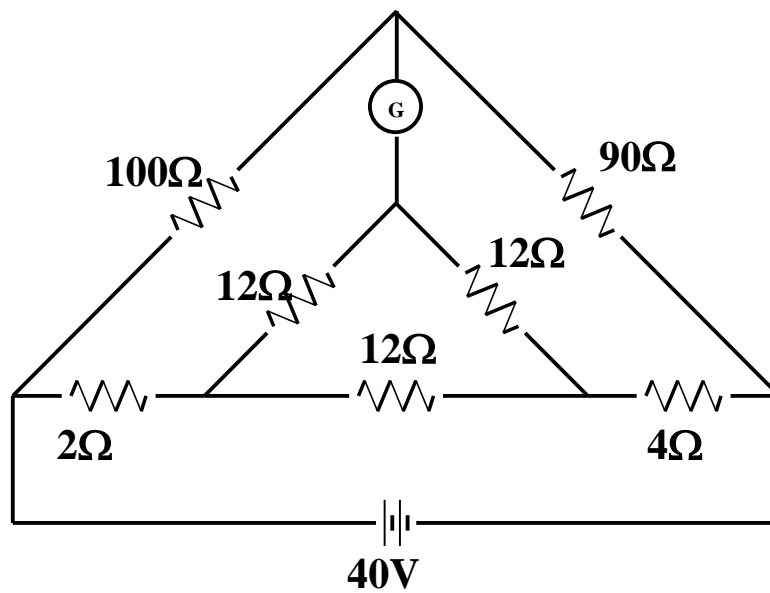


Fig. 6(A)

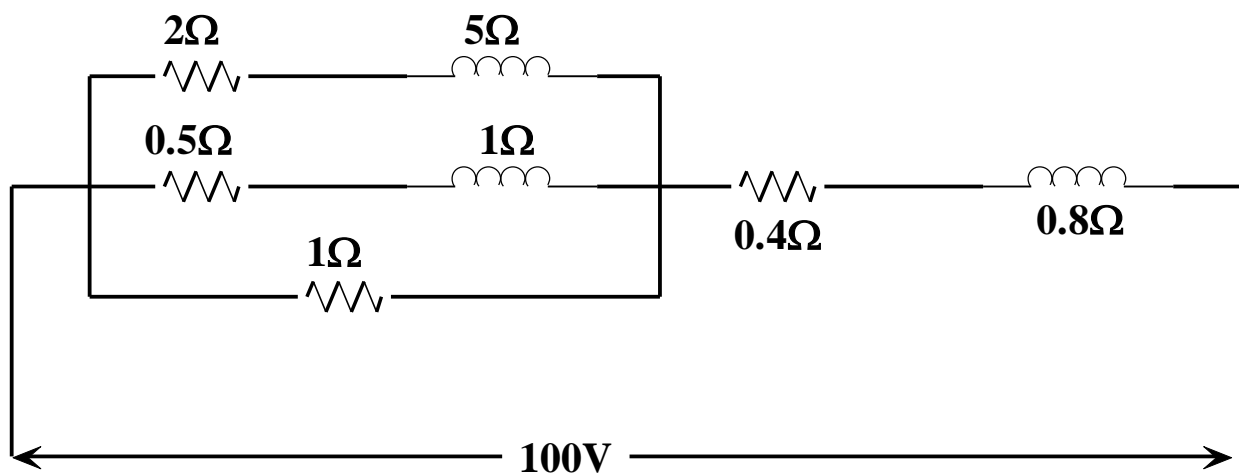


Fig. 7(A)

