## (BRANCH: COMPUTER ENGG \ E&C \ E&E) 24<sup>TH</sup> MAY, 2016 **Time: 3 Hours** Max. Marks: 100 ✓ Answer ANY FIVE Questions. Determine whether or not the signal x(t) is periodic. If the signal is periodic determine its fundamental period and frequency radian. in $\mathbf{x}(t) = \cos\left(\frac{\pi t}{3}\right) - \sin\left(\frac{\pi t}{5}\right) + 6\cos\left(\frac{\pi t}{4} + \frac{2\pi}{3}\right)$ Write the equation of the waveform shown in Fig. 1B in terms of step and ramp signals. Also, sketch its first derivative. Evaluate the integrals $I. \quad \int_{-\infty}^{\infty} \delta(t-5) [u(t-2) - r(t-4)] dt$

- II.  $\int_{-\infty}^{\infty} \cos t \left[ \delta(t-\pi) \delta(t-\frac{\pi}{2}) + \delta^{11}(t-\frac{\pi}{4}) \right] dt$  **2A.** The first derivative of the function f(t) is given by  $f^{1}(t) = 2u(t) - 4u(t-1) + u(t-2) + u(t-3) + u(t-4) - u(t-5)$  Sketch f<sup>1</sup>(t) and **8** f(t).
- **2B.** For the waveform shown in Fig.2B, determine the value of K such that (i)  $\int_{-\infty}^{\infty} f(t)dt = 0$  (ii)  $\int_{0^+}^{\infty} f(t)dt = 0$
- **2C.** Find odd and even components of the signal shown in Fig.2C
- **3A.** In the circuit of Fig. 3A, the switch is closed at t = 0. Find  $v_1$  and  $\frac{dv_1}{dt}$  at t = 0<sup>+</sup>. **10**
- **3B.** In the network shown in Fig.3B, the switch is opened at t=0. At t=0+, solve for the values of dv/dt and  $d^2v/dt^2$  if I=10amp, R=1000 $\Omega$  and C=1uf.
- **4A.** In the network shown in Fig.4A the switch is closed at t = 0. Determine *i*  $\frac{di}{dt}and\frac{d^2i}{dt^2}$  at t = 0<sup>+</sup>.
- **4B.** Find the Laplace transform of the periodic waveform shown in Fig. 4B
- 5A. In the network shown in Fig.5A, switch moves from position 1 to position 2 at t=0. Find the total current response. Use Laplace transforms method.10
- 5B. In the network of Fig.5B, switch is changed from position 1 to position 2 at t = 0. Find the expression for current through the inductor for t > 0 using time 10 domain analysis.

प्रज्ञानं ब्रह्म Manipal

1A.

1B.

1C.

## INTERNATIONAL CENTRE FOR APPLIED SCIENCES (Manipal University) III SEMESTER B.S. DEGREE EXAMINATION –MAY 2016 SUBJECT: LINEAR NETWORKS: TRANSIENT ANALYSIS (EE 231) (BRANCH: COMPUTER ENGG \ E&C \ E&E) 24<sup>TH</sup> MAY, 2016

Reg. No.

6

4

8

6

8

10

10 10

- **6A** In the network of Fig.6A, switch is opened at t = 0. Determine the current  $i_{L}(t)$  **10** for  $t \ge 0$ .
- **6B** In the network of Fig.6B, switch is changed from A to B at t = 0. Find the current response using Laplace Transform method. **10**
- **7A** A voltage of  $v(t) = 6e^{-3t}$  is applied to a series RL network with R = 5 $\Omega$  and L = 0.25H at t = 0. Find the voltage across the inductor for t > 0 using convolution integral theorem. **10**
- **7B** A function f(t) has its poles at s = 0 and s = -2 and zero at s = -5. The final value of the function is 5. Find f(t).
- **8A** Plot the pole zero diagram for the system  $\frac{(s+1)(s^2+1)}{s(s+2)(s^2+4)}$ . Obtain f (t) using pole zero diagram.
- **8B** Using convolution integral obtain the f(t) of a function  $F(s) = \frac{3}{s(s^2+4)}$ . Then verify your answer with pole zero map.











Fig. 4A

10

10



Fig. 6B