



- (C) For a typical BJT RC phase shift oscillator, derive an expression for each of the following: frequency of oscillations, phase of the loop gain and minimum value of  $h_{fe}$ . 8
4. (A) Determine the necessary transformer turn ratio for transferring maximum power to a  $16\Omega$  load from a source that has an output impedance of  $10\text{ K}\Omega$ . Also calculate the voltage across the external load if the terminal voltage of the source is  $10\text{V rms}$ . 6
- (B) What do you understand by multistage transistor amplifier? Mention its need. Draw a typical transformer coupled multistage amplifier. 6
- (C) How does the RC coupled transistor amplifier operate? Draw its circuit diagram and the low frequency model. 8
5. (A) Determine the input power, output power, and efficiency resulting in a class B amplifier providing a signal of  $20\text{ volt peak}$  to a  $10\text{ Ohm}$  load, using a single supply of  $V_{cc} = 30\text{v}$ . 6
- (B) Derive an expression for the conversion efficiency of a class A power amplifier circuit. Explain the operation of series fed Class A power amplifier circuit. 6
- (C) With a circuit diagram of class A push pull power amplifier circuit, explain its working. Mention the advantages of a push pull system. 8
6. (A) Show that the input impedance of the RC network of a RC phase shift oscillator at the frequency of oscillation is  $(0.83-j2.7)R$ . 6
- (B) Derive an expression for the frequency of oscillation of the Colpitts oscillator circuit. 6
- (C) For a parallel resonant circuit, prove mathematically how the circuit tends to become more selective and illustrate the resonance curve. 8