

5. (a) A square wave whose peak to peak value is 10 volt extends ± 5 volts with respect to ground. The duration of the positive section is 0.1msec and of the negative section is 0.2msec. If this waveform is impressed upon an RC high pass circuit whose time constant is 0.2msec, what are the steady state maximum and minimum values of the output wave form? 07
- (b) Derive the expression of output if a ramp waveform $V_i = \alpha t$ is applied to a high pass RC circuit, whose time constant is RC, where α is the slope of the ramp wave. 07
- (c) (i) The input voltage V_i is a sinusoidal waveform, is applied to the clipping circuit shown in fig.Q5c. Sketch the output voltage V_o and draw the transfer characteristics V_i vs V_o . Consider diode to be ideal. 06
- (ii) With the polarity of the diode interchanged, repeat part (i)

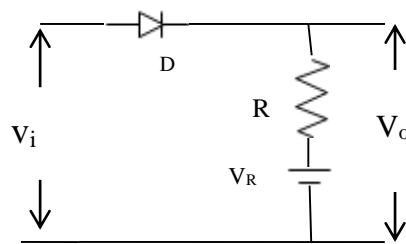


Fig.Q5c

6. (a) Draw the circuit of a mono-stable multi-vibrator circuit using transistors. Explain its operation with waveforms and derive the relation of pulse width. 10
- (b) Draw the circuit of a fixed biased binary using silicon *npn* transistors. 10

For this circuit $h_{FE \min} = 30$. The junction saturation voltages are,

$$V_{CEsat} = 0.2 \text{ Volts}, V_{BEsat} = 0.8 \text{ Volts}.$$

The circuit parameters are,

$V_{CC} = 12 \text{ Volts}$, $V_{BB} = -3 \text{ volts}$, $R_1 = 5K\Omega$, $R_2 = 10K\Omega$, $R_C = 1K\Omega$. Find the stable state voltages and currents.