



Reg. No.									
----------	--	--	--	--	--	--	--	--	--

MANIPAL INSTITUTE OF TECHNOLOGY
Manipal University



FOURTH SEMESTER B.TECH (E & C) DEGREE END SEMESTER EXAMINATION
JAN/MAY 2016
SUBJECT: IC SYSTEMS (ECE - 202)

TIME: 3 HOURS

MAX. MARKS: 50

Instructions to candidates

- Answer **ANY FIVE** full questions.
- Missing data may be suitably assumed.

- 1A. Draw the circuit diagram of an emitter coupled differential amplifier. Derive the expressions for the following: i) Differential gain ii) Common mode gain and iii) CMRR
- 1B. Design a current mirror circuit to mirror a current of 5mA. Assume transistors used are identical and β of 50 and V_{BE} of 0.7V.
- 1C. Why is the emitter resistor and collector resistor replaced by a constant current in differential amplifier?
(5+3+2)
- 2A. Using single Op-amp, design a suitable circuit to solve the following equation.
 $V_0 = 5V_1 + V_2 - V_3 - 2V_4$. (Do not invert the inputs)
- 2B. With necessary derivation and circuit explain the measurement of input and output impedance of an Op-amp.
- 2C. Find the gain V_0/V_1 for the circuit shown in **Fig.2C**
(5+3+2)
- 3A. With the help of a circuit diagram and analysis explain the working of instrumentation amplifier using three OPAMPs. Mention any three features of the circuit.
- 3B. Design a third order Butterworth low pass filter for the cut off frequency of 3.3kHz and pass band gain of 10.
- 3C. Design a circuit using single OPAMP to obtain output $V_0 = 5V_1 - 3V_2$ where V_1 and V_2 are the inputs.
(5+3+2)
- 4A. With the help of a circuit diagram and input-output waveforms, explain the working of full wave precision rectifier. Also derive the expression for the output voltage.
- 4B. With the help of a circuit diagram and waveforms, explain the working of sample and hold circuit.
- 4C. Design an inverting Schmitt trigger for the following specifications:
 $V_{UT} = 4V$, $V_{LT} = -4V$
 $+V_{CC} = -V_{EE} = 12$ Volts
(5+3+2)

- 5A. Draw a circuit of dual slope integrating type ADC. Explain the process of conversion with suitable example. Derive the equations used.
- 5B. Draw a circuit of R-2R 2-bit DAC. Give the expression for the output voltage. List its advantages over Binary weighted resistor type DAC.
- 5C. Define the following terms with respect to ADC/DAC (i) Linearity (ii) Accuracy
(5+3+2)
- 6A. Analyse application of IC NE555 timer as a linear ramp generator.
- 6B. Draw the block diagram of PLL. Explain the functions of each block.
- 6C. Design a square wave generator using IC555 to obtain a frequency of 5 kHz, duty cycle of 30%.
(5+3+2)

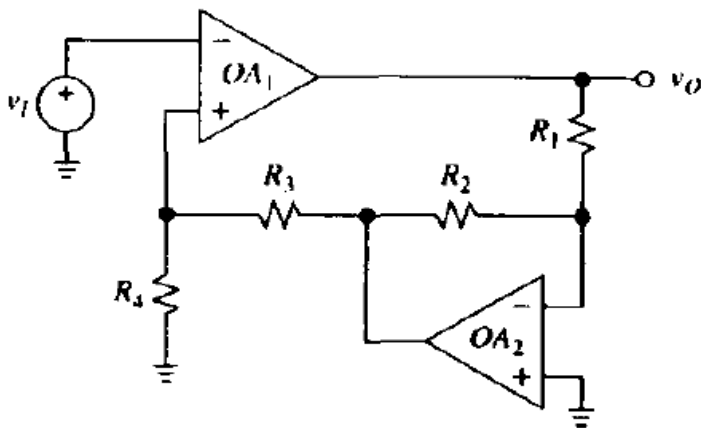


Fig. 2C