



# Manipal Institute of Technology, Manipal

(A Constituent Institute of Manipal University)



## II SEMESTER M.TECH (PESC) MAKEUP EXAMINATIONS, JUNE 2016

SUBJECT: POWER SEMICONDUCTOR CONTROLLED DRIVES [ELE 506]

REVISED CREDIT SYSTEM

Time: 3 Hours

28 JUNE 2016

MAX. MARKS: 50

### Instructions to Candidates:

- ❖ Answer **ANY FIVE FULL** questions.
- ❖ Missing data may be suitably assumed.
- ❖ Sine graph sheets shall be supplied, if required.

- 1A. Explain steady state stability and draw the speed-torque characteristic of DC CLM drive. **(05)**
- 1B. What are the main factors which decide the choice of electrical drive? **(05)**
- 2A. Explain the operation of a single phase fully controlled rectifier fed by a separately excited DC motor in continuous conduction mode. Draw the switch voltage, load voltage, source and output current waveforms. **(06)**
- 2B. A 220 V, 1500 rpm DC motor has  $R_a = 2 \Omega$  and  $L_a = 28.36 \text{ mH}$  respectively. It is controlled by 3 phase fully controlled rectifier from an AC source operating at 50 Hz.  $V_m = 230.38 \text{ V}$ ,  $K = 1.25$ ,  $Z = 9.13 \Omega$ ,  $\psi = 1.35 \text{ rad}$ . Calculate  $I_{ac}$  and  $T_{ac}$  values for  $\alpha = 60^\circ$ ,  $T_a = 1 \text{ Nm}$ . **(04)**
- 3A. Explain the operation of class B chopper and derive the expression for maximum and minimum armature currents with relevant waveforms. **(06)**
- 3B. A 220 V, 24 A, 100 rpm separately excited DC motor has a  $R_a = 2 \Omega$ . The motor is controlled by a chopper with a frequency of 500 Hz and a source voltage of 230 V. Calculate the duty ratio for 1.2 times the rated torque and 500 rpm. **(04)**
- 4A. Explain the static Kramer's system with a neat diagram. **(05)**
- 4B. Explain the brushless DC excitation of wound field synchronous machine drives. **(05)**
- 5A. Explain the vector control scheme of PMSM drive with a block diagram. **(05)**
- 5B. Explain the direct torque control scheme of AC motors with a neat block diagram. **(05)**
- 6A. Discuss any two mitigation methods of AC variable frequency drives in detail. **(05)**
- 6B. What is remote power quality monitoring? Explain the role of multi-stage converters in electrical traction system. **(05)**