



FIRST SEMESTER M.Tech. (INDUSTRIAL AUTOMATION AND ROBOTICS) DEGREE
END SEMESTER EXAMINATION
November /December 2016
SUBJECT: ANALOG AND DIGITAL ELECTRONICS (MTE-5131)

TIME: 3 HOURS

MAX. MARKS: 50

Instructions to candidates

- Answer **ANY FIVE** full questions.
- Missing data may be suitably assumed.

1A.	Servokon systems has recruited you as a design engineer. Your first task is to design a circuit for a voltage stabilizer that clamps the input waveform by 5 V. Design the circuit using an op-amp with necessary waveforms to support your design. (7)
1B.	Give a short note on the design of an Integrator using an op-amp. Support your answer with suitable equations. (3)
2A.	Differentiate between low pass and high pass active filters with suitable circuit diagrams. (3)
2B.	Velodynelidar is a manufacturer of LiDAR equipment used in scanners and sensors. Suggest the design of a filter that passes green color light only in the range of 520-560 nm. (7)
3A.	According to the system shown in Fig. 3 A below, design a 5421 to 8421 code converter. (5)
3B.	The operating conditions (ON = 1 and OFF = 0) of three pumps (x, y, z) are to be monitored. x = 1 implies that pump x is ON, and so is the case for pumps y and z. It is required that the indicator LED, P shown in Fig. 3 B below, should glow if majority of the pumps fail. Enter the logical values in the K-map in the format shown in Fig. 3 B, and derive the SOP expression, whose output is logical value 1, when a majority of the pumps fail. (5)
4A.	Describe the architecture of the Xilinx 3020 CLB with a suitable circuit diagram. (5)
4B.	Differentiate between the shareable and parallel expanders used in the ALTERA 7000 series of FPGAs. (5)
5A.	Analyse the Fig 5A and answer the following questions: i. What is the content of DATA register? ii. What would be the output for the instruction accessing DATA [8] [2]? iii. What would be the output for the instruction accessing DATA [8] [6:2]? (3)
5B.	Write a Verilog program to perform the gate level modelling of the circuit shown in Fig 5 B. (7)
6A.	Analyse the sequential circuit shown in Fig 6 A. (5)

- 6B. Design a sequential circuit using D flip flops for a lift that operates for two floors, GROUND and FIRST. When the UP button is pressed, the lift goes from GROUND to FIRST floor and a RED LED glows. When the DOWN button is pressed, the lift goes from FIRST to GROUND floor and a GREEN LED glows. Arrive at the final circuit by first designing the finite state machine (state diagram). (5)

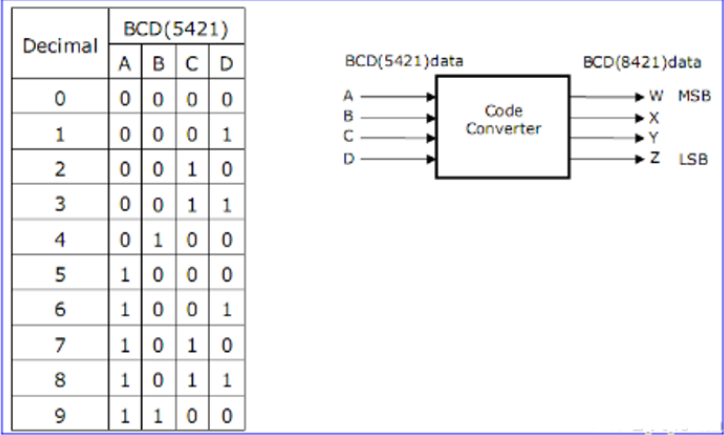


Figure 3A

 


Figure 3B

Verilog Code:
 reg [8:1] DATA;
 reg DRAM [10:1];
 DATA = DRAM [8];

DRAM Memory:

10101010
11011010
11111111
00000000
11110000
00001111
01010101
11001100
00110011
00011100

Figure 5A

 


Figure 5B

 


Figure 6A