

MANIPAL UNIVERSITY
SCHOOL OF INFORMATION SCIENCES

SECOND SEMESTER MASTER OF ENGINEERING – ME (VLSI DESIGN)
 DEGREE EXAMINATION – APRIL / MAY 2016

SUBJECT: EDA 616.11 (ELECTIVE 2) – ADVANCED LOGIC SYNTHESIS

Friday, May 6, 2016

Time: 10.00 – 13.00 Hrs.

Max. Marks: 100

1. A. Define synthesis and name at least 4 optimization criteria for synthesis.
 B. Write synthesizable Verilog code for a 4- bit shift register
 (5x2=10 marks)

2. Give the general formula for Shannon expansion and expand the following by taking A as splitting variable.
 A. $F = AB + AC + BC$
 B. $F = A'C + BC' + A'B'C + AB'C'$
 (5x2=10 marks)

3. Using Quine-McClusky method find the minimal SOP expressions of
 $F(w,x,y,z) = \sum 0,1,2,3,4,5,6,8,11,12,14$
 (10 marks)

4. Simplify the following by applying the consensus theorem.
 A. $wxy + wx'z + wyz$;
 B. $vw'y + vyz + wyz$
 C. $ab'c + bc'd + ad$
 D. $abc'd + c'd'e + abc'e$
 E. $abc + c'd + a'b$
 (2x5=10 marks)

5. Find minimum for following two-level multiple-output for the function and mention the reduction in number of Inputs & Gates
 $F1(A,B,C,D) = \sum m(3,4,6,9,11),$
 $F2(A,B,C,D) = \sum m(2,4,8,10,11,12),$
 $F3(A,B,C,D) = \sum m(3,6,7,10,11)$
 (10 marks)

6. Explain the simplified design flow for FSM and draw a Moore machine for detecting an overlapped input sequence 10101.
 (10 marks)

7. Find the equivalence partition by iterated collapsed approach and a corresponding reduced machine for the following sequential machine:

PS	x = 0	x = 1
1	2, 0	5, 0
2	5, 0	4, 0
3	4, 1	1, 0
4	3, 1	5, 0
5	2, 0	4, 0

(10 marks)

8. Find the prime compatibles of the incompletely specified FSM shown below

PS	NS, Output	
	I1	I2
A	F, 0	C, -
B	-, -	F, 1
C	E, 0	B, -
D	A, 1	D, 0
E	C, -	D, 1
F	A, 0	A, -

(10 marks)

9. Solve the following Binate covering problem using reduction techniques

$$F = (x_1 + x_2 + x_4)(x_4')(x_2 + x_6)(x_1 + x_3 + x_5 + x_6)(x_6' + x_2 + x_4)(x_5' + x_4 + x_1)$$

(10 marks)

10. Consider the logic network defined by following expressions:

$$x = ad' + a'b' + a'd' + bc + bd' + ac$$

$$y = a + b$$

$$z = a'c' + a'd' + b'c' + b'd' + e$$

$$u = a'c + a'd + b'd + e'$$

- Draw the logic network graph.
- Perform the algebraic division f_x/f_y and show all steps.
- Substitute y into f_x and redraw the network graph.
- Compute all kernels and co-kernels of z and u .
- Extract a multiple-cube sub-expression common to f_z and f_u . Show all steps. Redraw the network graph.

(2x5=10 marks)
