

VI SEMESTER B.TECH ELECTRICAL & ELECTRONICS ENGINEERING

MAKEUP EXAMINATIONS JULY 2016

SUBJECT: POWER ELECTRONICS [ELE 304]

REVISED CREDIT SYSTEM

Time: 3 Hours

06 JULY 2016

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ANY FIVE FULL** questions.
- ❖ Missing data may be suitable assumed.

- 1A. Explain latching current, holding current and different modes of operation of an SCR with the help of its I-V characteristics. 05
- 1B. With the help of circuit diagram, and waveforms of load voltage and load current, explain the working of a single phase fully controlled full wave rectifier feeding an RL load with discontinuous current. Derive the average output voltage. 05
- 2A. With the help of neat diagram explain the Safe Operating Area (SOA) of Power BJT and MOSFET. 05
- 2B. With neat circuit diagrams and relevant waveforms analyse the forced current commutation circuit for a thyristor with a resistive load. 05
- 3A. What is the necessity of connecting SCR's in series? What are the problems associate with series connection of SCRs? How are they eliminated? 04
- 3B. An R-L-E load with $R = 2 \text{ ohms}$, $L = 20 \text{ mH}$ and $E = 100\text{V}$ is fed from a half wave controlled rectifier which is periodically gated at 45° . The input to the rectifier is 120 V , 60 Hz single phase AC supply. Determine the Power observed by the resistor and power absorbed by the dc source in the load average load voltage and current. 06
- 4A. With the help of neat circuit diagram, explain all possible quadrants of operation of Class E Chopper fed DC motor. 05
- 4B. Describe the working of the three phase fully controlled converter with RL load with continuous conduction mode. Draw the load voltage and load current at firing angle 60° . And also derive the average value of output voltage. 05
- 5A. With relevant circuit diagram and neat waveforms with proper triggering sequence discuss the effect of source inductance in 3 phase controlled rectifiers. 05
- 5B. Explain in detail the principle and operation of a step-up cyclo-converter with the help of a neat circuit diagram and output waveform for $f_0 = 8f_s$ where f_s is the supply frequency. 05
- 6A. Discuss the switching scheme for 120° mode of operation of three phase square wave inverter. Hence plot the phase voltages and any one line voltage waveform. 05
- 6B. With the help of neat circuit diagram and relevant waveforms explain the working of cascaded multilevel inverter. What are its advantages and disadvantages? Explain its target applications. 05