

Reg. No.									
----------	--	--	--	--	--	--	--	--	--



MANIPAL INSTITUTE OF TECHNOLOGY  
Manipal University



**SIXTH SEMESTER B.TECH (E & C) DEGREE END SEMESTER EXAMINATION**  
**MAY/JUNE 2016**  
**SUBJECT: ASIC DESIGN (ECE - 320)**

**TIME: 3 HOURS**

**MAX. MARKS: 50**

**Instructions to candidates**

- Answer **ANY FIVE** full questions.
- Graph sheet will be provided.
- Missing data may be suitably assumed.

- 1A. Perform the Stockmeyer algorithm on slicing floorplan shown in **FIG.1A**. The (width, height) of the blocks 1 through 8 are  $\{(2,4), (1,3), (3,3), (3,5), (3,2), (5,3), (1,2), (2,4)\}$ . Assume that  $xHy$  means  $x$  is top and  $y$  is bottom, and  $xV y$  means  $x$  is left and  $y$  is right. Place the lower left corner of each block to the lower left corner of its room.
- 1B. Briefly explain the ASIC design flow with a neat diagram.
- 1C. Find the propagation delay and contamination delay for the circuit shown in **FIG. 1C**.  $a_0$ - $a_6$  are the arrival delays and the delay contributed by each gate is written inside the gate.

(5+3+2)

- 2A. Find the minimum number of tracks using left-edge algorithm. Given that

TOP	3	1	3	0	0	5	6	0	3	0	0	0
Bottom	1	2	4	2	4	1	5	7	0	7	6	0

- 2B. Braille is a system which allows a blind person to read alphanumeric by feeling a pattern of raised dots (●) given in **TABLE 2B**. Design a circuit that converts BCD to Braille and implement the same Xilinx FPGA
- 2C. What is fixed-die routing?


(5+3+2)

- 3A. Given the following locations of a clock source  $s_0$  (7,1) and eight sinks  $s_1$  (2,2),  $s_2$  (4,2),  $s_3$  (2,12),  $s_4$  (4,12),  $s_5$  (8,8),  $s_6$  (8,6),  $s_7$  (14,8) and  $s_8$  (14,6). (a) Draw the clock tree generated by MMM. (b) Draw the clock tree topology generated by MMM. (c) Calculate the total wire-length (in terms of grid units) and the clock skew using the linear delay model.
- 3B. Find the maximum operating frequency for the circuit shown in **FIG. 3B**.
- 3C. Explain working of SRAM Cell.


(5+3+2)

- 4A. Implement a code converter using PLA that converts BCD messages into Excess-3 code. The converter has four input lines carrying signals labeled  $w$ ,  $x$ ,  $y$ , and  $z$ , and four output lines carrying signals  $f_1$ ,  $f_2$ ,  $f_3$ , and  $f_4$ .

- 4B. What is Routing congestion? Given **FIG. 4B** placement  $P$  of blocks  $a-f$  and their pins (right), nets  $N1-N3$ , local vertical cut-lines  $v1-v6$ , local horizontal cut-lines  $h1-h6$ , and  $\sigma P(e) = 3$  for all local cut-lines  $e \in E$ . find the wire density  $\Phi(P)$  and determine the routability of  $P$  based on the RMST model.  $N1 = (a1, b1, d2)$   $N2 = (c1, d1, f1)$   $N3 = (e1, f2)$ .
- 4C. Consider a process in which pMOS transistors have three times the effective resistance as nMOS transistors. Find the logical effort of three input NAND gate.
- (5+3+2)
- 5A. Write a Verilog code for positive edge triggered D-flip flop using primitive and its test bench.
- 5B. For machine shown in **TABLE 5B**, find the equivalence partition and the corresponding reduced machine in standard form.
- 5C. Explain the partitioning. What is the quality of good partitioning?
- (5+3+2)
- 6A. Draw the layout of 3-input CMOS NAND gate using shared contacted diffusion for reduced parasitic capacitance.
- 6B. Write a Verilog program to generate a clock signal for  $t_{on}$  and  $t_{off}$  5 and 10 time unit respectively.
- 6C. What is week keeper circuit?
- (5+3+2)

 


**FIG. 1A**

 


**FIG. 1C**

**TABLE 2B**

A	B	C	D	W	X	y
0	0	0	0		•	•
0	0	0	1			
0	0	1	0	•		
0	0	1	1	•	•	
0	1	0	0	•	•	•
0	1	0	1	•		•
0	1	1	0	•	•	
0	1	1	1	•	•	•
1	0	0	0	•		•
1	0	0	1		•	

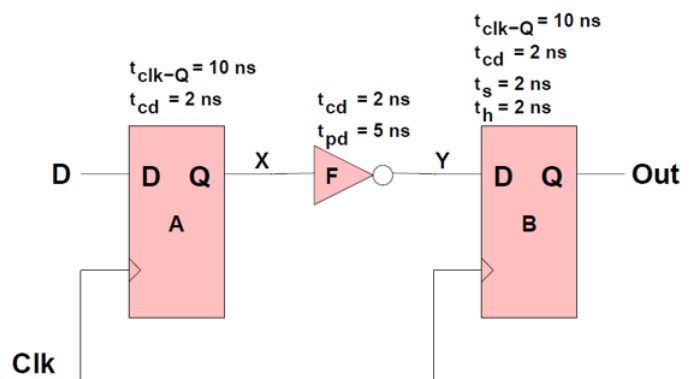

**FIG. 3 B**

 

**FIG. 4B**

<b>Table 5B</b>		
	NS, z	
PS	X=0	X=1
A	E,0	C,0
B	C,0	A,0
C	B,0	G,0
D	G,0	A,0
E	F,1	B,0
F	E,0	D,0
G	D,0	G,0