A Line		14
×1.		1 Miles
- A		Ser .
NSP.	IRED ON	LIFE



INTERNATIONAL CENTRE FOR APPLIED SCIENCES (Manipal University) IV SEMESTER B.S. DEGREE EXAMINATION – NOV./ DEC.2016 SUBJECT: ELECTRONIC DEVICES AND COMPUTER INTERFACING (CS 241) (BRANCH: CS & CE)

Thursday, 24 November 2016

Time: 3 Hours

Max. Marks: 100

- ✓ Answer ANY FIVE FULL Questions.
- ✓ Missing data may be suitably assumed.
- 1A. Design a Zener diode shunt regulated power supply with following specifications
 a) O/p voltage is 10V. b) Load current is 50mA c) Maximum power dissipation of 500mw and d) Input voltage 15 ± 2V
- 1B. Draw the circuit of negative and positive clamper and explain its operation with the input and output waveform. (10+10)
- 2A. For a full wave rectifier using center tapped transformer, derive a) Ripple factor b)The average value of load current c)The rms value of load current d)Efficiency of the rectifier.
- 2B. Explain with neat diagram operation of a) LED b) Photodiode.

(10+10)

- 3A. What are the drawback of fixed bias? How do you overcome it? Explain with neat circuit diagram the modified biasing circuit.
- 3B. Explain with neat circuit diagram RC-coupled amplifier. Explain all the components in them and why they are used. Draw the frequency response of the same.

(10+10)

- 4A. Explain Barkhausen criteria for sustained oscillations? Write the circuit of RC phase shift oscillator and explain its working. In an RC phase shift oscillator if the value of resistors are $R_1=R_2=R_3=150$ K Ω and the value of capacitors $C_1=C_2=C_3=0.25$ nF Determine the frequency of oscillation.
- 4B. Explain with neat block diagram flash type of ADC.

(10+10)

- 5A. Explain with circuit a differentiator and integrator circuit using OPAMP.
- 5B. Explain with circuit diagram a voltage follower (12+8)
- 6A. Explain with neat circuit diagram how SCR can be used as a half wave rectifier. How the output power can be controlled?
- 6B. Explain circuit using 555 timer that generates pulse output of 1.1msec every time a trigger is given (10+10)
- 7A. Explain how CMOS can be used as a NOT gate. What are the advantage of the CMOS?
- 7B. Write the block diagram of a data acquisition system and explain each of the functions of these blocks. (10+10)
- 8A. How many bits are required in a binary ladder to achieve a resolution of 1mV if full scale is +5V?
- 8B. Draw and explain the characteristics of following devices

a) Diac b) Zener diode c) pn diode d) TRIAC (4+16)

##