



III SEMESTER B.Tech. (BME) DEGREE MAKE-UP EXAMINATIONS DEC/JAN 2016-17

SUBJECT: NETWORK ANALYSIS (BME 2101)
(REVISED CREDIT SYSTEM)

Friday, 30th December 2016, 9 AM to 12 NOON

TIME: 3 HOURS

MAX. MARKS: 100

Instructions to Candidates:

1. Answer ALL questions.
2. Draw labeled diagram wherever necessary

- 1a)** For network shown in Fig. Q1a, Find the currents in all the branches of the resistors. (6)
Use mesh current analysis.

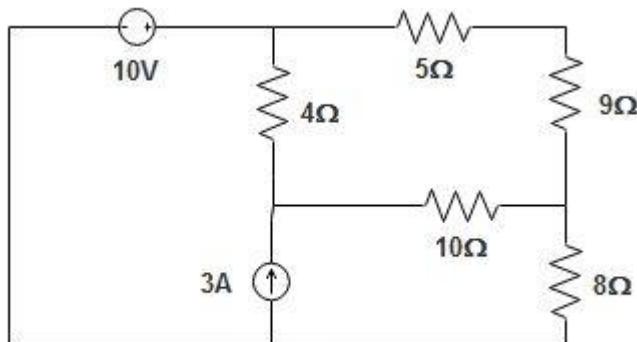


Fig.Q1a

- 1b)** For the network shown in Fig. Q1b, determine the value of R_L so that maximum power is delivered to it. What is the maximum power? (6)

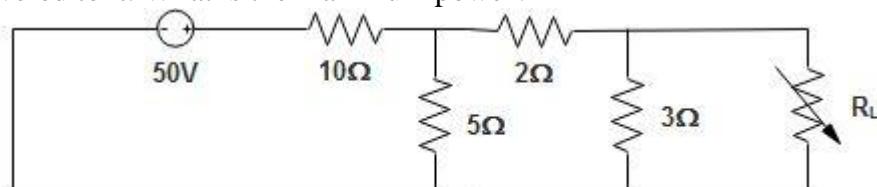


Fig.Q1b

- 1c)** For the network shown in Fig.Q1c, find the voltage v across 3Ω resistor using superposition theorem. (8)

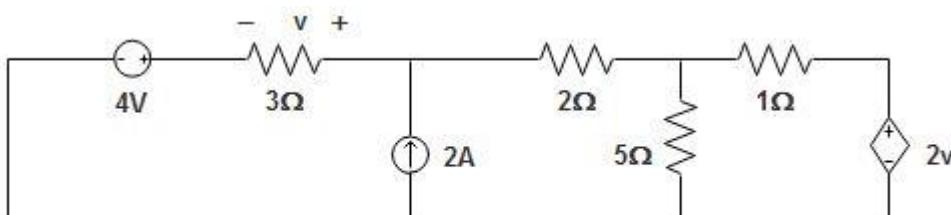


Fig.Q1c

- 2a) For the circuit shown in fig.Q2a, find the value of R_1 when the circuit resonates. (6)

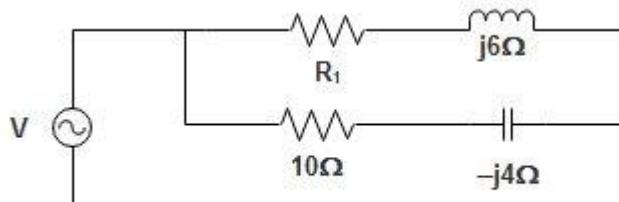


Fig.Q2a

- 2b) For the circuit shown in Fig.Q2b, Write the two mesh equations. (6)

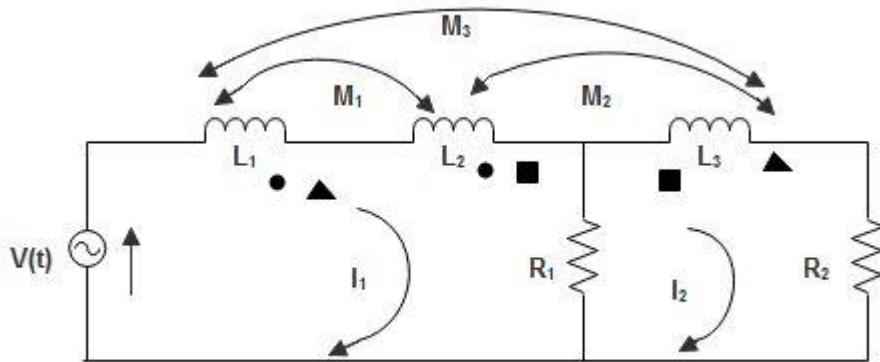


Fig.Q2b

- 2c) The network shown in the Fig.Q2c, find the current I in 10Ω resistor using Thevenin's theorem. (8)

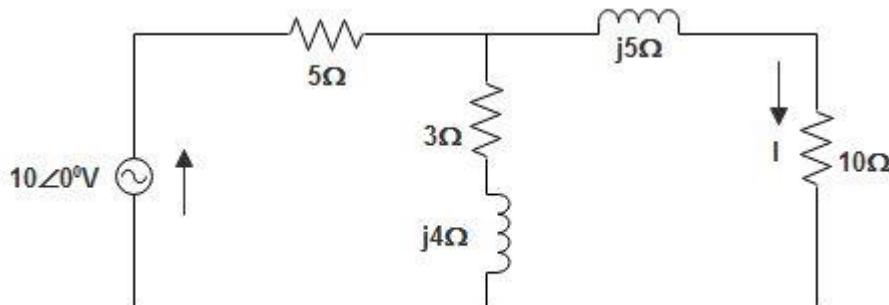


Fig.Q2c

- 3a) For the network shown in Fig.Q3a, obtain **STAR** equivalent circuit. (6)

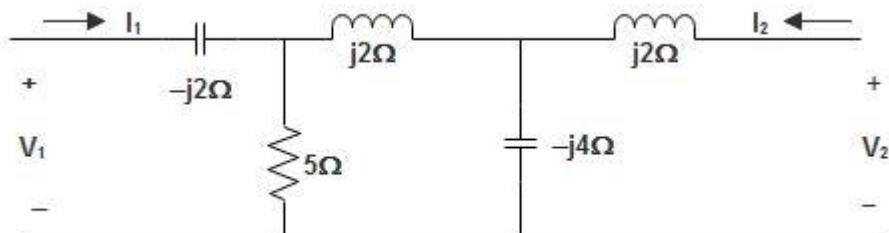


Fig.Q3a

- 3b) Find the Laplace transform of the following. (6)

$$(i) f_1(t) = 1 + 2t^3 - 4e^{3t} + 5e^{-t}$$

$$(ii) f_2(t) = 3 \cosh 4t + 4 \sin 3t$$

3c) State and prove initial value theorem and final value theorem. (8)

4a) In the network shown in Fig.Q4a, the switch K is closed at $t=0$. Find, (6)

$$(i) i(0^+) \quad (ii) \frac{di}{dt}(0^+) \quad (iii) \frac{d^2i}{dt^2}(0^+)$$

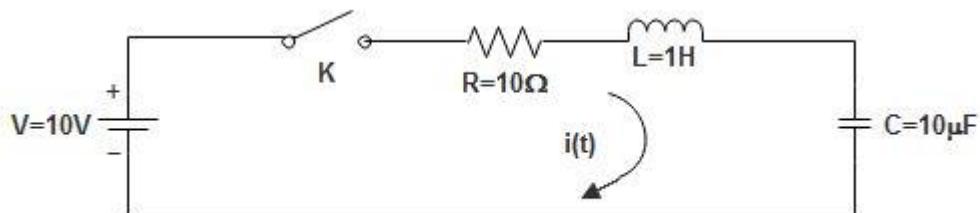


Fig.Q4a

4b) For the periodic waveform shown in the Fig.Q4b, obtain its Laplace transform $V(s)$. (6)

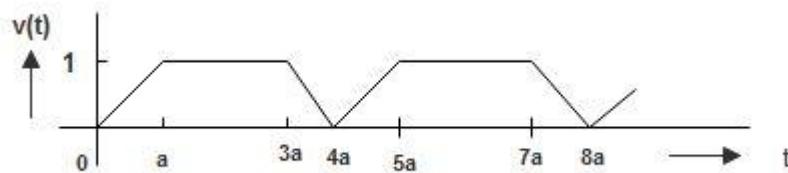


Fig.Q4b

4c) For the circuit shown in Fig.Q4c, the switch K is closed at $t=0$. With the network parameter values, solve for $i_2(t)$. (8)

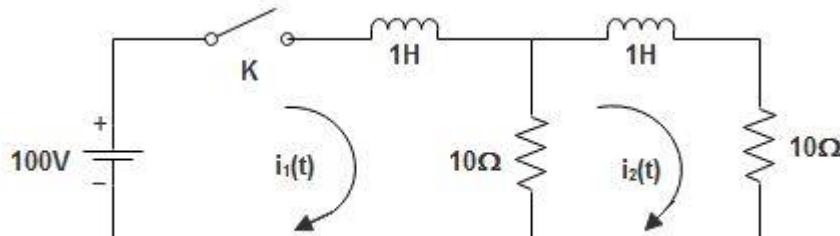


Fig.Q4c

5a) Convert Z parameters in terms of ABCD parameters. (6)

- 5b)** For the Twin T network shown in Fig.Q5b, find Y parameters. (8)

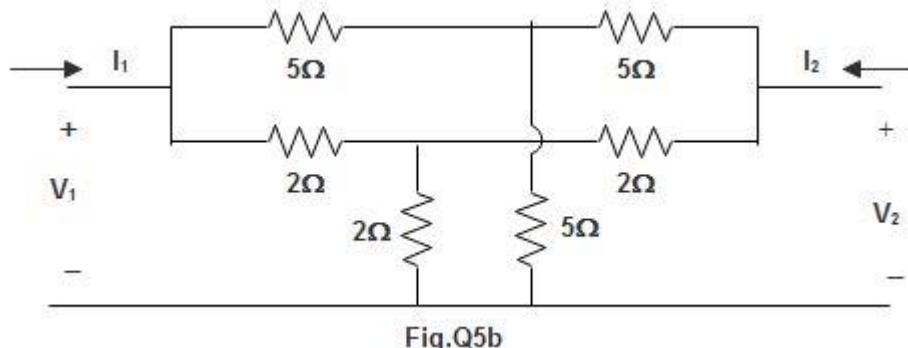


Fig.Q5b

- 5c)** For the network shown in Fig. Q5c, find $G_{12}(s) = \frac{V_2(s)}{V_1(s)}$ (6)

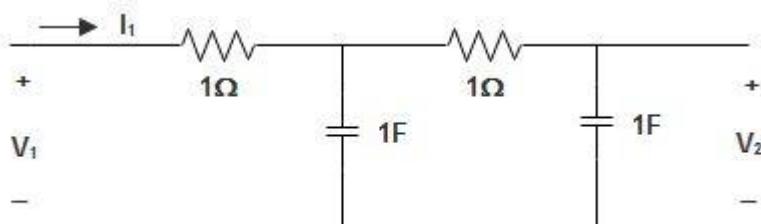


Fig.Q5c