

Reg. No.									
----------	--	--	--	--	--	--	--	--	--



MANIPAL INSTITUTE OF TECHNOLOGY
MANIPAL

A Constituent Institution of Manipal University

III SEMESTER B.Tech. (BME) DEGREE END SEM EXAMINATIONS NOV/DEC 2016

SUBJECT: NETWORK ANALYSIS (BME 2101)
(REVISED CREDIT SYSTEM)

Monday, 28th November, 2016, 9 AM to 12 NOON

TIME: 3 HOURS

MAX. MARKS: 100

Instructions to Candidates:

1. Answer ALL questions.
2. Draw labeled diagram wherever necessary

- 1a)** For network shown in Fig. Q1a, Find the current I . Then apply the Reciprocity theorem for this network and verify it. **(6)**

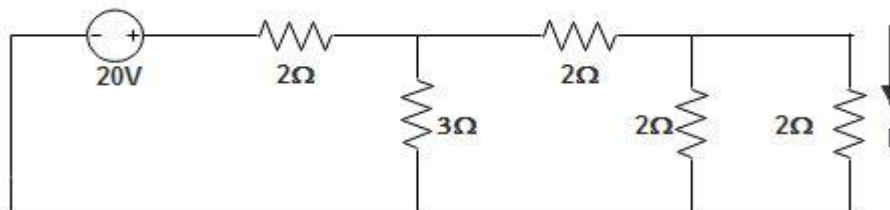


Fig.Q1a

- 1b)** For the network shown in Fig. Q1b, use node voltage analysis to find the branch current I . **(6)**

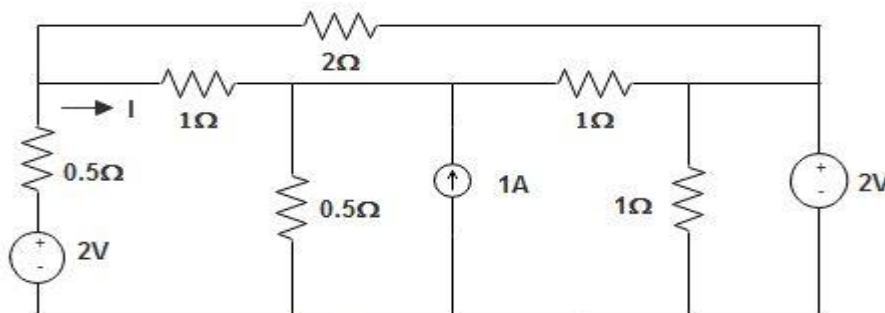


Fig.Q1b

- 1c)** For the network shown in Fig.Q1c, find the currents and power dissipated in all branches of resistors. **(8)**

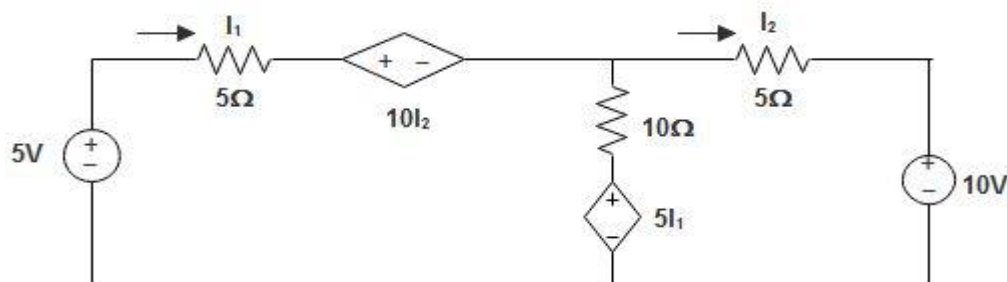


Fig.Q1c

- 2a) For the network shown in Fig.Q2a, determine the current I using Super position theorem. (6)

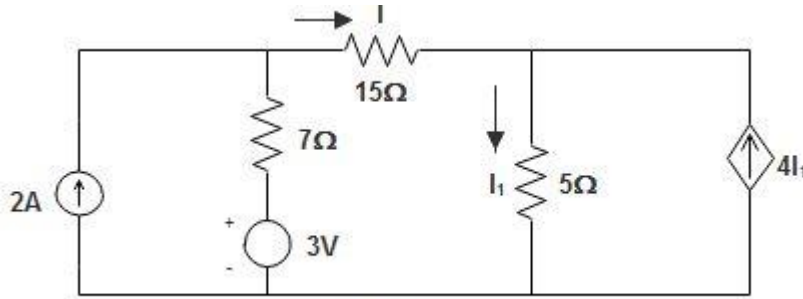


Fig.Q2a

- 2b) For the network shown in Fig.Q2b, the impedance Z_L is variable in both resistance and reactance. Find the value of Z_L to get the maximum power in the load. What is the maximum power? (6)

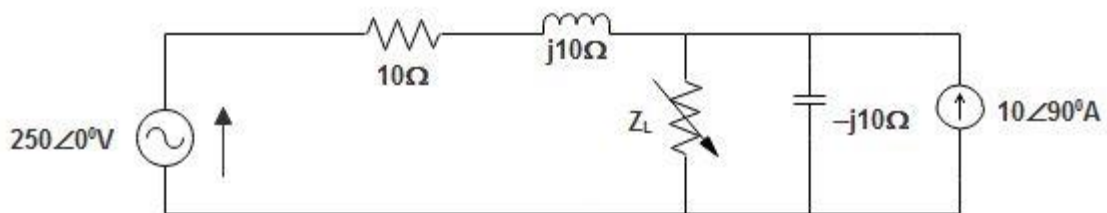


Fig.Q2b

- 2c) The network shown in the Fig.Q2c is a simple representation of a transistor. For the network determine Thevenin's equivalent network for the load R_L . (8)

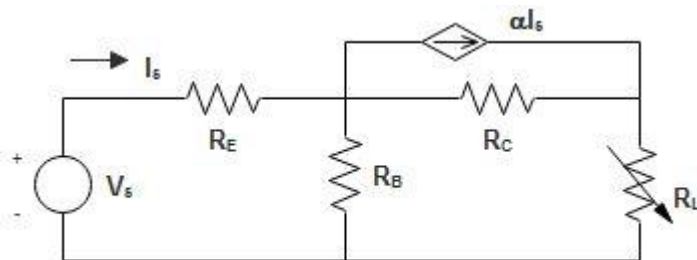


Fig.Q2c

- 3a) For a series RLC resonant circuit show that. (6)

$$Z = R(1 + j2Q_0\delta) \quad \text{where } \delta = \frac{f - f_0}{f_0}$$

- 3b) For the network shown in Fig. Q3b, find V_o . (6)

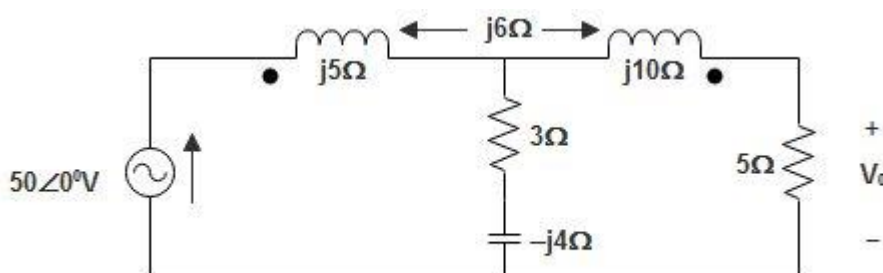


Fig.Q3b

3c) Find the inverse Laplace Transform of (8)

$$(i) F_1(s) = \frac{2s}{(s^2 + 4s + 13)} \quad (ii) F_2(s) = \frac{1}{(s+5)(s+2)} \quad (iii) F_3(s) = \frac{s+5}{s^2 + 4}$$

4a) In the network shown in Fig.Q4a, the switch K is closed at $t=0$. Find, (6)

$$(i) i_1(0^+), \quad (ii) i_2(0^+), \quad (iii) \frac{di_1(0^+)}{dt} \quad (iv) \frac{di_2(0^+)}{dt}$$

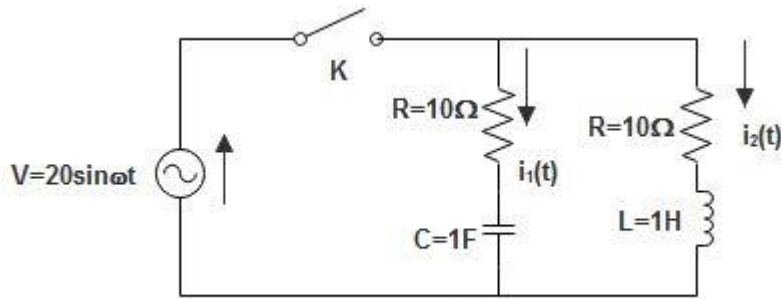


Fig.Q4a

4b) For the waveform shown in the Fig.Q4b, obtain its Laplace transform $V(s)$. (6)

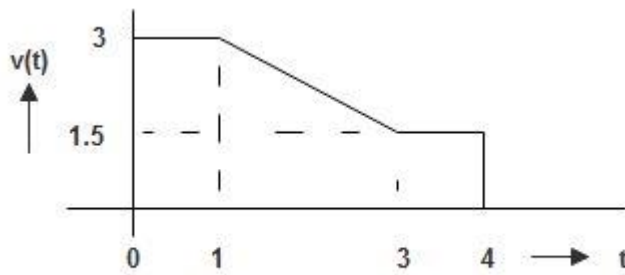


Fig.Q4b

4c) For the circuit shown in Fig.Q4c, the switch K was at position “a” to attain the steady state condition. At $t=0$, switch K is changed from position “a” to position “b”. Solve for $V(t)$. (8)


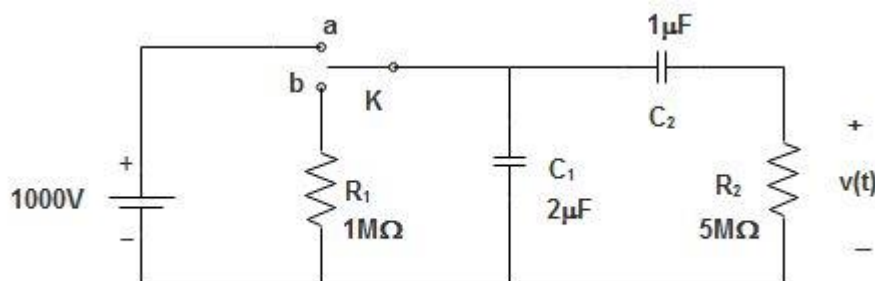


Fig.Q4c

5a) Convert h parameters in terms of Y parameters. (6)

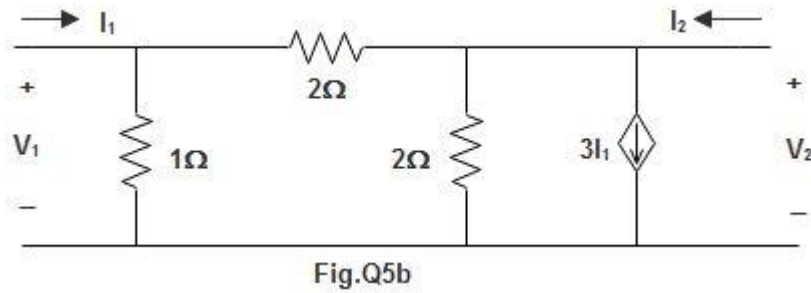5b) For the network shown in Fig.Q5b, find Z parameters. (6)



5c) For the network shown in Fig. Q5c, find (8)

(i) $G_{12}(s) = \frac{V_2(s)}{V_1(s)}$ (ii) $Z_{12}(s) = \frac{V_2(s)}{I_1(s)}$

