



III SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING)

END SEMESTER EXAMINATIONS NOV/DEC 2016

SUBJECT: DIGITAL ELECTRONIC CIRCUITS [ELE 2102]

REVISED CREDIT SYSTEM

Time: 3 Hours

Date: 28 November 2016

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ALL** questions.
- ❖ Missing data may be suitable assumed.

- 1A.** Design a logic circuit to implement $f(a,b,c,d) = \sum m(1,3,5,9,11,12,13,14) + d(2,6,8)$ using minimum number of NOR gates only **(03)**
- 1B.** Simplify $f(A,B,C,D,E) = \sum m(0,5,8,9,10,21,26,29,30) + d(1,7,12,13,14,15,16,17,20,22,25,27)$ using VEM technique **(05)**
- 1C.** Using 74LS194 wired as a right shift register implement Johnson counter. **(02)**
- 2A.** Design a 4 bit binary to gray code converter using 3 to 8 decoders. Residual gates may be used. **(04)**
- 2B.** Realize the Boolean expression
$$f(w,x,y,z) = \sum m(0,2,4,5,7,9,10,14)$$

Using a multiplexer tree structure. The first level should consist of two 4-to-1 line multiplexers with variables w and z on their select lines S1 and S0, respectively, and second level should consist of a single 2-to-1 line multiplexer with the variable y on its select line. **(04)**
- 2C.** State the importance of valid bit in 4 to 2 Priority encoder, with the help of relevant truth table **(02)**
- 3A.** Draw the state diagram of a synchronous 3 bit counter which works as a mod-8 binary counter when an input control signal G=0 and as a mod-8 gray code counter when G=1. Design and implement the counter using T flip flops. **(05)**
- 3B.** Using 74LS283 implement one digit BCD adder. **(03)**
- 3C.** Design a Divide by 10 counter using IC 7493 **(02)**
- 4A.** Simplify $f(A,B,C,D,E) = \sum m(1,8,21,28) + d(4,5,12,17,24,25,26,27,30)$ using Quine McCluskey (QM) method. **(04)**
- 4B.** Mention the different blocks with their significance in the Algorithmic State machine Chart. Draw the ASM chart for a 4 to 1 multiplexer. **(04)**
- 4C.** Draw the output waveforms (Q1, Q2) of the circuit given in Figure Q4C. **(02)**

- 5A. AB flip flop has a characteristic equation $Q^+ = BQ + A\bar{Q}$. Construct AB flip flop using T Flip flop (04)
- 5B. In a 10 bit input stream, count the no of occurrence of the sequence 010 as a Mealy machine. Implement using D flip flop and IC 74LS90. (06)

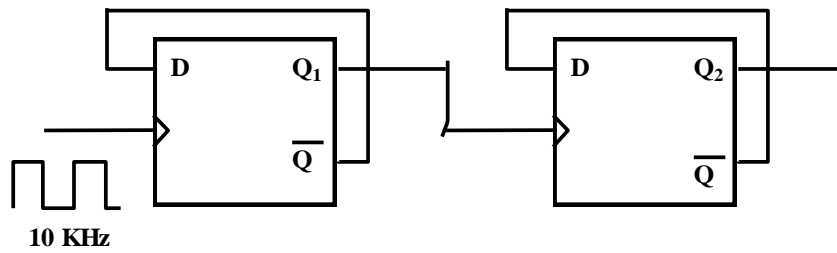


Figure Q 4C