



### III SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING)

MAKEUP EXAMINATIONS, DEC 2016 - JAN 2017

SUBJECT: ELECTRICAL CIRCUIT ANALYSIS [ELE 2101]

REVISED CREDIT SYSTEM

Time: 3 Hours

Date: 26 December 2016

Max. Marks: 50

#### Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A. In the network shown in Fig. 1A, determine the voltage across  $30 \Omega$  resistance using superposition theorem. (05)
- 1B. For the network shown in Fig. 1B, determine the current through  $2 \Omega$  resistance using Thevenin's theorem. (05)
- 2A. A two branch parallel circuit has  $R_C = 6 \Omega$  in series with  $X_C = 8 \Omega$  in one branch and  $X_L = 6.2 \Omega$  in series with a variable resistance in the other branch. The circuit is connected to a 100V a.c. voltage source. Draw the locus of total current and determine the values of (i) minimum current (ii) current at unity power factor. (05)
- 2B. Write the equation of the waveform shown in Fig. 2B in terms of step and ramp signals. Also, sketch its first derivative. (03)
- 2C. Evaluate the integrals:
- (i) 
$$\int_{-\infty}^{\infty} \delta(t-5)[u(t-2) - r(t-4)] dt$$
- (ii) 
$$\int_{-\infty}^{\infty} \cos t \left[ \delta(t-\pi) - \delta(t-\frac{\pi}{2}) + \delta^{(1)}(t-\frac{\pi}{4}) \right] dt$$
 (02)
- 3A. In the network of Fig. 3A, switch is closed at  $t = 0$ . Find  $i_1, i_2, \frac{di_1}{dt}$  and  $\frac{di_2}{dt}$  at  $t = 0^+$ . (05)
- 3B. Obtain the step and hence the impulse response of a series RLC circuit with  $R = 5 \Omega$ ,  $L = 1 \text{H}$  and  $C = 0.1667 \text{F}$  using time domain analysis. (05)
- 4A. In the network shown in Fig.4A, switch moves from position 1 to position 2 at  $t=0$ . Find the total current response. Use Laplace transforms method. (05)
- 4B. The transform of current response in a circuit is given by
- $$I(s) = \frac{5(s^2 + 4s + 3)}{(s^2 + 2s)(s^2 + 4)}$$
- Find  $I(t)$  using pole zero diagram. (05)
- 5A. Find the Laplace Transform of the waveform shown in Fig. 5A. (02)
- 5B. Find the h parameters of the network shown in Fig. 5B. (04)
- 5C. From fundamentals, deduce an inter-relationship to express z parameters in terms of transmission parameters. Hence calculate the values of z parameters, if ABCD parameters of a 2 port network is given as below. (04)
- $A=2, B=-1, C=3, D=-2.$

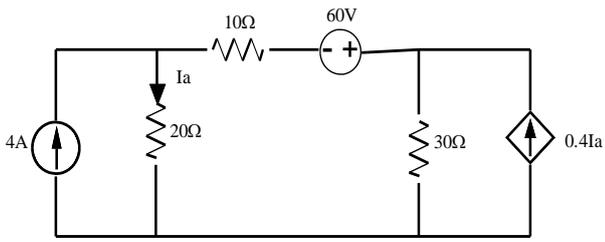


Fig. 1A

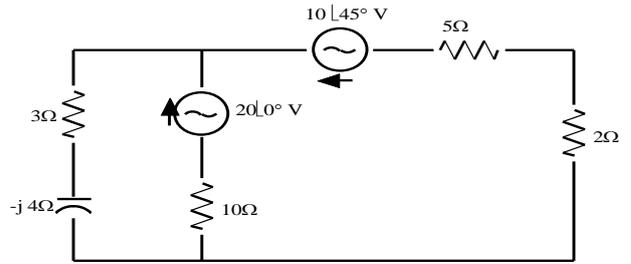


Fig. 1B

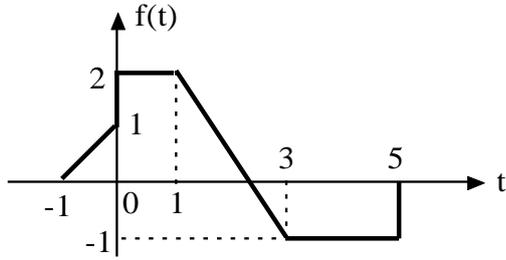


Fig. 2B

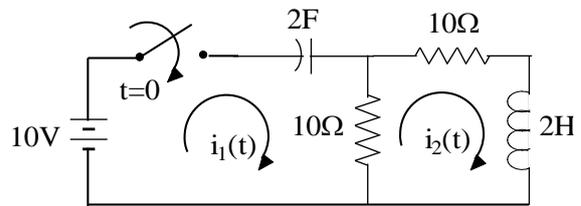


Fig. 3A

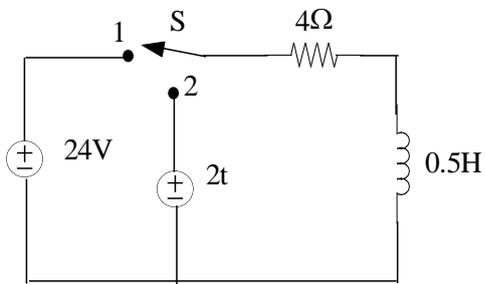


Fig. 4A

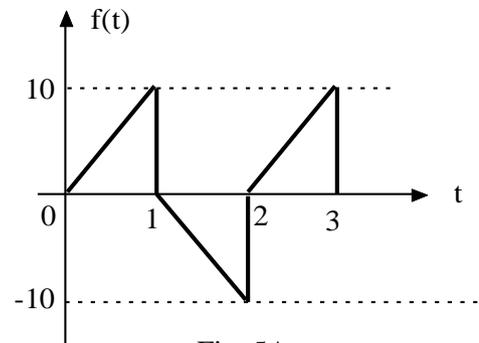


Fig. 5A

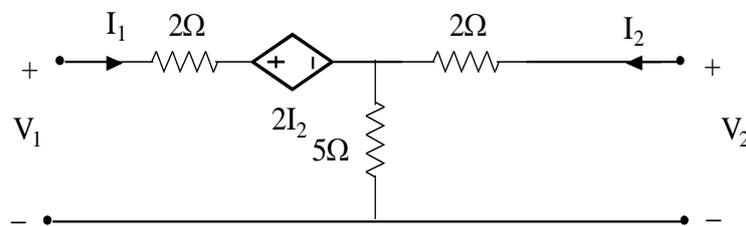


Fig. 5B