Reg. No.					



MANIPAL INSTITUTE OF TECHNOLOGY Manipal University THIRD SEMESTER B.TECH (E & C) DEGREE END SEMESTER EXAMINATION - NOV/DEC 2016 SUBJECT: NETWORK ANALYSIS (ECE - 2103)

TIME: 3 HOURS

MAX. MARKS: 50

- Instructions to candidatesAnswer ALL questions.
 - Missing data may be suitably assumed.
 - Do not use Laplace Transform unless specified.
- 1A. In the circuit shown in Fig. Q1A find the power delivered by 4V source and voltage across 2Ω resistor.
- 1B. For the circuit shown in Fig. Q1B, find voltage V_1 using superposition principle.
- 1C. Write KVL equations for the circuit shown in Fig. Q1C.

(5+3+2)

- 2A. In the circuit shown in Fig. Q2A, steady state is reached when switch S is open. At t=0 switch is closed. Find $V_c(0^-)$, $i_1(0^+)$, $i_2(0^+)$, $di_1/dt(0+)$, $di_2/dt(0+)$.
- 2B. In the network of the Fig. Q2B, the switch K is closed at t = 0 with the capacitor initially uncharged. For the numerical values given, find the general solution for i(t).
- 2C. Find the particular solution for the following homogeneous differential equation:

$$\frac{d^2i}{dt^2} + 7\frac{di}{dt} + 12i = 0$$
, subject to the initial conditions: $i(0^+) = 2$, $\frac{di(0^+)}{dt} = 1$.

(5+3+2)

- 3A. A symmetrical square wave is applied to a high-pass RC circuit having $R = 20 \text{ k}\Omega$ and $C = 0.05 \mu F$.
 - (i) If the frequency of the input signal is 1 kHz and the signal swings between ±5V, draw the output waveform and indicate the voltage levels.
 - (ii) What happens if the frequency of the signal is reduced to 100 Hz? Draw the output waveform.
- 3B. A limited ramp shown in the Fig. Q3B is applied to a low-pass RC circuit. Plot the output waveforms when (i) $T = \tau$ (ii) $T = 0.3 \tau$ (iii) $T = 6 \tau$.
- 3C. Prove that, if a square wave signal is applied to the low-pass RC circuit, the average value of the output signal is same as that of the input.

(5+3+2)

- 4A. In the circuit shown in Fig. Q4A, switch 1 is closed at t = 0 and then, at t = t' = 6ms, switch 2 is opened. Find the current i(t) in the intervals 0 < t < t' and t > t' using Laplace Transform.
- 4B. For the network shown in Fig. Q4B, find i_1 and i_2 , using Laplace Transform, when the switch is closed.
- 4C. Write the equation for v(t) and find V(S) for the waveform shown in Fig. Q4C.

(5+3+2)

- 5A. For the network shown in Fig. Q5A, determine the y parameters.
- 5B. Show that the overall transmission parameter matrix for cascaded two port network is the matrix product of the transmission matrices for each of the two port networks in cascade.
- 5C. The network N of Fig. Q5C is terminated at port 2 in impedance $Z_L = \frac{1}{Y_L}$. Show that the transfer impedance for the combination is

$$Z_{12} = \frac{z_{21}Z_L}{z_{22} + Z_L}$$

(5+3+2)



 $\mathbf{ECE} - \mathbf{2103}$

