

Reg. No.									
----------	--	--	--	--	--	--	--	--	--



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

A Constituent Institution of Manipal University

THIRD SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.)

END SEMESTER EXAMINATIONS, NOV/DEC 2016

SUBJECT: ANALOG ELECTRONIC CIRCUITS [ICE 2104]

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- | | | |
|------------|--|----------|
| 1A. | Plot the transfer characteristics of a E-MOSFET indicating its salient features | 3 |
| 1B. | With the constructional schematic of an n-type JFET explain its V-I characteristics. | 4 |
| 1C. | List the advantageous of FET over BJT | 3 |
| 2A. | For the circuit shown in Fig. Q2A compute the biasing parameters I_{DQ} , V_{DSQ} , V_{GSQ} , V_D , V_S | 3 |
| 2B. | Derive the biasing conditions for a common gate circuit. | 3 |
| 2C. | For the source follower circuit derive the expression for input impedance, output impedance, and gain considering the effect of signal and load resistance | 4 |
| 3A. | For the circuit shown in Fig. Q3A compute the input impedance, output impedance, and gain. | 4 |
| 3B. | Compute the input impedance, output impedance, and gain (with and without r_d) for the circuit given in Fig. Q3B | 4 |
| 3C. | Compare voltage series feedback and current series feedback amplifiers | 2 |
| 4A. | Plot the low frequency response for the circuit shown in Fig. Q4A | 4 |
| 4B. | Analyze the high frequency characteristics of the fixed bias circuit. | 3 |
| 4C. | Derive the expressions for input impedance, output impedance, and gain for a current shunt feedback amplifier | 3 |
| 5A. | Design a colpitts oscillator for the oscillatory frequency of 100kHz | 3 |
| 5B. | Describe the working of RC phase shift oscillator | 2 |
| 5C. | Discuss the working of Class B power amplifiers | 2 |
| 5D. | Comment on frequency response characteristics of cascode circuits | 3 |

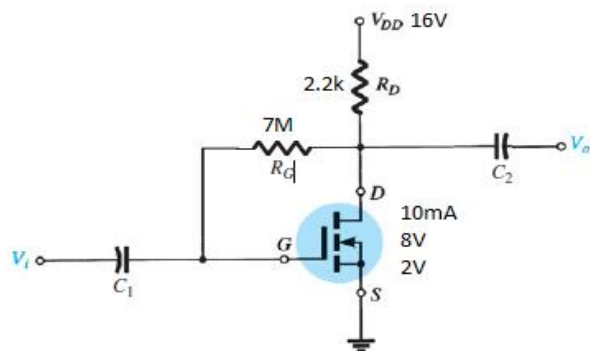


Fig. Q2A

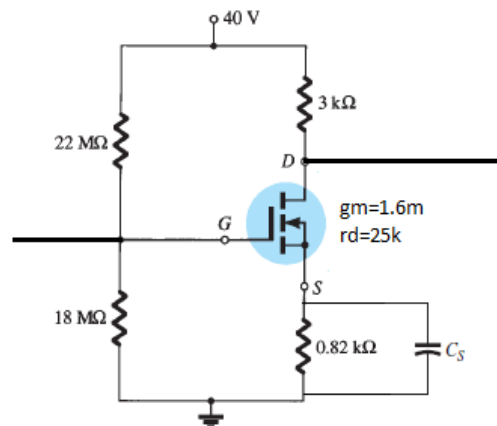


Fig. Q3A

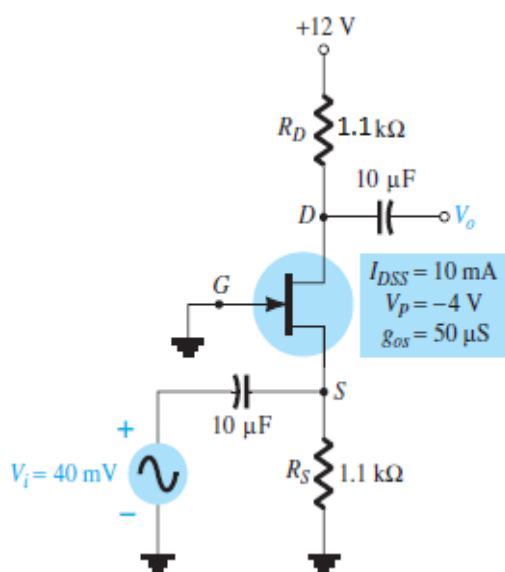


Fig. Q3B

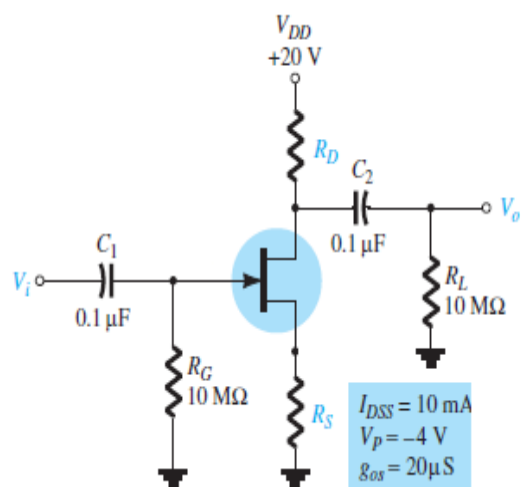


Fig. Q4A

***** END *****