

MANIPAL INSTITUTE OF TECHNOLOGY

A Constituent Institution of Manipal University

THIRD SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.)

END SEMESTER EXAMINATIONS, DEC 2016/JAN 2017

SUBJECT: DIGITAL ELECTRONIC CIRCUITS [ICE 2103]

Time: 3 Hours

MAX. MARKS: 50

2

3

2

3

5

3

Instructions to Candidates:

- ✤ Answer ALL the questions.
- Missing data may be suitably assumed.

1A.	State and prove De Morgan's theorem for 2 input variables.	
-----	--	--

- **1B.** i. $425_{10} =$ ______ in Gray code
 - ii. ABC.EF16 = ____10
 - iii. Find the odd one out:
 - a.0111 b.1000 c.1001 d.1010
- **1C.** Using the Quine McClusky method obtain the minimal expression for the Boolean **5** expression given by $F(A,B,C,D) = \sum m(0,1,3,5,9,10,11,13,14,15)$.
- 2A. Design a 1 bit magnitude comparator.
- **2B.** Design and implement a 3 bit binary to gray code converter.
- **2C.** Reduce using mapping the expression $f = \pi M$ (2, 8, 9, 10, 11, 12, 14). Implement the real minimal expression using NOR logic.
- **3A.** Define the terms setup time and hold time with respect to a flip flop.2**3B.** Realize the following function using a 4:1 multiplexer and additional gates3 $F(A,B,C,D) = \sum m(0,3,5,7,8,10,14)$ 3
- 3C. What are the differences between a latch and a flip flop? Convert a S-R flip-flop to J-K 5 flip-flop.
- 4A. With a neat logic diagram, explain the working of a SISO shift register.
 4B. Design a synchronous 3-bit Down Counter using J-K FFs.
 3
- **4C.** Design an overlapping sequence detector to detect the sequence 1010 using D FFs. **5**
- 5A. Draw the block diagram of an asynchronous sequential circuit and explain briefly. 2
- **5B.** Implement the full adder circuit using programmable logic array (PLA).

5C. Obtain state diagram and primitive flow table for a logic system with two inputs, x and y, and one output, z, that satisfy the following conditions. Initially x=y=0, z=0. When x = 1 and y=0, then z=1. When x = 0 and y=1, z =0. The output remains in the previous state (no change) when x=y. The logic system has edge triggered inputs (no clock).
