

Reg. No.									
----------	--	--	--	--	--	--	--	--	--



**MANIPAL INSTITUTE OF TECHNOLOGY**  
**MANIPAL**  
*A Constituent Institution of Manipal University*

**THIRD SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.)**  
**END SEMESTER EXAMINATIONS, NOV/DEC 2016**

**SUBJECT: ELECTRICAL & ELECTRONIC MEASUREMENTS [ICE 2102]**

Time: 3 Hours

MAX. MARKS: 50

**Instructions to Candidates:**

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A.** The voltages at opposite ends of  $470\Omega$ ,  $\pm 5\%$  resistor are measured as  $V_1 = 12V$  and  $V_2 = 5V$ . The measuring accuracies are  $\pm 0.5V$  for  $V_1$  and  $\pm 2\%$  for  $V_2$ . Calculate the level of current and specify its accuracy. Also calculate the power dissipated in the resistor when the same current is displayed by the ammeter with the 2% accuracy. Determine the accuracy of the result. **4**
- 1B.** Derive the expressions for Inductance and its internal resistance using Anderson's bridge. Also draw the phasor diagram. **4**
- 1C.** Define resolution and precision of an instrument **2**
- 2A.** The four arms of a bridge network are made up of as follows. **5**  
 AB and BC  $1000\Omega$  and  $1250\Omega$  respectively. CD unknown impedance. DA standard capacitance  $0.1\mu F$  connected in series with the  $10\Omega$  to give balance. The supply voltage is 15 V, 1000 Hz is given at the points B and D. Find components of unknown impedance.
- 2B.** What are the errors that are likely to occur in Single phase induction type energy meter? How they are compensated. **3**
- 2C.** Explain sampling and Hold in context with digital storage oscilloscope. **2**
- 3A.** Draw the block diagram of CRO. Brief the functions of blanking circuit and delay lines. **5**
- 3B.** With block and timing diagram, explain the working of Digital Frequency meter. **3**
- 3C.** With the signal generator frequency of a Q meter set to 1.25 MHz, the Q of a coil is measured as 98 when  $C = 147pF$ , Determine the coil inductance and resistance. **2**
- 4A.** With necessary figures explain recording and read out process of optical recording. **5**
- 4B.** With diagram describe the working of LCR meter **3**
- 4C.** Brief about Range changing in DVM. **2**

- 5A.** With block diagram elaborate the working of spectrum analyser. **5**
- 5B.** With the help of circuit diagram explain working of OPAMP based regulated power supply. **5**

\*\*\*\*\* END \*\*\*\*\*