| Reg. No. | | | | | | | | | | |
|----------|--|--|--|--|--|--|--|--|--|--|
|----------|--|--|--|--|--|--|--|--|--|--|



MANIPAL INSTITUTE OF TECHNOLOGY

THIRD SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.)

END SEMESTER EXAMINATIONS, DEC 2016/JAN 2017

SUBJECT: ELECTRICAL AND ELECTRONIC MEASUREMENTS [ICE-2102]

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ✤ Answer ALL the questions.
- ✤ Missing data may be suitably assumed.
- 1A. Derive expressions for unknown inductance and its internal resistance using 5 Maxwell-Inductance-capacitance bridge with phasor diagram.
- **1B.** Define the following terms as applied to the measuring instrument:
 3

 i) Linearity
 ii) Sensitivity

 iii) Hysteresis.
- **1C.** An unknown capacitor bushing forms an arm AB of a Schering Bridge and a standard capacitor of 500 pF capacitance and negligible loss forms an arm AD. Arm BC consists of a non-inductive resistance of 300Ω . When the bridge is balanced, arm CD has resistance of 72.6Ω in parallel with a capacitance of 0.148μ F.The supply frequency is 50Hz. Calculate the capacitance and dielectric loss angle of the capacitor.
- **2A.** With neat diagram describe the working of 3 phase Induction type energy meter. **5**
- 2B. Draw the block diagram of dual trace oscilloscope. What is the difference between 3 chop mode and alternate mode?
- 2C. If the horizontal frequency is 100Hz. Determine the unknown frequency for the Lissajous pattern shown in Fig.Q. 2C.
- 3A. Write the difference between LCD and LED. With neat figures explain the working 5 of LCD.
- 3B. Draw the block diagram and timing diagram of sampling oscilloscope and brief about 5 its working.
- **4A.** With the diagram describe the working of potentiometric type DVM.
- **4B.** What is Q factor of coil? The Q-meter circuit is in resonance when, E=200 mV, **3** $R=3\Omega$ and $X_L=X_C=95\Omega$. Calculate the coil Q and the voltmeter indication.
- **4C.** Draw the block diagram of Digital Storage Oscilloscope.

2

5

- **5A.** Explain recording of data using galvanometric recorder.
- **5B.** With neat figure explain the working of Swept Super heterodyne spectrum Analyzer.
- **5C.** Draw the block diagram of DC Regulated power supply



2