

Reg. No.									
----------	--	--	--	--	--	--	--	--	--



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

A Constituent Institution of Manipal University

THIRD SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.)

END SEMESTER EXAMINATIONS, DEC 2016/JAN 2017

SUBJECT: ELECTRICAL CIRCUIT ANALYSIS [ICE 2101]

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A.** For the circuit shown in Fig.Q1A, determine the mesh currents. **5**
- 1B.** Calculate the node voltages V_1 and V_2 for the circuit shown in Fig.Q1B **3**
- 1C.** For the circuit shown in Fig.Q1C calculate the current in $3k\Omega$ resistor **2**
- 2A.** Use Thevenin's theorem to find the current in 10Ω resistor in the circuit shown in Fig.Q2A. **5**
- 2B.** State and prove maximum power transfer theorem for the resistive load. **3**
- 2C.** For the network shown in Fig.Q2C, determine the current through 10Ω resistor using superposition theorem **2**
- 3A.** In the network of the Fig.Q3A the switch k is opened at $t=0$ after the network has attained steady state with the switch closed. Determine $V_K(0+)$, and $\frac{dV_k}{dt}(0+)$ **5**
- 3B.** A resistance of 10Ω , capacitor of $10\mu F$ and Inductance of $10mH$ is connected in series with ac source of $100V$. Determine the resonating frequency, quality factor and bandwidth of the circuit. Also determine maximum power dissipated in the circuit. **3**
- 3C.** In the circuit shown in Fig.Q3C, find current for $t \geq 0$. **2**
- 4A.** In the network of the Fig.Q4A the switch k is opened at $t=0$ after the network has attained steady state with the switch closed. Obtain expression for current $i(t)$ in complementary and particular solution form. **5**
- 4B.** Obtain expression for current in the circuit shown in Fig.Q4B. **3**
- 4C.** Plot $x(t) = r(t) - 2r(t-1) + 2r(t-3) + r(t-4)$ **2**
- 5A.** Use Laplace transform to find current $i(t)$ in the circuit shown in Fig.Q5A **4**
- 5B.** For the network shown in Fig.Q5B find Y parameters. **4**
- 5C.** Obtain the relationship between Y and Z parameters **2**

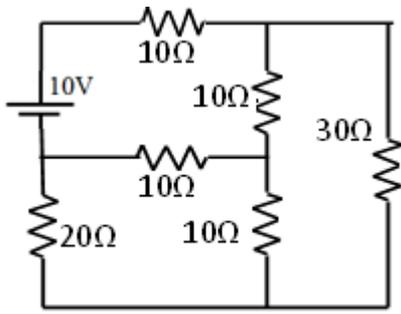


Fig. Q1A

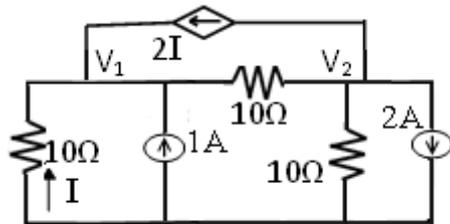


Fig. Q1B

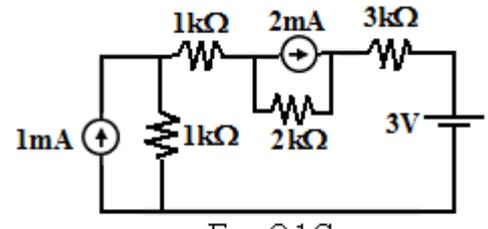


Fig. Q1C

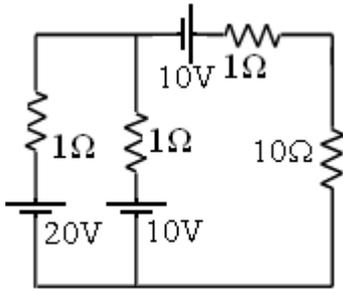


Fig. Q2A

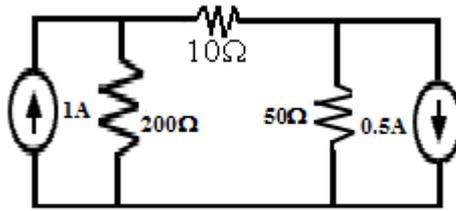


Fig. Q2C

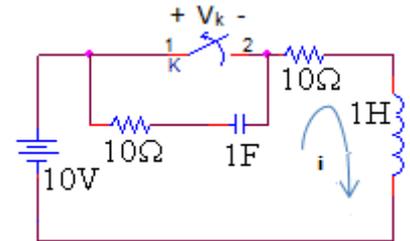


Fig. Q3A

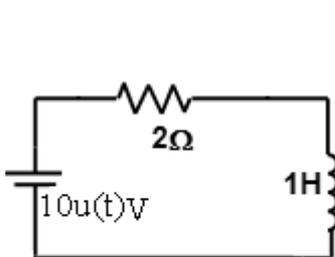


Fig. Q3C

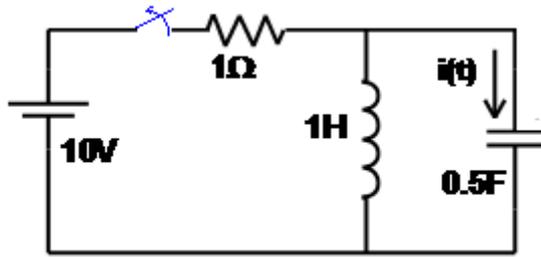


Fig. Q4A

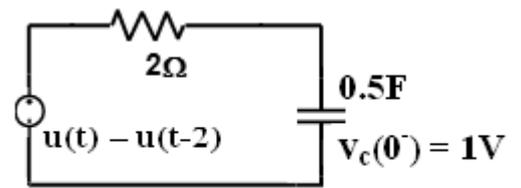


Fig. Q4B

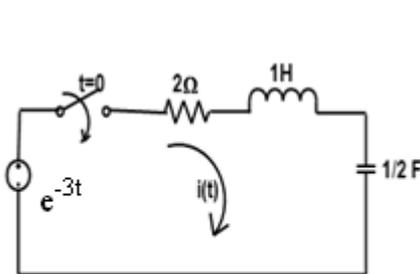


Fig. Q5A

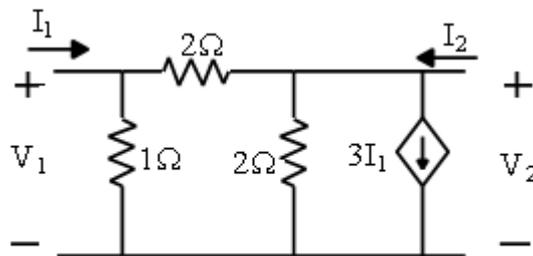


Fig. Q5B
