

|          |  |  |  |  |  |  |  |  |  |
|----------|--|--|--|--|--|--|--|--|--|
| Reg. No. |  |  |  |  |  |  |  |  |  |
|----------|--|--|--|--|--|--|--|--|--|



**MANIPAL INSTITUTE OF TECHNOLOGY**  
**MANIPAL**  
*A Constituent Institution of Manipal University*

**THIRD SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.)**  
**END SEMESTER EXAMINATIONS, NOV/DEC 2016**

**SUBJECT: ELECTRICAL CIRCUIT ANALYSIS [ICE 2101]**

Time: 3 Hours

MAX. MARKS: 50

**Instructions to Candidates:**

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- |            |  |          |
|------------|--|----------|
| <b>1A.</b> | For the circuit shown in Fig.Q1A, determine the mesh currents.   | <b>5</b> |
| <b>1B.</b> | determine the node voltages for the circuit shown in Fig.Q1B   | <b>3</b> |
| <b>1C.</b> | For the circuit shown in Fig.Q1B, find the current in $10\Omega$ resistor using superposition theorem.   | <b>2</b> |
| <b>2A.</b> | Obtain Norton's equivalent for the circuit shown in Fig.Q2A, with respect to $R_L$ .   | <b>5</b> |
| <b>2B.</b> | In the circuit shown in Fig.Q2B, find current $I$ and verify reciprocity theorem.  | <b>3</b> |
| <b>2C.</b> | Obtain Thevinin's equivalent for the circuit shown in Fig.Q2C, with respect to $R_L$   | <b>2</b> |
| <b>3A.</b> | In the network shown Fig. Q3A, the switch is closed at $t=0$ , a steady state having previously been attained. Determine $v_a(0^-)$ and $v_a(0^+)$ .   | <b>5</b> |
| <b>3B.</b> | A source of 100V with source impedance $5+j3$ and frequency 1000 Hz is connected to a load of capacitor $C$ in series with $10\Omega$ resistor. At what value of $C$ , power in the $10\Omega$ resistor is maximum? What is the power? | <b>3</b> |
| <b>3C.</b> | For the circuit shown in Fig.Q3C, find current in the circuit at 5 seconds.  | <b>2</b> |
| <b>4A.</b> | For the circuit shown in Fig. Q4A, obtain expression for current in complementary and particular solution form.  | <b>5</b> |
| <b>4B.</b> | Obtain expression for current in the circuit shown in Fig.Q4B.   | <b>3</b> |
| <b>4C.</b> | Express the waveform shown in Fig. Q4C using basic signals and write the Laplace transform.  | <b>2</b> |
| <b>5A.</b> | Use Laplace transform to find $i_1$ and $i_2$ in the circuit shown in Fig.Q5A  | <b>4</b> |
| <b>5B.</b> | For the network shown in Fig.Q5B find $Y$ parameters. Hence find $Z$ parameters  | <b>4</b> |
| <b>5C.</b> | Find $h$ parameters for the circuit shown in Fig.Q5C   | <b>2</b> |

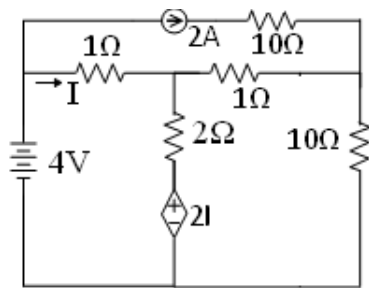


Fig. Q1A

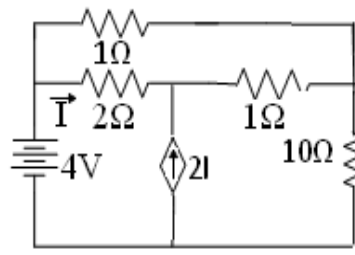


Fig. Q1B

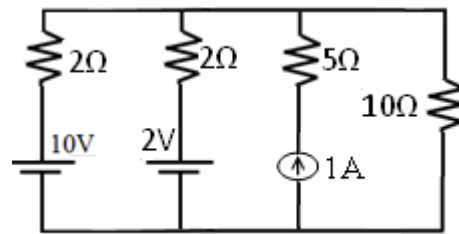


Fig. Q1C

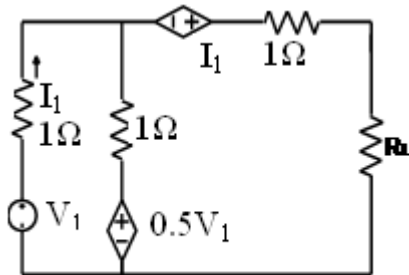


Fig. Q2A

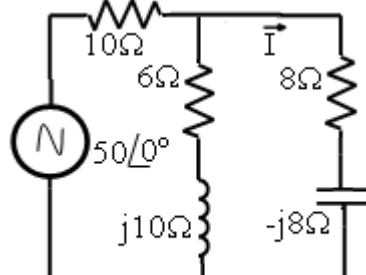


Fig. Q2B

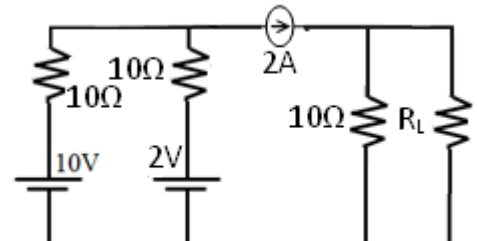


Fig. Q2C

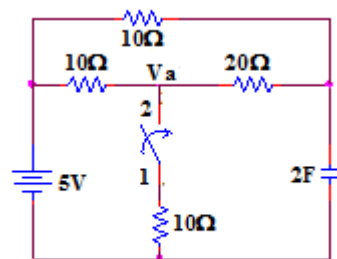


Fig. Q3A

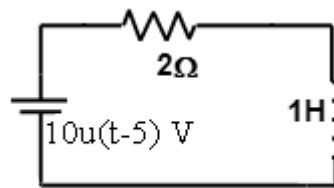


Fig. Q3C

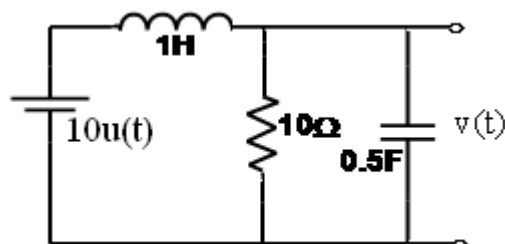


Fig. Q4A

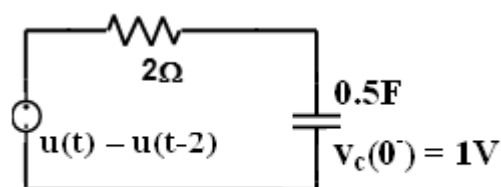


Fig. Q4B

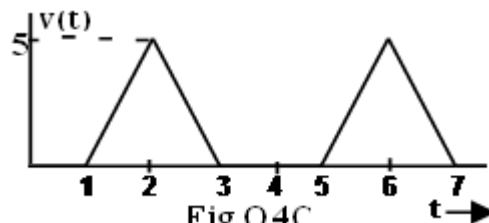


Fig. Q4C

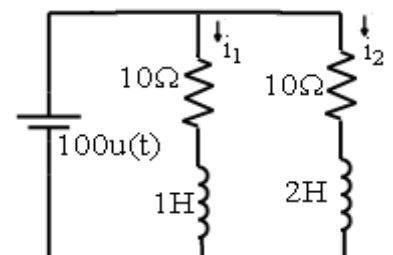


Fig. Q5A

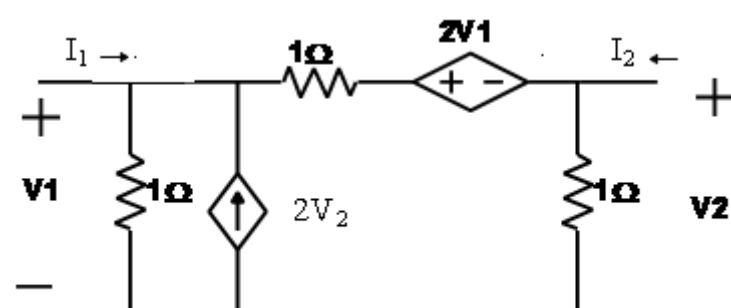


Fig. Q5B

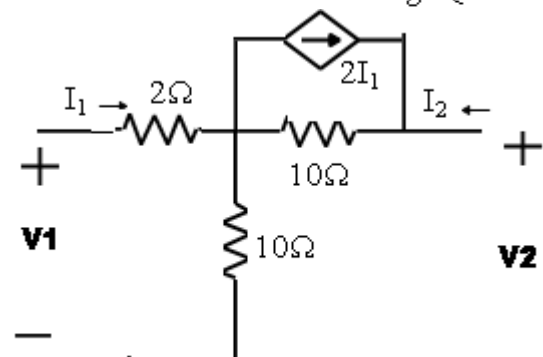


Fig. Q5C

\*\*\*\*\*