



III SEMESTER B.TECH. (MECHATRONICS ENGINEERING)

END SEMESTER EXAMINATIONS, DEC/JAN 2017

SUBJECT: Linear Integrated Circuits and Applications [MTE 2104]

REVISED CREDIT SYSTEM

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitable assumed.

1A. Design an analog divider circuit using 741IC. **4**

1B. Design a timer to switch ON heater for 5 seconds when push button is pressed. **3**

1C. Design an inverting adder circuit using opamp to get the output expression given below. **3**
 V_1, V_2, V_3 are inputs. Assume $R_f = 10k\Omega$.

$$V_o = -(0.5V_1 + V_2 + 10V_3)$$

2A. Design a Voltage Controlled Oscillator to produce a free running frequency of 500Hz. **4**
 $V_{cc} = 10V$, $R_T = 10k\Omega$, $C_T = 0.1\mu F$. Also estimate

- (i) Variation in free running frequency if Modulating voltage is varied between 7v and 9V. Hence find Voltage to frequency Conversion factor of VCO.
- (ii) Draw the Square wave output if the modulating input is a sine wave.

2B. Demonstrate the working of full wave rectifier using opamp 741. **4**

2C. Elucidate the working of PLL as frequency multiplier **2**

3A. Calculate the output voltage of the circuit shown in **fig.Q3(A)** if $V_1 = -V_2 = 300mV$ **4**

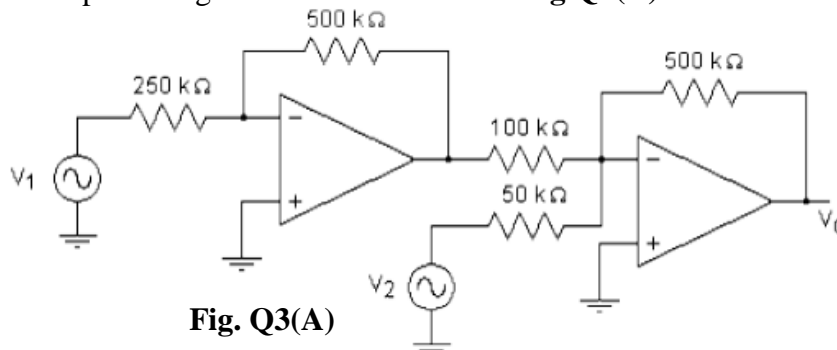


Fig. Q3(A)

3B. Elucidate the working of a Flash type ADC with the help of a 3 bit digital word. **4**

- 3C.** (i) Determine the output voltage of the adjustable regulator shown in Fig.Q3(C) 2
(ii) If R2 is varied from 1KΩ to 10KΩ compute the range of output voltage.
(Assume the quiescent current as 100μA)

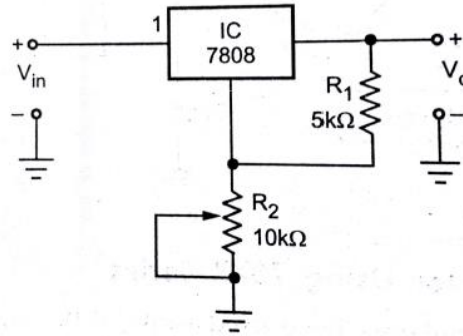


Fig.Q3(C)

- 4A.** Design a 2nd order Butterworth filter which passes all frequencies between 0 to 1kHz. 6
Sketch the response of the filter. Assume C = 0.1μF.
- 4B.** Design a PLL circuit using NE 565 to obtain the free running frequency of 5kHz, 4
Lock range of 3kHz and capture range of 150Hz. Assume supply voltages of $\pm 10V$ is available.
- 5A.** Design a Dual slope ADC which uses a 16bit counter and 4MHz clock. Maximum input 4
voltage is 10V and maximum integrator output voltage is -8V, when counter has cycled through 2ⁿ counts. Assume C=0.1μF. Also find the equivalent digital number if the input is V_a=4.129V.
- 5B.** Design a timer using IC 555 to generate a square wave of free running frequency, 3
10kHz with 65% duty cycle.
- 5C.** Design following 2nd order Differential Equation using Op-amps 3

$$5 \frac{dV_1}{dt} + 7V_1 - 3V_2 = 0$$