Dec Ne					
Keg. No.					



MANIPAL INSTITUTE OF TECHNOLOGY Manipal University



FIRST SEMESTER B.TECH (E & C) DEGREE END SEMESTER EXAMINATION NOV/DEC 2015 SUBJECT: BASIC ELECTRONICS (ECE - 1001)

TIME: 3 HOURS

MAX. MARKS: 50

Instructions to candidates

- Answer ALL questions.
- Missing data may be suitably assumed.
- 1A. A 100V-0-100V, 50 Hz is available at the secondary of the center tapped transformer in a fullwave rectifier with load 500 Ω . Calculate the output DC voltage, DC load current and Ripple factor for the cases (a) without capacitive filter and (b) with capacitive filter. Assume C= 1000 μ F, and ideal diodes. Draw the circuit of full-wave rectifier.
- 1B. For a Zener voltage regulator output voltage is 10V, load current is 50mA. $P_{z max}$ = 1000mW. Input voltage varies from 20V to 30V. Draw the circuit and find the maximum and minimum value of Zener current.
- 1C. A Silicon diode has a saturation current of 1pA at 20^oC. Find the (i) Diode bias voltage when diode current is 3mA.
 (ii) Diode bias current when the temperature is 100^oC, assuming the diode voltage to be constant.

(5+3+2)

- 2A. In a self-bias common emitter circuit using NPN transistor $R_c = 4.7 \text{ k}\Omega$, $R_E = 1 \text{k}\Omega$, $R_1 = 100 \text{ k}\Omega$, $R_2 = 18 \text{ k}\Omega$, $V_{CC} = 15 \text{V}$, $\beta = 80$ and $V_{BE} = 0.6 \text{V}$. Determine the Q point. Draw the circuit and indicate Q point on the output characteristics.
- 2B. Draw the input and output characteristics of PNP transistor in CB mode and indicate the salient features.
- 2C. A Germanium transistor with β = 100 has collector base leakage current of 5µA. If the transistor is connected in common emitter configuration, find the collector current for base currents of 0µA and 40µA respectively.

(5+3+2)

- 3A. A. An Op-amp has inputs $V_1 = 10$ mV and $V_2 = 8$ mV. If the differential gain is 60dB and CMRR is 80 dB calculate differential output voltage and common mode output voltage.
 - B. Draw a circuit using single op-amp for the following specification: (a) $A_v = 1$, (b) $A_v = -1$
- 3B. Perform the following operations.
 - i) Give BCD representation of the $(7305)_{10}$ number.
 - ii) Subtract $(-68)_{10}$ from $(125)_{10}$ using 2's complement.
- 3C. In a square wave generator using op-amp, find out the value of feedback resistor 'R', connected to the inverting terminal for the following specifications: Frequency of oscillation = 5 kHz, $V_{o(p-p)} = 10V$. C = 0.01µF and $\beta = 0.5$.

(5+3+2)

- 4A. i) Simplify the switching function using K-Map. F(ABC) = A'B'C'+A'B'C+A'BC+A'B C'+ABC
 - ii) Certain circuit has three inputs say, A, B and C. The output Z will be at logic 1 only if at least two or more inputs are at logic 1. Draw the truth table, give the output expression and implement using logic gates.
- 4B. Simplify the Boolean expression $Y=A\overline{B}\overline{C}+\overline{A}\overline{B}\overline{C}+\overline{B}\overline{C}+A\overline{C}$ and realize using logic gates.
- 4C. Draw the circuit of 4 bit SISO shift register using D flip-flops.

(5+3+2)

- 5A. If an audio signal of $10sin(2\pi 1000t)$ volts amplitude modulates a carrier of $40sin(2\pi 2000t)$ volts, determine:
 - i. Modulation index
 - ii. Sideband frequencies
 - iii. Bandwidth
 - iv. Total power delivered if $R_L = 1k\Omega$
 - v. Amplitude of each side band components
- 5B. List the different network topologies and ISO-OSI layers.
- 5C. State the sampling theorem. Consider the analog signal x (t) = $3 \cos 100\pi t + 10 \sin 300\pi t \cos 500\pi t$. What is the Nyquist rate of sampling for this signal?

(5+3+2)