

Reg. No.									
----------	--	--	--	--	--	--	--	--	--

# MANIPAL UNIVERSITY

THIRD SEMESTER B.S. (ENGG.) DEGREE EXAMINATION – DECEMBER 2015

SUBJECT: ELECTRONIC DEVICES AND CIRCUITS (EC 241)

(BRANCH: E&C/E&E)

(OLD SCHEME)

Monday, December 14, 2015

Time: 10:00 – 13:00 Hrs.

Max. Marks: 100

✍ Answer any FIVE full questions.

✍ Missing data, if any, may be suitably assumed.

1A. Explain Superposition theorem and maximum theorem with any example.

1B. Explain thevenin's equivalent circuit with any example.

(10+10 = 20 marks)

2A. Explain the self bias circuit and determine the expressions for the operating point. Perform the load line analysis for the same for variations in  $V_{CC}$ ,  $I_B$  and  $R_C$ .

2B. Compare half wave, full wave and bridge rectifier. With circuit diagrams input and output waveforms derive the equations for  $V_{dc}$ ,  $I_{dc}$ ,  $V_{rms}$ ,  $I_{rms}$ , ripple factor and efficiency.

(10+10 = 20 marks)

3A. Explain the input / output characteristics of a CE mode transistors. Explain what region the transistor has to operate to work as switch amplifier.

3B. An AC voltage of 230V, 50Hz is applied to transformer having turns ratio 10:1. The secondary of transformer is connected to half wave rectifier. The diode has cut-in voltage 0.6V and forward resistance  $10\Omega$ . Determine average and rms values of output current and voltage. What should be the PIV rating of the diode?

(10+10 = 20 marks)

4A. Explain the working of Transistor as a switch. Explain the region of operation of transistor as a switch.

4B. For a fixed bias circuit,  $V_{CC} = 12\text{ V}$  and  $R_C = 4\text{k}\Omega$ . The Ge transistor used is characterized by  $\beta = 50$ ,  $I_{CEO} = 0$  and  $V_{CEsat} = 0.2\text{ V}$ . Find the value of  $R_B$  that just results in saturation.

(10+10 = 20 marks)

5A. Explain the construction, operation and characteristics of Depletion MOSFET.

5B. Design a zener voltage regulator for the following specifications: Output voltage 5 V, input voltage  $(12 \pm 3)\text{ V}$ , load current 20 mA, zener maximum wattage 500 mW and minimum zener current 2 mA.

(10+10 = 20 marks)

- 6A. Determine  $v_o$  for the network shown in Fig Q6A for the input indicated. Explain the steps involved.
- 6B. Explain the construction and working of PN junction diode along with diode current equation and its VI characteristics under different bias conditions.

(10+10 = 20 marks)

- 7A. Explain the construction of JFET and its output and transfer characteristics.
- 7B. Briefly discuss the necessity of biasing. Explain the self bias circuit and derive the equations for  $I_B$ ,  $I_C$ , and  $V_{CE}$ .

(10+10 = 20 marks)

8. Write short notes on following:

- 8A. JFET small signal model
- 8B. Emitter follower
- 8C. CMRR
- 8D. Darlington Amplifier

(5 marks  $\times$  4 = 20 marks)

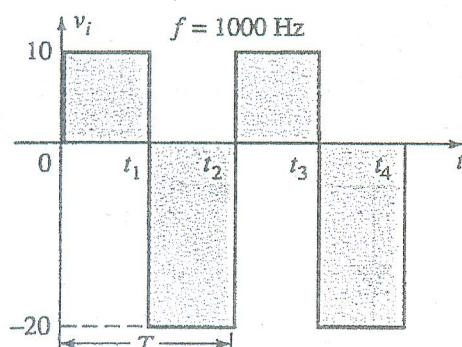


Fig 6A

