

Reg. No.									
----------	--	--	--	--	--	--	--	--	--



MANIPAL INSTITUTE OF TECHNOLOGY

(A Constituent Institute of Manipal University)

Manipal – 576 104



III SEMESTER B.Tech (BME) DEGREE END-SEM EXAMINATIONS, NOV / DEC 2015

SUBJECT: DIGITAL ELECTRONICS (BME 2103)

(REVISED CREDIT SYSTEM)

Thursday, December 03, 2015: 9.00a.m. - 12.00Noon

TIME: 3 HOURS

MAX. MARKS: 100

Instruction to Candidates:

Answer ALL the questions.

1. A. Design a decoder circuit to display octal numbers using the common-cathode type seven-segment display used in Biomedical equipment's. (08)
- B. (a) Define a digital Multiplexer. (08)
- (b) Realize the Boolean function $f = \sum(0, 3, 5, 7, 8, 10, 14)$ using:
 - (i) 8:1 Multiplexer, (ii) 4:1 Multiplexer, and additional gates.
- (c) Mention one application of a digital Multiplexer in Biomedical equipment's.
- C. Construct the state diagram for a Moore sequential circuit that will detect a non-overlapping sequence "1100" from an input sequence. (04)
2. A. Simplify the following Boolean function using "Quine-McCluskey" method: (08)

$$f(A, B, C, D) = \sum m (1, 4, 9, 10, 15) + \sum d (6, 7, 8, 11) \quad d \rightarrow \text{don't cares}$$
- B. (a) Design a Mod-13 Ripple counter using JK Flip-flops. (08)
- (b) A 4-bit Ripple counter uses Flip-flops with propagation delay of 20ns each. What will be the maximum possible time required for change of state?
- (c) The output frequency of a Mod-12 counter is 6kHz. What is its input frequency?
- C. Convert a JK Flip-flop to a SR Flip-flop. (04)

3. A. What is a Shift Register? Design a 3-bit Parallel-in Parallel-out (PIPO) / Parallel-in Serial-out (PISO) Shift Register using D Flip-flops. (08)
- B. Simplify the following 5-variable Boolean function using “Karnaugh-Map”. (08)

$$F(A, B, C, D, E) = \sum m(0, 1, 4, 5, 13, 15, 20, 21, 22, 23, 24, 26, 28, 30, 31)$$
- C. What is a digital comparator? Design a 1-bit digital comparator. (04)
4. A. Illustrate the design of a Mealy sequential circuit, by designing a sequence detector which will detect an overlapping sequence 1010 from an input sequence. (08)
- B. Design a circuit to subtract 1001 from 1101, using the following methods: (08)
 (i) 1’s complement (ii) 2’s complement.
- C. (a) Fill in the blanks: (04)
 (i) $(35)_8 = (_)_{10}$ (ii) $(AC5)_{16} = (_)_{10}$
 (b) Express the following decimal numbers in “8421” and “2421” codes:
 (i) 807 (ii) 429.5
5. A. Design a synchronous counter with the following binary sequence: 0, 1, 3, 4, 5, 6 and repeat. Use JK Flip-flops. (08)
- B. What is a parity bit? Mention its significance. Design a 3-bit Even-parity Generator / Checker. (08)
- C. (a) Perform the following decimal additions in the 8421 code. (04)
 (i) $88.7 + 265.8$ (ii) $204.6 + 185.56$
 (b) Convert the following numbers to Gray code.
 (i) $(45)_{10}$ (ii) $(234)_8$