



Manipal Institute of Technology, Manipal

(A Constituent Institute of Manipal University)



III SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING)

MAKE UP EXAMINATIONS, DEC 2015 / JAN 2016

SUBJECT: ANALOG ELECTRONIC CIRCUITS [ELE 2105]

REVISED CREDIT SYSTEM

Time: 3 Hours

09 January 2016

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitable assumed.

- 1A. In the figure as shown in fig.Q1A, if V_i has a peak of 30 V, then draw the transfer characteristics. 4
- 1B. In the figure as shown in fig.Q1B, identify the diode ($V_D = 0.6$ V) based circuit. 3
- 1C. Design a Zener voltage regulator for the following specifications: output voltage = 5V, input voltage = 12 ± 3 V, load current = 20 mA, zener power rating = 500 mW. 3
- 2A. Discuss the transconductance of MOSFET. Hence derive the equations governing the relationship between transconductance, current, aspect ratio and gate overdrive voltage of the MOSFET. 3
- 2B. Assuming $\lambda \neq 0$, draw the small signal model of the circuit shown in Fig.Q2B. 3
- 2C. Design the circuit shown in Fig. Q2C for a voltage gain of 5V/V and a power budget of 6mW. Assume that the voltage divider branch consumes 5% of total power and voltage drop across R_s is equal to the overdrive voltage of the transistor. Also assume $R_D = 200\Omega$, $V_{TH} = 0.4$ V, $\mu_n C_{ox} = 200 \mu A/V^2$, $\lambda = 0$. 4
- 3A. For the NMOS common source amplifier shown in Fig. Q3A, the transistor parameters are: $V_{th} = 0.8$ V, $\mu_n C_{ox} (W/2L) = 1$ mA/V², $V_{DD} = 5$ V, $R_s = 1$ k Ω , $R_D = 4$ k Ω , $R_1 = 225$ k Ω , $R_2 = 175$ k Ω . Calculate the quiescent values I_{DQ} and V_{DSQ} . Draw the small signal model and hence determine the small signal gain for R_L is infinite. Neglect Channel length modulation. 5
- 3B. Determine the small signal voltage gain of the multistage cascade circuit shown in Fig. Q3B. Draw the small signal model and neglect channel length modulation. 5
- 4A. Bandwidth of an amplifier lies between 150 Hz and 100 kHz. Find frequency range over which voltage gain is less than 2 dB from mid-band value. 3
- 4B. Design an NMOS current mirror with $V_{DD} = 6$ V, $V_{SS} = 0$ V, $I_{ref} = 100 \mu A$. For the matched transistors $L = 10 \mu m$, $W = 100 \mu m$, $V_{TH} = 1$ V, $\mu_n C_{ox} = 20 \mu A/V^2$. 3

4C. Derive expressions for Differential gain, Common mode gain and CMRR of a MOS Differential Pair. **4**

5A. State and prove Millers theorem for a MOSFET based amplifier circuit and derive suitable expressions for Miller Capacitance. **5**

5B. Derive the expression for conversion efficiency of Class A series fed and transformer coupled Power amplifiers. **5**

 


Fig Q1A

 


Fig Q1B

 


Fig.Q2B

 


Fig. Q2C

 


Fig. Q3A

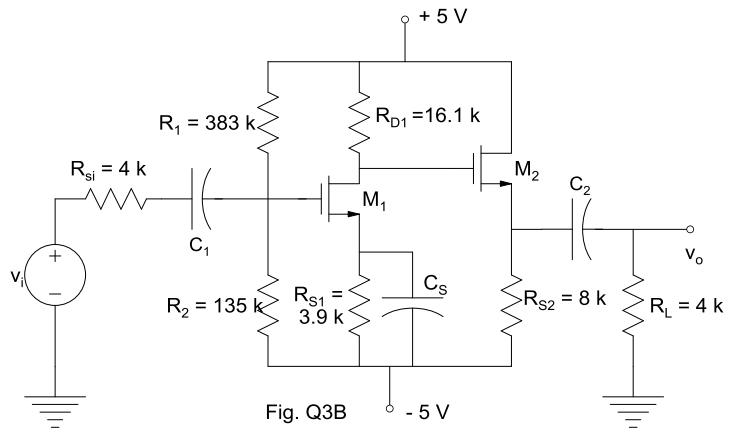


Fig. Q3B