



III SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING)

END SEMESTER EXAMINATIONS, NOV/DEC 2015

SUBJECT: ANALOG ELECTRONIC CIRCUITS [ELE 209]

REVISED CREDIT SYSTEM

Time: 3 Hours

08 DECEMBER 2015

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ANY FIVE** Full questions.
- ❖ Missing data may be suitably assumed.

- 1A. Determine V_o , I , I_1 and I_2 for the circuit shown in Fig.Q1A. Assume Silicon diodes. 02
- 1B. Plot v_o v/s time for the circuit shown in Fig. Q1B. Assume ideal diodes. 05
- 1C. Parameters of a 6.3 V Zener diode for voltage regulator are: $V_Z = 6.3$ V at $I_{ZT} = 40$ mA and $R_Z = 2 \Omega$. V_s varied between 12 V to 18 V. Minimum load current is 0mA. Minimum Zener diode current is 1 mA. Power dissipation of Zener diode must not exceed 750 mW at 25°C. Determine a) i_{zmax} b) value of R_s that limits the Zener current i_{zmax} to value determined in part a) and c) power rating of R_s . 03
- 2A. Design a circuit to obtain the output voltage waveform shown in Fig. Q2A, for the given input waveform and justify. Assume silicon diodes. 03
- 2B. Determine R_i , R_i' , A_v , A_{vS} , A_i and A_{iS} for the circuit shown in Fig.Q2B. Assume A_v to be very high. Draw the h parameter model. Given $h_{ie} = 1.1$ k, $h_{fe} = 50$. 07
- 3A. In the amplifier shown in Fig. Q3A, the MOSFET has $V_{TH} = 0.7$ V, $\mu_n C_{ox} = 500 \mu A/V^2$, $\lambda = 0$, drain current $I_D = 1$ mA. Determine
 - a) W/L and gm of the MOSFET 03
 - b) Maximum small signal gain from V_{sig} to V_o
- 3B. With a neat circuit diagram, discuss the MOSFET based RC coupled amplifier. Hence discuss the role played by each discrete circuit element in defining the gain and frequency response. 03
- 3C. In the cascaded amplifier shown in Fig. Q3C, the MOSFETs have, drain currents $I_{D1} = 2$ mA, $I_{D2} = 1$ mA, $V_{TH} = 0.7$ V, $\mu_n C_{ox} = 500 \mu A/V^2$, $\lambda = 0$
 - a) Draw the small signal model
 - b) Find the small signal gain from V_{sig} to V_L
 - c) Determine R_{in} and R_{out} of the amplifier. 04
- 4A. For the amplifier shown in fig. Q4A, if it is required to have cut-off frequencies as 1 kHz and 40kHz, then determine the values of capacitances C_1 , C_2 and C_L . Assume $\lambda = 0.01$ per volt. 03

- 4B.** In the circuit shown in Fig Q4B, if $(\mu n\text{Cox})_1 = (\mu n\text{Cox})_2 = 200 \mu\text{A/V}^2$, $I_{D1} = 100 \mu\text{A}$, $V_{TH1} = V_{TH2} = 0.4 \text{ V}$, $\lambda = 0$, $(W/L)_1 = 5$, then determine
- Resistance R_1 03
 - V_{DS2} if $(W/L)_2 = 0.1 \times (W/L)_1$ 03
- 4C.** With a neat circuit and diagram and necessary waveforms, evaluate maximum efficiency of a series fed class A power amplifier. Suggest suitable modifications to improve the efficiency. 04
- 5A.** Design a voltage divider bias circuit for following specifications: $\beta = 50$, $V_{BE} = 0.7 \text{ V}$, $V_{CC} = 22.5 \text{ V}$, $R_C = 5.6 \text{ k}\Omega$, Q point at $V_{CE} = 12 \text{ V}$, $I_C = 1.5 \text{ mA}$, $S \leq 3$. 03
- 5B.** For a class B Power amplifier providing a 20 V peak signal to a 8Ω load (speaker) and a power supply of $V_{CC} = |V_{EE}| = 30 \text{ V}$, determine the input power, output power and efficiency of the circuit. 03
- 5C.** Write a note on Basic Series and Shunt Voltage Regulators with neat circuit diagrams. 04
- 6A.** For a full bridge rectifier supplying a load of 200Ω from an ac source of 30 V at 50 Hz , calculate average load voltage and percentage ripple if a capacitor of $1000 \mu\text{F}$ is used as filter. 04
- 6B.** With relevant waveforms define storage time, transition time and reverse recovery time of PN junction diode. 03
- 6C.** Classify the power amplifier based on the conduction angle. 03

 


Fig.Q1A

 


Fig. Q1B

 


Fig. Q2A

 


Fig.Q2B

 


Fig. Q3A

 


Fig. Q3C

 


Fig. Q4A

 


Fig. Q4B