

III SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING)
END SEMESTER EXAMINATIONS, NOV/DEC 2015

SUBJECT: DIGITAL ELECTRONIC CIRCUITS [ELE 203]

REVISED CREDIT SYSTEM

Time: 3 Hours

01 Decemeber 2015

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer any **FIVE FULL** questions.
- ❖ Missing data may be suitably assumed.

- 1A.** Given the network of Figure 1A , determine the functions f_2 and f_3 if $f_1 = \bar{A}$ and the overall function is to be $F(A,B,C,D) = \prod M(1,2,5,6,12,15) + d(3,4,8,10,13,14)$. Also Find G.

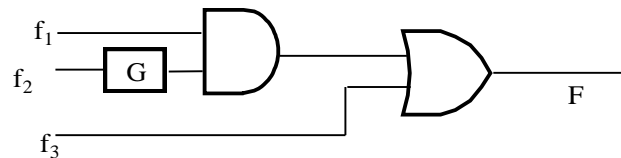


Figure 1A

(04)

- 1B.** Simplify the following Expression using VEM.

$$F(A,B,C,D,E) = \prod M(0,1,7,8,9,12,14,18,19,21,27) + d(2,3,4,5,6,10,13,16,17,23,24,25,30,31)$$

(04)

- 1C.** A mux based circuit is given in the Figure 1C. Find the expression of Z_0 , Z_1 and Z_2 .

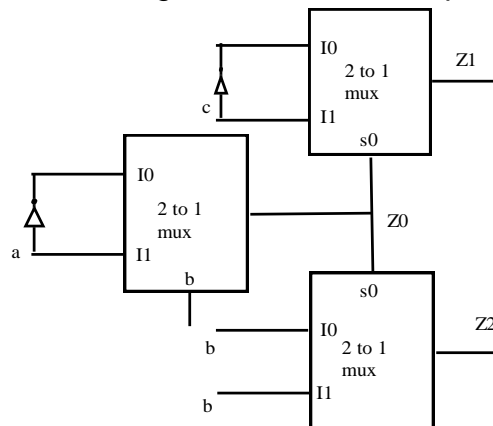


Figure 1C

(02)

- 2A.** Implement $f = a\bar{b} + \bar{a}c + bc$ using

1. Single 4:1 mux
2. 2 to 4 decoders

(04)

- 2B.** Design 2 digit BCD adder using 74LS283

(04)

2C. Draw the state diagram for the digital circuit shown in Figure 2C.

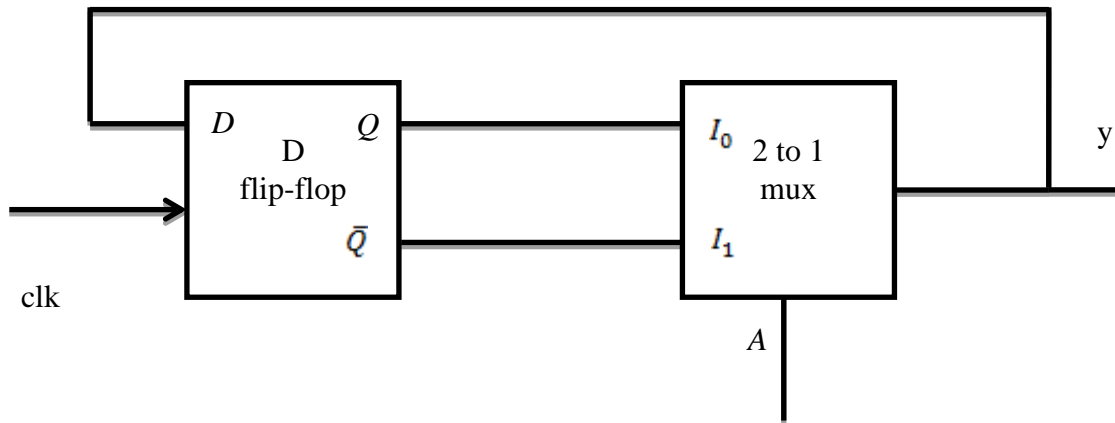


Figure 2C

(02)

3A. Design a presettable counter which counts from 3 to 11 using D flip flops (03)

3B. Draw an ASM chart to detect the sequences 011 and 101 in a continuous data stream, as a Moore machine. (04)

3C. Design a 4 to 2 Priority encoder and mention its advantages. (03)

4A. Using a 4 bit universal shift register (74LS194) design a sequence generator which cycles through the following sequence. 0-8-12-6-13-11-7-3-1-0-.....

4B. Design a two digit octal counter in the range 00-77 using 74LS90. (03)

4C. An AB FF is constructed from an SR FF as shown in Figure 4C

a) Obtain expression for S and R in terms of A and B.

b) Write an expression for the next state Q^+ in terms of A, B and present state y.

c) Construct the excitation requirements table for A and B.

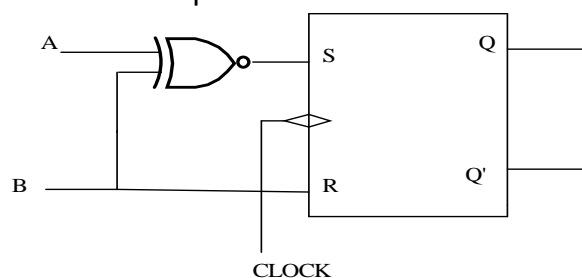


Figure 4C

(03)

5A. A sequence Detector is to detect the sequence 1010 as a Mealy machine in a stream of 16 bits. Draw the state diagram and implement the circuit using D flip flops and 7493 IC. (07)

5B. Implement the equation $f = \overline{A} + A\overline{B}$ with CMOS logic. Use minimum number of MOS transistors. (03)

6A Express the following Boolean function using Shannon's expansion in terms of variable B. Also write it's dual.

a. $F = A'B + ABC' + A'B'C$

b. $F = AB'C + BC + A'B'C'$

(04)

6B Convert the following binary numbers expressed in Hex to its equivalent gray code and express the results in Hex.

(i) 8EFD

(ii) 5AB7

(02)

6C Give one example each for the following codes

(i) Weighted decimal codes

(ii) Non-weighted decimal codes

(iii) Unit distance codes

(iv) Reflected codes

(04)