

**THIRD SEMESTER B.TECH (E & C) DEGREE END SEMESTER EXAMINATION
NOV/DEC 2015**

SUBJECT: ANALOG ELECTRONIC CIRCUITS (ECE - 2101)

TIME: 3 HOURS

MAX. MARKS: 50

Instructions to candidates

- Answer **ALL** questions.
- Missing data may be suitably assumed.

- 1A. Consider the circuit shown in Fig. Q1(A), where v_1 represents the signal generated by a microphone, $I_S = 3 \times 10^{-16} \text{ A}$, $\beta = 100$, and Q_1 operates in the active mode. (i) If $v_1 = 0$, determine the small-signal parameters of Q_1 . (ii) If the microphone generates a 1mV signal, how much change is observed in the collector and base currents?
- 1B. Due to a manufacturing error, the base width of a bipolar transistor has increased by a factor of two.
- How does the collector current change?
 - If this change has to be compensated by emitter area, what should be the emitter area with respect to original emitter area?
 - If the transistor is a pnp transistor; is the current value same as that of npn transistor?
- 1C. A degenerated CE stage is biased at a collector current of 1 mA. If the circuit provides a voltage gain of 20 with no emitter degeneration and 10 with degeneration, calculate the value of R_C and R_E .

 


Fig. Q1(A)

 


Fig. Q2(A)

 


Fig. Q2(C)

 


Fig. Q3(A)





(5+3+2)

- 2A. The circuit of Fig. Q2(A) must be designed for a voltage drop of 200mV across R_S . Assume $V_{TH} = 0.4 \text{ V}$, $\lambda = 0$ and $\mu_n C_{OX} = 200 \mu\text{A/V}^2$.
- Calculate the minimum allowable value of W/L if M_1 must remain in saturation.
 - Assuming $V_G = 0.8 \text{ V}$, design the values of R_1 and R_2 to get the input impedance of at least 30kΩ.
- 2B. The drain current of an NMOS device is 1 mA with $V_{GS} - V_{TH} = 0.6 \text{ V}$ and 1.6mA with $V_{GS} - V_{TH} = 0.8 \text{ V}$. If the device operates in the triode region, calculate V_{DS} and W/L . Assume $\mu_n C_{OX} = 200 \mu\text{A/V}^2$.
- 2C. Sketch the drain current of M_1 in Fig. Q2(C) versus V_1 , as V_1 varies from zero to V_{DD} . Assume $\lambda = 0$.

(5+3+2)



- 3A. Design the amplifier shown in Fig. Q3(A) to provide a voltage gain of 4 with a power budget of 2mW while the voltage drop across R_S is 200mV. The overdrive voltage of the transistor must not exceed 300mV and current through R_1 and R_2 is 5% of current drawn from supply. Assume $V_{TH}=0.4V$, and $\mu_n C_{OX}=200\mu A/V^2$.
- 3B. In the amplifier shown in Fig. Q3(B), collector current of Q_1 is 1mA, $R_1=1k\Omega$ & $C_L=1pF$. Calculate the frequency at which gain falls by 10%. Neglect the junction capacitors and channel length modulation.
- 3C. Figure Q3(C) is a two-stage amplifier consisting of a CS circuit and a source follower. Assuming $\lambda \neq 0$ for M_1 and M_2 but $\lambda = 0$ for M_3 , and neglecting all capacitances except C_{GS3} , compute the output impedance of the amplifier.

(5+3+2)

    **Fig. Q3(B)****Fig. Q3(C)****Fig. Q4(A)****Fig. Q4(B)**

- 4A. Calculate the closed loop gain, input and output resistance for the circuit in Fig. Q4(A).
- 4B. Identify the sense and return mechanisms, and the polarity of the feedback in the circuit of Fig. Q4(B). Redraw the circuit with no feedback.
- 4C. Calculate the loop gain of the circuit in Fig. Q4(C). Assume the Opamp exhibits an open-loop gain of A_1 , but is otherwise ideal. Also, $\lambda = 0$ for the MOSFET.

(5+3+2)

 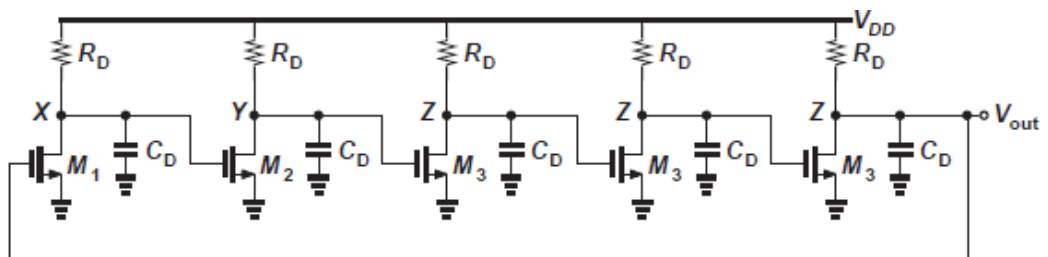**Fig. Q4(C)****Fig. Q5(A)**

- 5A. Derive the oscillation frequency and startup condition for the ring oscillator of Fig. Q5(A).
- 5B. For a BJT $i_b=2\mu A \cos \omega t$ and $i_c=100i_b + 3i_b^2$. Calculate the DC content in the collector current, amplitude of fundamental and 2nd harmonics. Also calculate the 2nd harmonic distortion in the collector current.
- 5C. Show that the transformer coupling has the best conversion efficiency of 50%.

(5+3+2)