

THIRD SEMESTER B.TECH (INSTRUMENTATION & CONTROL ENGINEERING)
END SEMESTER EXAMINATIONS, NOV/DEC 2015

SUBJECT: ANALOG ELECTRONICS CIRCUIT [ICE-2104]

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A.** Sketch and explain the transfer characteristics of JFET. **3**
- 1B.** Explain the construction and working of n – channel enhancement type MOSFET. **3**
 Sketch the drain charectoristic.
- 1C.** Compute V_{GSQ} , I_{DQ} , V_{DS} , V_D for the circuit shown in Fig. 1. **4**

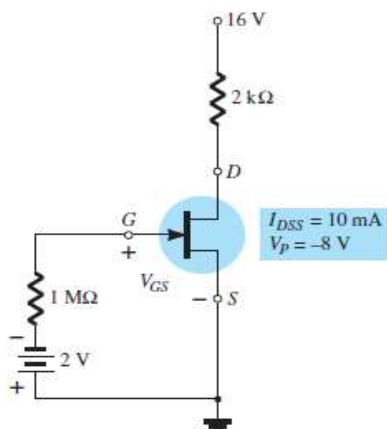


Fig. 1

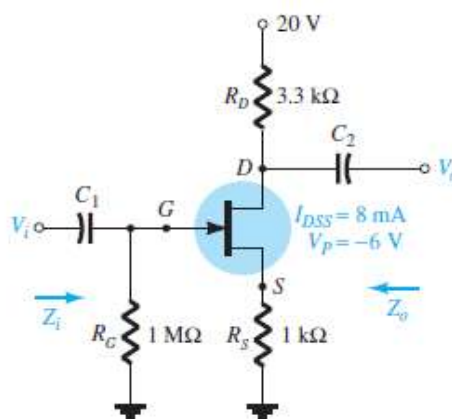


Fig. 2

- 2A.** Construct an E-MOSFET voltage divider biasing network and derive the conditions for V_G , V_{GS} and V_{DS} . **3**
- 2B.** Determine the Input impedance, Output impedance and gain for the circuit shown in Fig. 2, and also represent the model of the same. Given: $V_{SGQ} = -2.6V$, $I_{DQ} = 2.6mA$ and $Y_{os} = 20\mu S$. **3**
- 2C.** Derive the equation for input impedance, output impedance, and gain for a source - **4**

follower considering the effect of load and signal resistance.

- 3A.** Determine the low frequency response characteristics for the circuit shown in Fig. 3, **3**
having $R_{sig} = 100 \Omega$ and $R_L = 2.2k\Omega$.
- 3B.** Plot the high frequency response characteristics of the circuit shown in Fig. 4. **4**

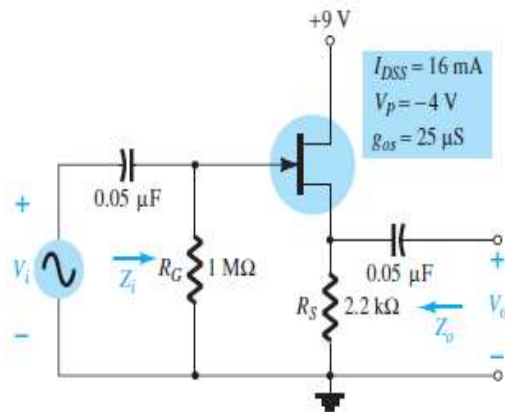


Fig. 3

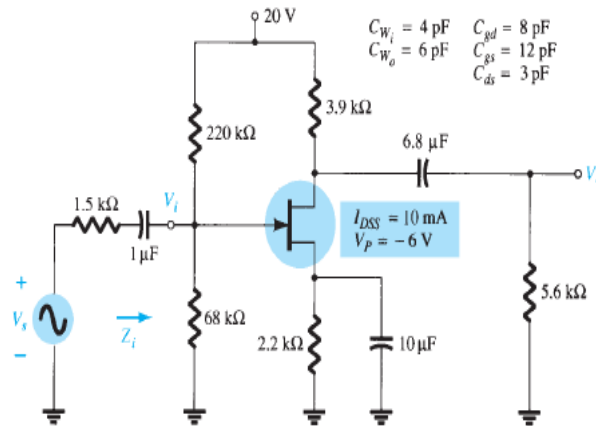


Fig. 4

- 3C.** Draw the diagram of cascade amplifier. Sketch the frequency response and analyze. **3**
- 4A.** With a circuit, analyze the characteristics of a current series feedback amplifier. **4**
- 4B.** Discuss the effect of feedback on gain, input impedance and output impedance of voltage series and voltage shunt topologies. **3**
- 4C.** Design the RC elements of a Wien-bridge oscillator for the operating frequency of $f_o = 10\text{KHz}$. **3**
- 5A.** In a Hartley oscillator, uses 2mH and 20μH inductors and a variable capacitor. Calculate the range over which the capacitor need to be varied for oscillating frequency from 950kHz to 2050kHz **3**
- 5B.** Design and explain the working of RC phase shift oscillator. **4**
- 5C.** Discuss the effect of ac load line on Class A and Class B type of power amplifiers. **3**
