

Reg. No.



# Manipal Institute of Technology, Manipal

(A Constituent Institute of Manipal University)



**THIRD SEMESTER B.TECH (INSTRUMENTATION & CONTROL ENGG.)**

**END SEMESTER EXAMINATIONS, NOV/DEC 2015**

**SUBJECT: DIGITAL ELECTRONICS CIRCUITS [ICE 2103]**


Time: 3 Hours

MAX. MARKS: 50

## Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A.** Prove that  $AB'C + A'BC + ABC = A(B + C)$  using Boolean algebra. **(2M)**
- 1B.** Implement the following expression without further reducing, using only NAND gates. **(3M)**
- $$F = (A + C)(ABC + ACD).$$
- 1C.** Using the tabular method, obtain the minimal expression for **(5M)**
- $$f = \sum m(0, 1, 2, 8, 9, 15, 17, 21, 24, 25, 27, 31).$$
- 2A.** Design a logic circuit with 4 inputs A, B, C, D that will produce output '1' only whenever two adjacent input variables are 1's. A & D are also to be treated as adjacent. Implement it using NAND gates. **(4M)**
- 2B.** Design an odd parity bit generator for a 4-bit input. **(3M)**
- 2C.** Implement the following Boolean function using an 8:1 MUX considering D as the input and A, B, C as the selection lines: **(3M)**
- $$F(A, B, C, D) = AB' + BD + B'CD'$$
- 3A.** The waveforms shown in the Fig.1 are applied to a negative edge – triggered S – R flip flop with active – HIGH PRESET and CLEAR. Draw the output waveform. Assume initially, the output Q is LOW. **(2M)**

 

**Fig. 1**

- 3B.** Explain the working of a parallel-in, serial-out shift register. Also draw the block diagram. **(3M)**
- 3C.** Design a Synchronous 3-bit up-down counter using J-K flip flop. Also draw the state diagram and the logic diagram. **(5M)**
- 4A.** Design a 2-input 2-output synchronous sequential circuit which produces an output  $z = 1$ , whenever any of the following input sequences 1100, 1010 or 1001 occur. The circuit resets to its initial state whenever output become 1. Use Mealy model. **(6M)**
- 4B.** Draw an ASM chart and state table for a 2-bit up-down counter having mode control input. **(4M)**

$M = 1$ : Up counting

$M = 0$ : Down counting

The circuit should generate an output 1 whenever the count becomes minimum or maximum.

- 5A.** What do you mean by programmable logic devices? Compare the important features of PROM, PLA and PAL devices. **(3M)**
- 5B.** Determine the size of the PROM required for implementing a single-digit BCD adder/ subtractor with a single control input for selection of operation. **(2M)**
- 5C.** Obtain a primitive flow table for a circuit with two inputs  $x_1$  and  $x_2$ , and two outputs  $z_1$  and  $z_2$ , that satisfy the following four conditions: **(5M)**
- (i) When  $x_1x_2 = 00$ , the output is  $z_1z_2 = 00$ .
  - (ii) When  $x_1 = 1$  and  $x_2$  changes from 0 to 1, the output is  $z_1z_2 = 01$ .
  - (iii) When  $x_2 = 1$  and  $x_1$  changes from 0 to 1, the output is  $z_1z_2 = 10$ .
  - (iv) Otherwise, the output doesn't change.

\*\*\*\*\*