

Reg. No.									
----------	--	--	--	--	--	--	--	--	--



Manipal Institute of Technology, Manipal

(A Constituent Institute of Manipal University)



THIRD SEMESTER B.TECH (INSTRUMENTATION & CONTROL ENGINEERING)

END SEMESTER EXAMINATIONS, NOV/DEC 2015

SUBJECT: ELECTRICAL & ELECTRONIC MEASUREMENTS [ICE 2102]

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ALL** the questions.
- ❖ Missing data may be suitably assumed.

- 1A.** Derive the expressions for unknown capacitance, its series internal resistance, dissipation factor, loss angle and power factor using Schering bridge. Also draw the phasor diagram under balance condition. **5**
- 1B.** With the help of schematic diagram and symbol, explain the working of electro-dynamometer type wattmeter. Also show how the pointer deflection is proportional to the active power dissipated in the load. **3**
- 1C.** With an example differentiate resolution and precision as applied to a voltmeter. **2**
- 2A.** Sketch the basic Cathode Ray Tube. Name each section. Explain the phenomena of displaying a time varying signal on the CRT screen. **5**
- 2B.** A Wein's bridge consists of the following constants arm AB, a resistance of 800Ω in parallel with a capacitance $0.4\mu F$, BC a resistance of 384Ω , CD a resistance 1200Ω and DA a resistance of 500Ω in series with a capacitance of $1\mu F$. Find the frequency for which the bridge is balanced. **3**
- 2C.** The voltages at opposite ends of 470Ω , $\pm 5\%$ resistor are measured as $V_1 = 12V$ and $V_2 = 5V$. The measuring accuracies are $\pm 0.5V$ for V_1 and $\pm 2\%$ for V_2 . Calculate the level of current and specify its accuracy. Also calculate the power dissipated in the resistor when the same current is displayed by an ammeter with $\pm 2\%$ accuracy. Determine the accuracy of the result. **2**
- 3A.** Describe how the Q factor of a coil is measured using a Q meter. **3**
- 3B.** With the block diagram and timing diagram explain the working of ramp type DVM. **3**
- 3C.** With a block schematic, explain the working principle of digital energy meter. **2**

3D.	With the help of neat circuit, explain the method of measurement of frequency using modulated ring technique.	2
4A.	With a figure explain construction and working of LED. With a circuit explain how is it used as a seven segment display.	3
4B.	With the help of necessary figures explain the working of optical recorder.	3
4C.	Draw and explain the circuit diagram for driving LCD (7 segment display). Illustrate how a decimal number '4' is made to display using LCD.	2
4D	How digital frequency meter can be used to determine the ratio of two frequencies?	2
5A.	With neat diagram explain the working of basic Regulated Power Supply.	4
5B.	With block diagram describe the working of spectrum analyser	4
5C.	Illustrate the digital technique for the measurement of capacitance.	2