

Reg. No.

I SEMESTER M.TECH (PESC)

END SEMESTER EXAMINATIONS, NOVEMBER 2015

SUBJECT: ANALOG AND DIGITAL SYSTEM DESIGN [ELE 509]

REVISED CREDIT SYSTEM

Time: 3 Hours

26 November 2015

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ANY FIVE FULL** questions.
- ❖ Missing data may be suitably assumed.
- ❖ DSP Quick reference table may be used.

1A. Design and implement a Butterworth high pass filter with magnitude/frequency response of 3dB attenuation at a frequency of 2KHz and 15dB attenuation at a frequency of 1KHz.

06

1B. Design and implement 4 bit flash ADC. Take $V_{ref}=5V$. If V_{in} is 2V find the value of b_1 , b_2 , b_3 and b_4 .

04

2A. Determine the analog filter transfer function of low pass Chebyshev Type-I filter with the following specifications: $A_p = -0.2dB$; $A_s = -18 dB$; $\Omega_p = 10,000$ rad/sec; $\Omega_s = 14,000$ rad/sec.

06

2B. Show that the circuit shown in Figure 2B has voltage gain A of the form

$$A = \frac{V_o}{V_i} = -K \frac{R_2}{R_1}.$$

 


Figure 2B

04

3A. List various operators in VHDL and give their order of precedence.

03

3B. Design and implement an analog square rooter with the help of analog multiplier.

02

3C. Draw the state diagram of logic design shown in Figure 3C.

 


Figure Q3C

05

4A. Write VHDL code for a 4 bit universal type shift register to do the following operations.

S1	S0	Operations
0	0	Hold
0	1	Shift left by one bit
1	0	Shift right by one bit
1	1	Parallel load

04

4B. Write the VHDL code to generate the sequence 16-8-4-2-1-16-8-4-2-1..... at a frequency of 1 Hz. System clock frequency available is 4.4 MHz.

04

4C. Translate the following code to a when...else statement.

```

process(a,b,j,k)
begin
    if a='1' and b='0' then
        step<="0100";
    elsif a='0' then
        step<=j;
    elsif b='1' then
        step<=k;
    else
        step<="0000";
    end if;
end process;

```

02

5A. Explain the structure of CLB in Xilinx Spartan IIE.

04

5B. Write a VHDL code for implementing 4:1 Mux using "with select" construct.

03

5C. Differentiate between signal assignment & variable assignment.

03

6A. With a block diagram explain the working of PLL. Hence design a frequency multiplier to generate frequency of 1 MHz from input frequency of 1 kHz.

06

6B. Evaluate the following expression and determine the resulting value.

W= "01010101", X="1001", Y="0110", Z="01010100";

(i) K= W or X & not Y xor Z rol 2 (ii) -7 mod -2

02

6C. List the merits and demerits of analog active filters compared to passive filters.

02