



Reg. No.									
----------	--	--	--	--	--	--	--	--	--

MANIPAL INSTITUTE OF TECHNOLOGY  
Manipal University



**FIRST SEMESTER M.TECH (DEAC & ME) DEGREE END SEMESTER EXAMINATION**  
**NOV/DEC 2015**  
**SUBJECT: ANALOG AND RF VLSI DESIGN [ECE - 503]**

**TIME: 3 HOURS**

**MAX. MARKS: 50**

**Instructions to candidates**

- Answer **ANY FIVE** full questions.
- Missing data may be suitably assumed.

- 1A. Give the circuit of double cascode current sink. Using small signal ac model, derive the expression for output resistance. What is the minimum output voltage across the current sink?
- 1B. Apply half-circuit concept to find small-signal differential voltage gain for the circuit given in FIG. 1B. Given that all transistors in the circuit are saturated. Assume  $\lambda \neq 0$ ,  $\gamma \neq 0$ .
- 1C. Show that a negative capacitance can be realized using an amplifier block having suitable gain A and a passive capacitance C. State the principle used.

(5+3+2)

- 2A. Discuss the improved wide-swing cascode current mirror circuits.
- 2B. In a NMOS source follower circuit with a current sink load, all transistors have  $W/L = 100 \mu\text{m} / 2 \mu\text{m}$ . Given that  $I_{\text{bias}} = 100 \mu\text{A}$ ,  $\eta = 0.1$ ,  $K_n = 75 \mu\text{A}/\text{V}^2$ ,  $K_p = 30 \mu\text{A}/\text{V}^2$ ,  $r_{\text{ds-n}} = 128 \text{ k}\Omega$ ,  $r_{\text{ds-p}} = 192 \text{ k}\Omega$ . Find small-signal voltage gain and output resistance.
- 2C. Define the term single parameter sensitivity. Derive an expression for sensitivity of output current  $I_o$  with respect to  $V_{\text{DD}}$  in a cascode current sink circuit. Give your comments.

(5+3+2)

- 3A. Give the schematic circuit of a PMOS based folded cascode amplifier. Derive the exact expression for small-signal voltage gain and output resistance. Also give the approximate expression for voltage gain.
- 3B. Show that the small-signal voltage gain neglecting channel length modulation effect for the circuit shown in FIG. 3B is given by  $A_v = 1/(1 + \eta)$ .
- 3C. Give the circuit diagram of folded cascade opamp topology and salient features.

(5+3+2)

- 4A. Show how a variable gain amplifier (VGA) is implemented using differential amplifier. Discuss the two Gilbert cell topologies.
- 4B. Consider the circuit of nMOS CG amplifier with a pMOS current source load.  $M_1$  is the input MOS device and  $M_2$  is the output MOS of  $M_2$ - $M_3$  current source circuit. Assume that the CG amplifier has a bias current of 0.1mA and that all transistors have a  $W/L$  of  $100 \mu\text{m} / 2 \mu\text{m}$ . Given that  $K_n = 50 \mu\text{A}/\text{V}^2$ ,  $K_p = 17 \mu\text{A}/\text{V}^2$ ,  $g_{\text{ds,n}} = 10 \mu\text{mho}$ ,  $g_{\text{ds,p}} = 5 \mu\text{mho}$ ,  $\eta = 0.1$ . Compute small-signal voltage gain.
- 4C. Derive the expression for small-signal common-mode voltage gain in a source-coupled NMOS differential amplifier neglecting second-order effects.

(5+3+2)

- 5A. Give the CMOS circuit of balanced Operational Transconductance Amplifier? Compare OTA and op-amp with respect to following: [i] area [ii] input and output resistance [iii] gain [iv] bandwidth
- 5B. Explain the channel length modulation. Derive the expression for channel length modulation parameter ( $\lambda$ ).
- 5C. Discuss the structure of double poly capacitor.

(5+3+2)

- 6A. Explain the basic PLL block diagram with necessary analog building blocks. Show how PLL can be used for FM demodulation.
- 6B. With appropriate figures, explain how the differential operation can reduce following: [i] effect of supply noise [ii] Effect of coupled noise from digital clock signal.
- 6C. State the principle used in the design of RF Mixers.

(5+3+2)

 


FIG. 1B

 


FIG. 3B