

Reg. No.									
----------	--	--	--	--	--	--	--	--	--



Manipal Institute of Technology, Manipal

(A Constituent Institute of Manipal University)



FIFTH SEMESTER B.TECH (INSTRUMENTATION AND CONTROL ENGINEERING)

END SEMESTER EXAMINATIONS, NOV/DEC 2015

SUBJECT: DATA ACQUISITION AND INTERFACING [ICE 309]

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ANY FIVE FULL** questions.
- ❖ Missing data may be suitably assumed.

- | | | |
|------------|---|----------|
| 1A. | With a neat diagram explain the operation of sample and hold circuit as
(i) Peak follower (ii) Tracking Sample/Hold | 3 |
| 1B. | Explain the operation of multiplexer
(i) which is characterized by high immunity to transient voltages
(ii) which is used to remove any interference due to common-mode signal. | 4 |
| 1C. | With necessary sketches explain various characteristics of MOS switches. | 3 |
| 2A. | Explain the operation of sigma delta converter with necessary block diagram and waveform | 3 |
| 2B. | An 8 bit DAC produces $V_{out}=0.05$ V for digital input of 00000001. Find the full scale output voltage. What is the resolution? What is V_{out} for an input of 00101010? | 4 |
| 2C. | Explain the transfer characteristics of PLL with necessary sketch. | 3 |
| 3A. | Describe different modes of operation of 8255 with its block diagram. | 5 |
| 3B. | With a neat diagram explain the operation of PLL as AM detector and phase shifter. | 3 |
| 3C. | Explain the interrupt sequence of 8259. | 2 |
| 4A. | With neat diagram explain the interfacing of temperature sensor with PIC micro controller. | 3 |
| 4B. | Write an ALP for 8051 to rotate a stepper motor by 90° clockwise. Assume step angle of 2° | 2 |
| 4C. | With a block diagram explain control logic, registers, transmitter and receiver sections of 8251 | 5 |
| 5A. | Explain bidirectional motor control using L293 chip. | 3 |
| 5B. | Explain the flowchart for working of microcontroller based angular speed measuring instrument. | 2 |
| 5C. | With a neat diagram explain time multiplexed 7-Segment Display interface with the microcontroller. | 3 |
| 5D. | For a given ADC0848 $V_{ref}=2.56$ V. Calculate the D0-D7 output if the analog input is (a) 1.7V (b) 2.1V | 2 |
| 6A. | List the performance specifications of ADC | 2 |
| 6B. | Explain delta modulation and demodulation with necessary block diagrams. | 4 |
| 6C. | With timing diagram write the steps of data conversion of ADC 0804. | 4 |
