

To Dr. AK

By DR. AMITA TOLPADI

Amita Tolpadi
6.12.2016

Reg. No.



MANIPAL INSTITUTE OF TECHNOLOGY

MANIPAL

A Constituent Institution of Manipal University

I SEMESTER MSc. Physics

END SEMESTER EXAMINATIONS, NOV 2016

SUBJECT: Fundamentals of Electronics (PHY 607)

Time: 3 Hours

MAX. MARKS: 50

❖ Answer **ANY FIVE FULL** questions.

1A. Draw the a.c. equivalent circuit for bipolar junction transistor in common emitter configuration and obtain the expressions for the following parameters: (i) input impedance (ii) voltage gain (iii) output impedance. **(6 M)**

1B. Determine the following for the network of Fig. 1.
(a) V_D . Given $I_{DQ} = 2.4\text{mA}$ and $V_{GSQ} = -1.8\text{V}$
(b) V_S
(c) V_{DS}
(d) V_{DG}

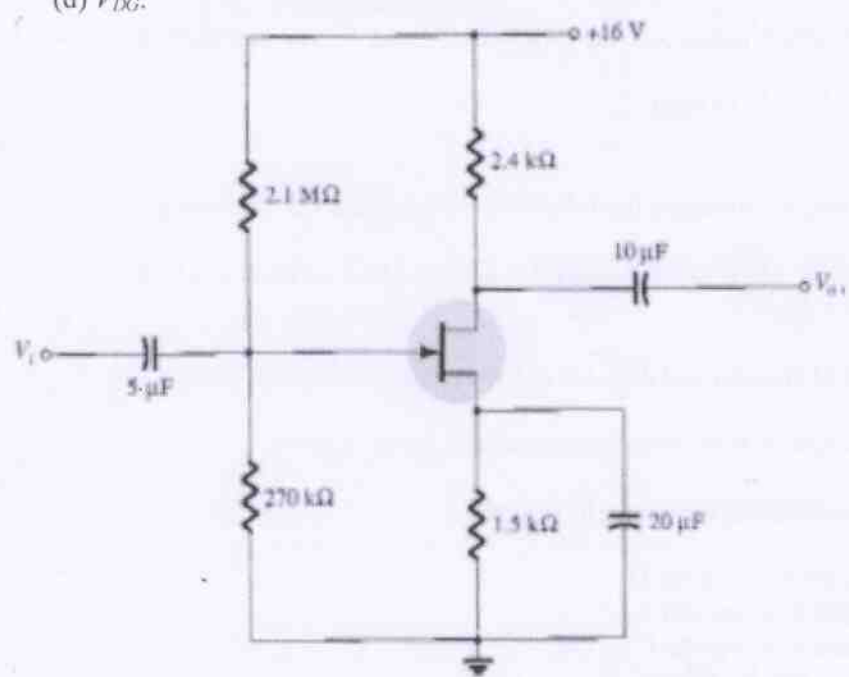


Fig.1


(4M)

2A. Discuss how Timmer 555 can be used as monostable multivibrator. **(5 M)**

2B. Draw the circuit diagram of high pass filter using op-amp and derive the expression for its gain. **(5 M)**

3A. Describe the working of UJT relaxation oscillator and obtain an expression for its time period. (6 M)

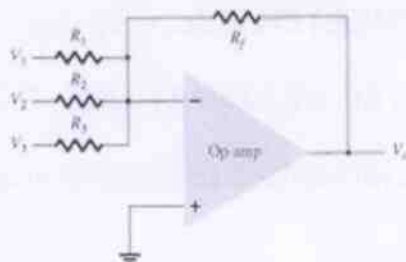3B. Calculate the output voltage of the given op-amp summing amplifier for the following sets of voltages and resistors. $R_f = 1 \text{ M}\Omega$, $V_1 = 1 \text{ V}$, $V_2 = 2 \text{ V}$, $V_3 = 3 \text{ V}$, $R_1 = 500 \text{ k}\Omega$, $R_2 = 1 \text{ M}\Omega$, $R_3 = 1 \text{ M}\Omega$.



(2 M)

3C. Draw the circuit diagram for adjustable voltage regulator using LM317. (2M)

4A. Discuss in detail the design of synchronous counter. (6 M)

4B. Determine the output voltage caused by most significant bit in a 3-bit ladder ($R/2R$) if the input levels are 0=0V and 1=10V. (4 M)

5A. Draw the circuit diagram of clocked J-K flip-flop with preset and clear inputs using NAND gates and explain its truth table. (3 M)

5B. (i) Convert the following decimal number to binary:
 a) 45 b) 0.625 (2M)
 (ii) Determine the decimal values of the following signed binary numbers expressed in 1's complement:
 a) 00010111 b) 11101000

(2 M)

(iii) Use a Karnaugh map to minimize the following SOP expression

$$\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}CD + A\bar{B}CD + \bar{A}\bar{B}C\bar{D} + \bar{A}BC\bar{D} + ABC\bar{D} + A\bar{B}C\bar{D}$$

(3 M)

6A. Explain the functions of encoder and decoder and give an application of each. (3 M)

6B. Describe the bus structure of 8085 microprocessor with block diagram. (4 M)

6C. Write a program to perform the following functions

- Load the number 8BH in register D
- Load the number 6FH in register C
- Increment the content of register C by one
- Add the contents of registers C and D
- Display the sum at the output port1

(3 M)
