Reg. No.



MANIPAL INSTITUTE OF TECHNOLOGY

A Constituent Institution of Manipal University

## I SEMESTER M.TECH (POWER ELECTRONICS AND DRIVES) **END SEMESTER EXAMINATIONS, NOV/DEC 2016**

SUBJECT: POWER ELECTRONICS DEVICES & CONVERTER TOPOLOGIES [ELE 5121] **REVISED CREDIT SYSTEM** 

| Time       | e: 3 Hours   | Date:                             | 29 November 2016  | MAX. MARKS: 5   | 50        |
|------------|--|-----------------------------------|---|---|-----------|
| Instr      | ructions to Candidates:  |                                   |   |   |           |
|            | Answer <b>ALL</b> the questions.   |                                   |   |   |           |
|            | Missing data may be suitab   | le assun                          | ned.  |   |           |
| 1A.        | Explain the operating princip<br>MOSFET.   | le of G                           | ΓO and draw the switching character   | istics of power   | 05        |
| 1B.        | Derive the expression for switc (slow charging) case.  | h transi                          | tion energy losses in turn off snubber of   | ircuits for k > 1   | 03        |
| 1C.        | A thyristor has a maximum aver<br>pulsed gate current at a pulse<br>cathode voltage drop to be 1.5 v   | rage gate<br>frequen<br>olt. Find | e power dissipation limit of 0.4 watts. It is<br>bey of 15 KHz and duty ratio of 0.5. As<br>d out the allowable peak gate current ma                              | s triggered with<br>suming the gate<br>gnitude.             | <i>02</i> |
| 2A.        | Explain the extinction angle confection for the extinction of the extinction of the extension of the extensi | ontrol ar<br>vaveforn             | nd pulse-width modulation control sch<br>ns.  | emes for power  | 05        |
| 2B.        | A $3\phi$ fully controlled thyristor b<br>50 $\Omega$ . Determine the average loa<br>30°. The supply voltage is 415V,  | oridge is<br>ad volta<br>Зф. Ass  | connected to a highly inductive load wit<br>ge, average load current, input PF for a<br>sume the load current is ripple free.                                     | h a resistance of<br>trigger angle of                       | 03        |
| 2C.        | A $1\phi$ full converter fed from 2<br>When loaded with a constant<br>Compute the value of source inc  | 20V, 60<br>output<br>luctance     | Hz supply gives an output voltage of 2<br>current of 15A, the overlap angle is<br>e.  | 00V at no load.<br>found to be 8º.                          | <i>02</i> |
| 3A.        | Draw the circuit diagram of the waveforms.   | e boost s                         | switching regulator and explain its oper  | cation with neat  | 05        |
| 3B.        | The buck regulator has an inp<br>Va=7V and the peak to peak out<br>the peak to peak ripple current<br>inductance c) filter capacitor.  | out volta<br>put ripp<br>of indu  | ge of Vs=15V. The required average o<br>ole voltage is 25mV. The switching freque<br>actor is limited to 0.9A. Determine a) du                                    | utput voltage is<br>ency is 30KHz. If<br>ty cycle b) filter | 03        |
| 3C.        | Draw the circuit diagram of Cuk  | regulate                          | or.   |   | <i>02</i> |
| 4A.        | Explain the principle of opera circuit diagram and waveforms.  | tion of                           | single phase/single phase cycloconver   | ter with a neat   | 05        |
| 4B.        | A single phase full wave ac vol $Vs=120V(rms)$ , 50Hz. The delay a) rms output voltage $V_0$ b) input  | oltage co<br>angles<br>(t PF c) a | ontroller has a R load of R=20Ω and th<br>of thyristors T <sub>1</sub> & T <sub>2</sub> are equal: $\alpha_1 = \alpha_2 = \alpha_2$<br>average thyristor current. | ie input voltage<br>= $\pi/2$ . Determine                   | 03        |
| <b>4C.</b> | Draw the load voltage and curre  | ent wave                          | forms for a synchronous tap changer wi  | th RL load.   | <i>02</i> |
| 5A.        | Briefly explain the 180° conduct   | tion mod                          | le of three phase inverters.  |   | 05        |
| 5B.        | A single phase full bridge inver<br>Determine a) rms output voltage<br>neak currents of each transist  | rter has<br>ge at fun             | a R load of R = $2.8\Omega$ and the dc input<br>adamental frequency V <sub>1</sub> b) output power  | voltage is 52V.<br>r c) average and                         |           |
|            | f) DF.   | Ji uj pe                          | an reverse blocking voltage of call the   |   | <i>03</i> |
| 5C.        | What are the methods for voltage   | ge contro                         | ol in single phase inverters?   |   | 02        |