



MANIPAL INSTITUTE OF TECHNOLOGY  
Manipal University  
**FIFTH SEMESTER B.TECH (E & C) DEGREE END SEMESTER**  
**EXAMINATION - NOV/ DEC 2016**  
**SUBJECT: VLSI DESIGN (ECE - 305)**

TIME: 3 HOURS

MAX. MARKS: 50

**Instructions to candidates**

- Answer **any five full** questions.
- Missing data may be suitably assumed.



- 1A. Explain the transfer characteristic of the CMOS inverter showing different regions. For CMOS inverter, derive the expression for  $V_{inv}$ .  
(5+3+2)
- 1B. Compare BJT and MOSFET with respect to following parameters:  
(i) Transconductance value (ii) Input impedance (iii) Noise (iv) Current handling capability
- 1C. Discuss the influence of  $\beta_n/\beta_p$  on inverter DC transfer characteristic.  
(5+3+2)
- 2A. Explain the steps involved in the twin-tub fabrication process. What is the use of epitaxial layer?
- 2B. Calculate the effective capacitance for the multi-layer structure given in **FIG. 2B** for 5  $\mu\text{m}$  process. Refer the **Table I** for area capacitance calculation.
- 2C. Draw stick notation for [i] Depletion type pull-up NMOS inverter [ii] Single phase Pre-charge Evaluate Dynamic CMOS two-input NOR gate  
(5+3+2)
- 3A. Derive  $Z_{pu}/Z_{pd}$  ratio for Pseudo NMOS inverter driven from a similar inverter.
- 3B. Explain the working of 6T SRAM cell.
- 3C. Find the region of operation for NMOS based circuits given in **FIG. 3C**. Assume  $V_T = 0.4\text{V}$   
(5+3+2)
- 4A. [i] The NMOS transistors in the circuit of **FIG. 4A** have  $V_{thn} = 1\text{ V}$ ,  $\mu_n C_{ox} = 120\ \mu\text{A/V}^2$  and  $L_1 = L_2 = L_3 = 1\ \mu\text{m}$ . Find the required values of gate width for each of  $Q_1$ ,  $Q_2$  and  $Q_3$  to obtain the voltage and current values indicated.  
[ii] State the advantages of transmission gate over NMOS/PMOS pass transistors.
- 4B. Justify as why the NOR gate is preferred over NAND gate for the implementation of NMOS PLA. Explain with an example.
- 4C. Give the CMOS implementation and stick notation for the function  $Z = (A B + C)'$ .  
(5+3+2)

- 5A. Give the implementation of NMOS based R/2 stage shift register cell and explain the working principle. Give the stick notation and layout of the NMOS based R/2 stage shift register cell.
- 5B. With a truth table, give the NMOS implementation of NOR based SR latch
- 5C. Give the NMOS implementation of following functions:  $F = \overline{ABC} + D$  and  $Y = A \odot B$ .

(5+3+2)

- 6A Explain structured implementation of N-bit bus arbitration logic. Give the stick notation. Discuss the suitability of implementation using NMOS/ CMOS technology.
- 6B Give the implementation of two-input NOR gate using BiCMOS.
- 6C Give an account of different trends in VLSI technology.

(5+3+2)

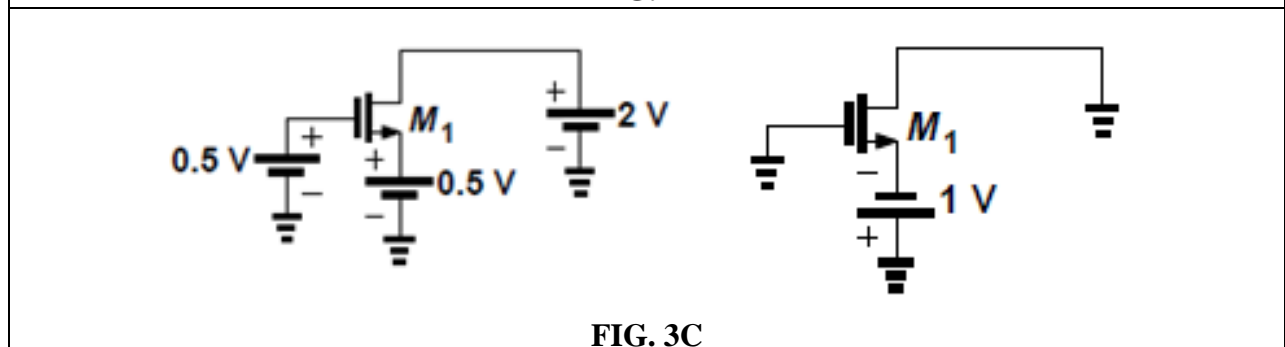 

 


FIG. 4A

Table I Typical values of area capacitance for 5  $\mu\text{m}$  technology

<i>Capacitance</i>	<i>Value in <math>\text{pF} \times 10^{-4}/\mu\text{m}^2</math> (Relative values in brackets)</i>	
Gate to channel	4	(1.0)
Diffusion (active)	1	(0.25)
Polysilicon* to substrate	0.4	(0.1)
Metal 1 to substrate	0.3	(0.075)
Metal 2 to substrate	0.2	(0.05)
Metal 2 to metal 1	0.4	(0.1)
Metal 2 to polysilicon	0.3	(0.075)