

Reg. No.									
----------	--	--	--	--	--	--	--	--	--



MANIPAL INSTITUTE OF TECHNOLOGY
MANIPAL

A Constituent Institution of Manipal University

FIFTH SEMESTER B.TECH. (INSTRUMENTATION AND CONTROL ENGG.)
END SEMESTER EXAMINATIONS, NOV/DEC 2016

SUBJECT: DATA ACQUISITION AND INTERFACING [ICE 309]

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ANY FIVE** questions.
- ❖ Missing data may be suitably assumed.

- 1A.** Explain the basic and inverting type of sample / hold circuit with necessary diagrams. **5**
- 1B.** What is low level multiplexing? Explain flying capacitor multiplexer in detail. **5**
- 2A.** Describe any four specifications of DAC. **4**
- 2B.** Explain any three methods of Signal conditioning in data acquisition system. **3**
- 2C.** Compare flash and pipeline ADC. **3**
- 3A.** With schematic and tree diagram explain the working of successive approximation ADC. **5**
- 3B.** Find the output of 6 bit two stage flash ADC for an input of 6.8V with reference voltage 10V **3**
- 3C.** List the advantages and disadvantages of binary weighted DAC **2**
- 4A.** With necessary diagrams explain the working of R-2R DAC. What is the output voltage when the input is 0010. **5**
- 4B.** Explain the working of edge triggered phase detector with necessary diagrams. **3**
- 4C.** Write the control word format for 8255. **2**
- 5A.** With a neat block diagram explain programmable interval timer **5**
- 5B.** With a neat diagram explain any two applications of PLL. **5**
- 6A.** Explain with block diagram **5**
 - i) Control logic and registers
 - ii) Transmitter and receiver sections of 8251
- 6B.** With neat block diagram explain microcontroller based angular speed measuring instrument. **5**