



## FIFTH SEMESTER B.TECH (INSTRUMENTATION & CONTROL ENGG.)

END SEMESTER EXAMINATIONS, NOV/DEC 2016

SUBJECT: DIGITAL SYSTEM DESIGN [ICE 311]

Time: 3 Hours

MAX. MARKS: 50

### Instructions to Candidates:


- ❖ Answer **ANY FIVE FULL** questions.
- ❖ Missing data may be suitably assumed.

1A. Write the truth table for following equation: 3

$$F = (A \oplus B)C + A'(B \oplus C)$$

1B. Write VHDL code for the following circuit. Assume that the gate delays are negligible. 4

 - (a) Use concurrent statements.  
(b) Use a process with sequential statements.



1C. What do you mean by hazards in combinational networks? Explain the types of hazards. 3


2A. Explain the different Scalar data types used in VHDL. Illustrate each with examples. 4

2B. Draw a complete Y-chart showing different levels and domains of abstraction. 3

2C. Explain the structure of a VHDL program. 3

3A. Write a sequential VHDL code for a T flip-flop. 3

 3B. Write a VHDL description of the following combinational circuit using concurrent statements. 4



3C. Explain procedures and write a procedure for sorting a greater value when two values are provided. 3

4A. Write a structural VHDL code for a full adder assuming that full adder has been defined as a component. 4

- 4B.** Briefly explain the different operators used in VHDL. **3**
- 4C.** Write a test bench to verify the working of a JK flip-flop. **3**
- 5A.** Briefly explain how ROMs are classified. **3**
- 5B.** Explain the different types of FPGA programming technologies. **4**
- 5C.** Find a minimum-row PLA to implement the following two functions: **3**
- $$f(A, B, C, D) = \Sigma m(3, 4, 6, 9, 11)$$
- $$g(A, B, C, D) = \Sigma m(2, 4, 8, 10, 12, 14)$$
- $$h(A, B, C, D) = \Sigma m(3, 6, 7, 10, 11)$$
- 6A.** With a block diagram explain the operation of a programmable I/O block in FPGA. **6**
- 6B.** Explain scan testing with a block diagram. **4**

\*\*\*\*\* END \*\*\*\*\*