



VII SEMESTER B.TECH (ELECTRICAL & ELECTRONICS ENGINEERING)

MAKEUP EXAMINATIONS, DEC 2016 - JAN 2017

SUBJECT: HVDC & FACTS [ELE 433]

REVISED CREDIT SYSTEM

Time: 3 Hours

Date: 28 December 2016

Max. Marks: 50

Instructions to Candidates:

- ❖ Answer **ANY FIVE FULL** questions.
- ❖ Missing data may be suitably assumed.

- 1 A. A 400KV, 50 Hz symmetrical transmission line is compensated by connecting a capacitor in series at the midpoint of the line. Design the capacitor to increase the maximum power transferred through the line by 10% for transmission lines i) 200Km long and ii) 250Km long.
 $l=1\text{mH/Km}$ and $c=11.1\text{nF/Km}$. (05)
- 1 B. Draw the equivalent circuit diagram of an SVC. Explain its working principle. (05)
- 2 A. A 66KV, 50Hz line with line parameters $l=1\text{mH/Km}$ and $c=11.1\text{nF/Km}$. Design a STATCOM (controlled by SPWM method) to maintain uniform voltage throughout the line of length 100Km. (05)
- 2 B. Draw the circuit diagram of a 3 phase 3 level cascaded H-bridge multi-level. Explain the operating principle and draw the waveforms of pole voltage, line voltage and phase voltage of any one phase. (05)
- 3 A. Draw a schematic diagram of the feedback control system of STATCOM. Explain its working. (05)
- 3 B. Compare SSSC and TCSC connected in series at the midpoint of the transmission line. (05)
- 4 A. A 22KV, 50Hz symmetrical line with parameters $l=1\text{mH/Km}$ and $c=11.1\text{nF/Km}$ is compensated with TCSC connected at the midpoint of the line. The length of the line is 200Km. Design the TCSC to transmit any power at constant δ of 10° . (05)
- 4 B. Draw the equivalent circuit diagram of a UPFC connected to the transmission line. Explain its operation. (05)
- 5 A. Draw the schematic diagram of a HVDC converter station and explain each part. (05)
- 5 B. Explain the schemes for interconnecting two areas of different frequencies, draw the schematic diagram. (05)
- 6 A. The input voltage of the HVDC rectifier is 80KV, Find the current and the average output voltage if a) $\alpha=10^\circ$ and $u=10^\circ$ b) $\alpha=20^\circ$ and $u=15^\circ$ transformer leakage reactance 10Ω (05)
- 6 B. Explain overcurrent and overvoltage protection schemes in HVDC system converters. (05)