



SEVENTH SEMESTER B.TECH. (INSTRUMENTATION & CONTROL ENGG.)
END SEMESTER EXAMINATIONS, DEC 2016/JAN 2017

SUBJECT: POWER ELECTRONICS [ICE 405]

Time: 3 Hours

MAX. MARKS: 50

Instructions to Candidates:

- ❖ Answer **ANY FIVE FULL** questions.
- ❖ Missing data may be suitably assumed.

- 1A.** With a two transistor model, obtain an expression for the anode current of a SCR. **4**
- 1B.** An AC circuit using a SCR has a dv/dt rating of 25 volts/ μs , source inductance of 0.2 mH and RMS value of supply voltage is 230 V. With a damping factor 0.65, find the values of resistance & capacitance of the snubber circuit. **3**
- 1C.** With neat circuit diagram and relevant waveforms, describe the working of a UJT trigger circuit for an SCR. **3**
- 2A.** What is the need of a commutation circuit? With the help of relevant circuit, waveforms and mathematical equations, explain the working of class-D commutation circuit. **5**
- 2B.** With circuit diagram and waveforms, discuss the working of class A commutation circuit. **3**
- 2C.** SCRs with ratings of 1100 Volts and 250 Amperes are available to be used in a string to handle a load 6kV and 1 kA. Calculate the number of series and parallel units required in the string for a de-rating factor of (a) 0.2 (b) 0.4. **2**
- 3A.** An AC source voltage of 230 V, 50 Hz is connected to $R = 8\Omega$ and a DC battery $E = 150$ V through a single SCR. On the assumption that the SCR is fired continuously, find
 - a) Average value of charging current.
 - b) RMS value of the charging current.
 Derive the expressions used. **5**
- 3B.** With the help of circuit diagram and waveforms, describe the working of a single phase semi converter. **3**
- 3C.** List any four comparison between BJT and IGBT. **2**

- 4A.** A 230 V, 50 Hz single phase supply is connected to a single phase half wave converter with the following load configurations : **5**
- a) R Load
 - b) RL Load
- Assuming a firing angle delay of 30° , draw the load voltage and load current waveforms with respect to supply voltage. Also calculate average DC output voltage for each circuit configurations.
- 4B.** Describe the working of three phase full converter with a neat circuit diagram. Show the conduction range of the SCR's for firing angle of 0° and 30° with respect to input pulse. **5**
- 5A.** With the help of neat diagram and waveforms, explain the working of Morgan's chopper. **4**
- 5B.** How can the duty cycle be varied to control the operation of a step up chopper? Derive the expression used. **3**
- 5C.** What are dual converters? Describe the working of a dual converter with circulating current mode of operation. **3**
- 6A.** What are inverters? Explain the working of three phase bridge inverter with firing sequence and output waveforms for phase and line voltage for 120° mode of operation. **6**
- 6B.** Discuss the operation of a single phase AC to AC voltage control with respect to phase control and ON-OFF control. **4**
