

## MANIPAL INSTITUTE OF TECHNOLOGY MANIPAL A Constituent Institution of Manipal University

## SEVENTH SEMESTER B.TECH. (INSTRUMENTATION & CONTROL ENGG.) END SEMESTER EXAMINATIONS, NOV/DEC 2016

## SUBJECT: POWER ELECTRONICS [ICE 405]

Time: 3 Hours

MAX. MARKS: 50

## Instructions to Candidates:

- \* Answer ANY FIVE FULL questions.
- Missing data may be suitably assumed.
- 1A. What is the need for static and dynamic equalization circuits for series connected SCR's? 4Draw the equalization circuits and hence explain how they achieve equalization.
- 1B. With neat circuit diagram and waveforms, describe the working of a line synchronized 3UJT circuit capable of producing trigger pulses in each half cycle of the AC waveform.
- 1C. A SCR is used as a semi-conductor switch to connect a load of 5Ω and 0.05H to a 240 3
  Volts, 50 Hz supply. Find the expression for current and triggering angle to ensure that no current transient occurs.
- 2A. What are the purposes of commutation circuits? With relevant circuit, waveforms and 5 mathematical model, discuss the working of a class-B commutation circuit.
- **2B.** For a LC circuit (L =  $10\mu$ H and C= $50\mu$ F), supplied with a DC voltage of 220 volts, the **3** SCR is turned on at time t=0. Determine the conducting time of the SCR and voltage across the capacitor at the instant of turnoff if the initial current of the inductor is 0 when the capacitor is uncharged.
- **2C.** The V<sub>g</sub>-I<sub>g</sub> characteristics of a SCR is given by  $V_g = 1 + (9*I_g)$ . The gate pulses are **2** rectangular with an amplitude of 12 V and duration of 60 µs with a duty cycle of 0.3. Find series resistance  $R_g$  in the gate circuit to limit peak power loss to 6 Watts and the average gate power loss.
- 3A. Explain the effect of source inductance on the performance of line commutated 4 converters. Derive an expression for output DC voltage of a single phase fully controlled converter taking into account of source inductance.
- **3B.** For a half controlled AC DC converter configuration fed by a 230 Volts, 50 Hz supply, **4** an inductance of L = 0.2H is connected in series with a battery of E = 50 V to limit the

charging current. The SCR is gated at  $W_t = 60^\circ$ . Find

- I. Expression of charging current.
- II. Current extinction angle and SCR conduction angle.
- **3C.** Write any four points of comparison between a P-MOSFET and IGBT.
- 4A. A 230 V, 50 Hz single phase supply is connected to single phase bridge converter of the 6 following configurations :
  - I. Half controlled bridge rectifier
  - II. Fully controlled bridge rectifier

Assuming firing angle delay of 30°, draw the load voltage and load current waveforms with respect to supply voltage. Also calculate average DC output voltage for each circuit configurations.

- 4B. With a neat circuit diagram, describe the working of a three phase full converter. Show4 the conduction range of the SCR's for firing angle of 0° with respect to the input pulse.
- 5A. With the help of neat diagram and waveforms, explain the working of Morgan's chopper. 4
- 5B. Discuss the time ratio control method of choppers with relative advantages and 3 disadvantages.
- 5C. What are dual converters? Describe the working of a dual converter with non-circulating 3 current mode of operation.
- 6A. What are inverters? Explain the working of three phase bridge inverter with firing 6 sequence and output waveforms for phase and line voltage for 180° mode of operation.
- 6B. What are cyclo-converters? With the help of neat circuit diagram discuss the working of 4 a single phase mid-point step down cyclo-converter.

2