



Reg. No.

INTERNATIONAL CENTRE FOR APPLIED SCIENCES
(Manipal University)
II SEMESTER B.S. DEGREE EXAMINATION
SUBJECT: ELEMENTS OF BIOMEDICAL ENGINEERING (BM121)
(BRANCH: BIOMEDICAL)
Wednesday, 3 May 2017

Time: 3 Hours

Max. Marks: 100

- ✓ **Answer ANY FIVE full Questions.**
- ✓ **Assume relevant data if missing.**
- ✓ **Draw diagrams wherever necessary.**

1. (a) Simplify the Boolean function using KMap method. (6)
$$F(A, B, C, D) = \sum m(0, 2, 3, 4, 6, 8, 10, 11, 12, 14)$$

(b) Design an asynchronous decade counter using JK Flipflops. (8)
(c) Perform the following subtractions using 1's and 2's complements. (6)
(i) $11010_2 - 10000_2$ (ii) $11010_2 - 1101_2$ (iii) $100_2 - 11000_2$
2. (a) With neat diagrams, explain the working of PN diode under forward and reverse biased conditions. Draw and explain its V-I characteristics. (7)
(b) What is the major difference between photodiode and LED? Give the construction, working principle and two applications of LED. (6)
(c) What is Junction Field Effect Transistor (JFET)? With a neat diagram, explain its construction details and operation. (7)
3. (a) What is virtual ground with reference to an op-amp? Illustrate. (4)
(b) What are the characteristics of an ideal operational amplifier? (6)
(c) Draw an op-amp open-loop and closed loop inverting amplifier circuit and derive expressions for gain of the amplifier in both configurations. (10)
4. (a) What is bio-metrics? List and explain all essential factors to be considered in biomedical instrumentation. (8)
(b) With help of a block diagram explain different components of "man-instrument" system. (6)
(c) What is electrode-electrolyte interface? Explain. (6)

5. (a) Simplify the given expression using Boolean algebra techniques. (2)

$$[A\bar{B}(C + BD) + \bar{A}\bar{B}]C$$
- (b) List and explain various bio-potential recording electrodes. (12)
- (c) Design a 3-input op-amp summing amplifier with a gain of 1. (6)
6. (a) What is a Flipflop? Give the logic diagram and truth table of a JK Flipflop. (8)
- (b) An op-amp inverting amplifier has $R_F = 5K\Omega$, and $R_G = 10K\Omega$. Compute the closed loop gain of the amplifier, and the output voltage, if the input voltage is -3 V. (5)
- (c) Realize the following Boolean function using 8x1 MUX. (7)

$$F(A B C D) = \sum 1, 2, 4, 5, 6, 8, 10, 11, 12, 14$$
7. (a) Draw typical electrocardiogram and explain different waves present in it. (2+6)
- (b) What is a Half adder? Design a half adder using minimum number of NAND gates. (5)
- (c) Design a 4-bit binary adder-subtractor circuit. (7)
8. (a) What is Zener break down? With a neat diagram, describe a reverse biased Zener diode and its reverse characteristics. (6)
- (b) With a neat diagram, describe how a NPN transistor is biased. List two important applications of BJT. (6)
- (c) How do you make use of Electromyogram to measure sensory nerve conduction velocity? (8)

