



Reg. No.									
----------	--	--	--	--	--	--	--	--	--

# INTERNATIONAL CENTRE FOR APPLIED SCIENCES

(Manipal University)

## III SEMESTER B.S. DEGREE EXAMINATION – APRIL / MAY 2017

SUBJECT: DC AC CIRCUIT ANALYSIS (EE 232)

(BRANCH: MECH, MET & IP)

Saturday, 13 May 2017

Time: 3 Hours

Max. Marks: 100

- ✓ Answer ANY FIVE full Questions.
- ✓ Missing data, if any, may be suitably assumed

**1A.** A 3 Phase, 220 V, 50 Hz, 11.2 kW induction motor has a full load efficiency of 88% and draws a line current of 38 A under full load. Find the power factor of the motor and the wattmeter readings to measure power input.

**1B.** Find the resistance between A & B (Fig 1B).

(10+10)

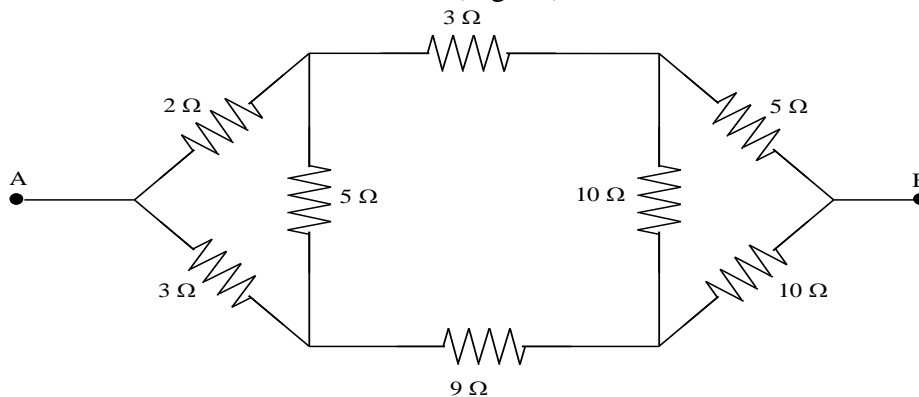


Fig 1B.

**2A.** Find the impedance  $Z_L$  so that maximum power can be transferred to it. Find the maximum power (Fig 2A).

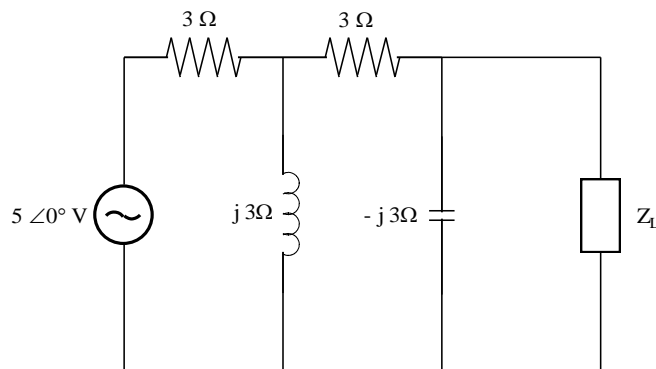


Fig 2A

**2B.** Find the value of R such that the circuit is in resonance (Fig 2B)

(12+8)

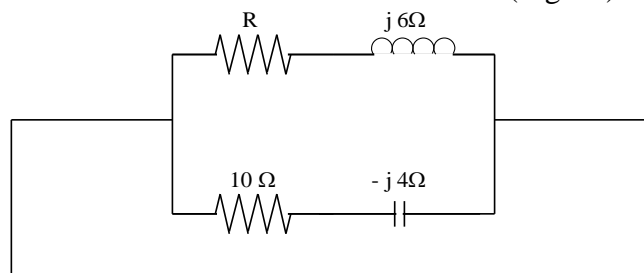


Fig 2B

- 3A.** Using mesh analysis determine the current supplied by the source. Verify the answer by node analysis (Fig 3A)

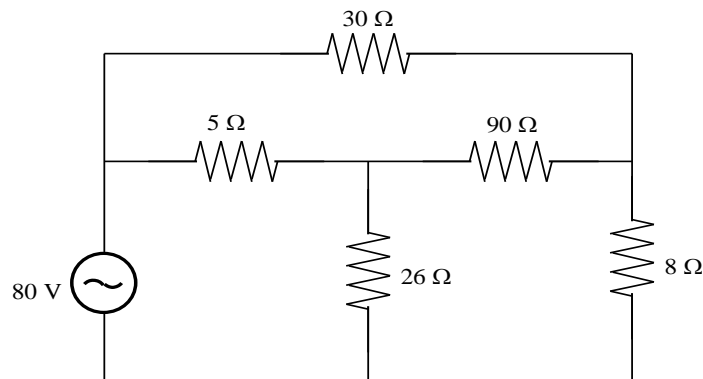


Fig 3A

- 3B.** A voltage  $v(t) = 10 \sin \omega t$  is applied to a series RLC circuit. At resonant frequency the voltage across capacitor is 500 V. The bandwidth of the circuit is 400 rads / sec. At resonance impedance of the circuit is 100  $\Omega$ . Determine inductance, capacitance, resonant frequency, upper and lower cutoff frequencies. (12+8)

- 4A.** Inductor loads of 0.8 kW and 1.2 kW at lagging power factors of 0.8 and 0.6 respectively are connected across a 200 V, 50 Hz supply. Find the total current, power factor and the value of the capacitor to be put in parallel to make the overall power factor 0.94 lag.

- 4B.** Use Norton's theorem to find current through  $Z_L$  (Fig 4B) (10+10)

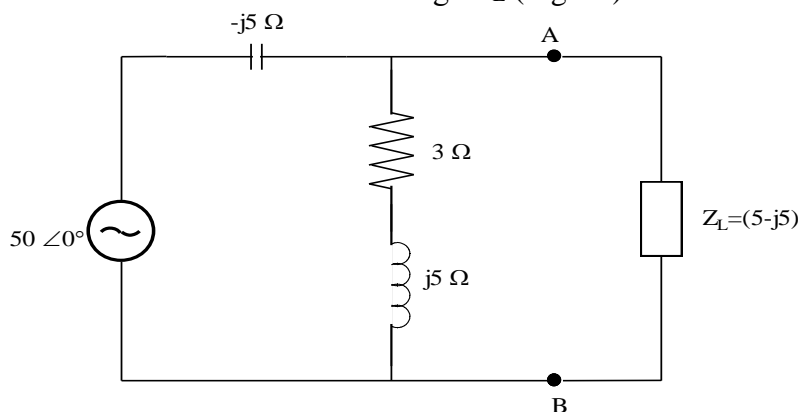


Fig 4B

- 5A** A Generator of voltage 400 V  $\angle 0^\circ$  is connected to a motor of voltage  $E_b \angle \Phi$  V, through a line impedance  $(1 + j4) \Omega$ .

Find the supply current, power factor, power input & power output of motor for the following cases.

- $E_b = 400 \angle -20^\circ$  V
- $E_b = 350 \angle -20^\circ$  V
- $E_b = 450 \angle -20^\circ$  V

- 5B** With a neat connection diagram & phasor diagram prove that two wattmeters are sufficient to measure three phase power. Explain how the wattmeter readings are affected by the load power factor. (12+8)

- 6A** A generator of 400  $\angle 0^\circ$  V is connected to a constant magnitude load but variable phase angle, the load draws a current of 10 A at unity, 0.8 pf lag & 0.8 pf lead. Find the load voltage for the above cases, given line impedance of  $(0.5 + j3) \Omega$ .

- 6B.** Find the equivalent impedance and the power factor of the circuit given in Fig 6B (10+10)

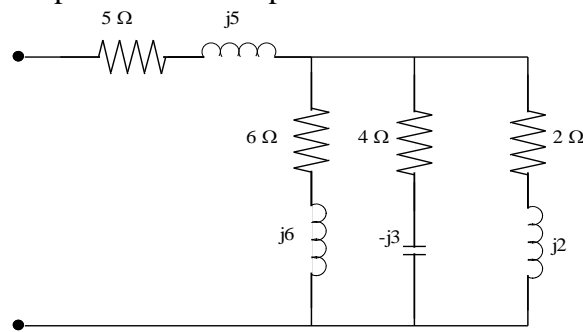


Fig 6B

- 7A.** An industry has the following loads

- A 3 phase circuit  $\gamma$  connected operating at 400 V drawing a line current of 20 A at 0.8 pf lag
- A 3 phase circuit  $\Delta$  connected with a phase current of 15 A at 400 V and power factor 0.707 lag.
- A 10 kW motor with efficiency 0.8 and pf 0.8 operating at 400 V

Find the total load kVA and resultant power factor.

- 7B.** Obtain the thevenin equivalent circuit for the network shown in Fig 7B. (10+10)

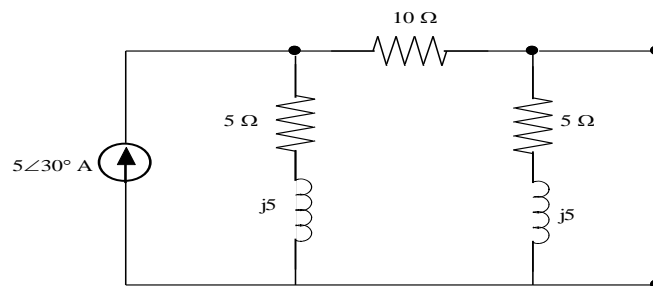


Fig 7B

- 8A.** Find the power output of the current source shown in Fig 8A

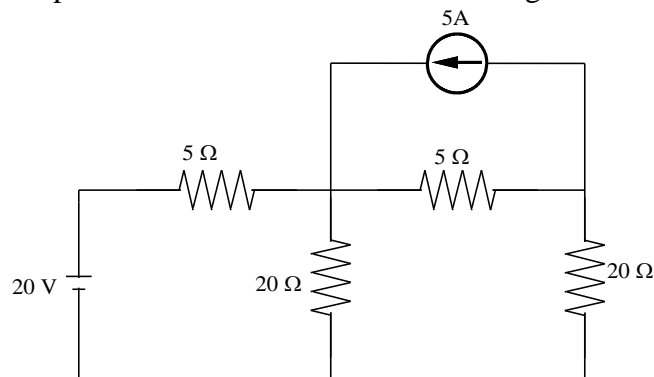


Fig 8A

- 8B.** Find the source voltage, source current and power input (Fig 8B). (10+10)

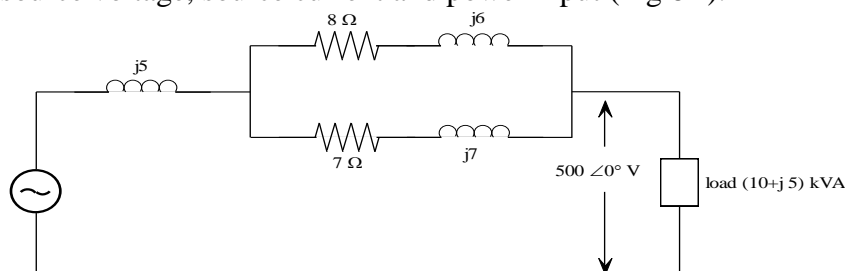


Fig 8B

