



Reg. No.									
----------	--	--	--	--	--	--	--	--	--

# INTERNATIONAL CENTRE FOR APPLIED SCIENCES

(Manipal University)

## III SEMESTER B.S. DEGREE EXAMINATION – APRIL / MAY 2017

SUBJECT: LINEAR NETWORK TRANSIENT ANALYSIS (EE 231)

(BRANCH: E&E and E&C)



Saturday, 13 May 2017

Time: 3 Hours

Max. Marks: 100

- ✓ Answer ANY FIVE full Questions.
- ✓ Missing data, if any, may be suitably assumed

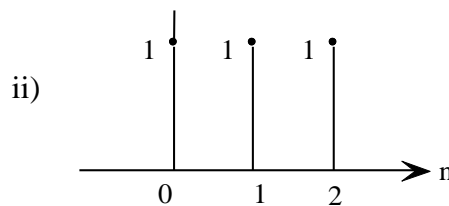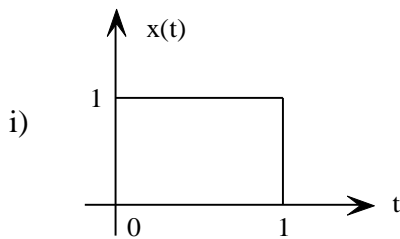1A. Find the odd and even components of the following.



iii)  $x(t) = (1+t^3) \cos^3 10t$

1B. Find the laplace transformation of the periodic rectified sine wave with period T and peak value of A. (10+10)

2A. Find the initial and final values of the function whose laplace transform is

$$F(s) = \frac{(2S+1)}{(6S^2+11S+6)} \quad \text{and} \quad F(s) = \frac{10}{S(S^2+2S+4)}$$

2B. A step voltage of E volts is applied to a series RLC circuit with  $L=1H$ ,  $C=\frac{1}{4}F$ .

Find the voltage across the capacitor for the following values of resistance.

$R=2\Omega$ ,  $R=4\Omega$  and  $R=5\Omega$ . Comment on the results. (8+12)

3A. The voltage  $V(s)$  of a network is  $V(s) = \frac{3s}{(s+2)(s^2+2s+2)}$ . Draw the pole zero diagram & determine the residues of poles.

3B. Find the laplace transform of the following functions.

i)  $f(t) = \cos^2 t$       ii)  $f(t) = t \sin \omega t$       iii)  $f(t) = \frac{(1-e^{-t})}{t}$       iv)  $(t+1)^2 e^t$  (8+12)

4A. Using convolution theorem evaluate the inverse laplace transform of the following.

i)  $\frac{1}{(s+a)^2}$       ii)  $\frac{1}{s(s+a)}$       iii)  $\frac{1}{(s^2+1)^2}$

4B.  $V=50 \sin 10t$  is applied to a series R-C circuit.  $R=2\Omega$  and  $C=0.25F$ . Find the equation for the current in the circuit. Assume zero initial conditions (10+10)

- 5A** In the network shown in Fig 5A, the switch is moved from a to b, at  $t=0$ , find  $V(t)$ .

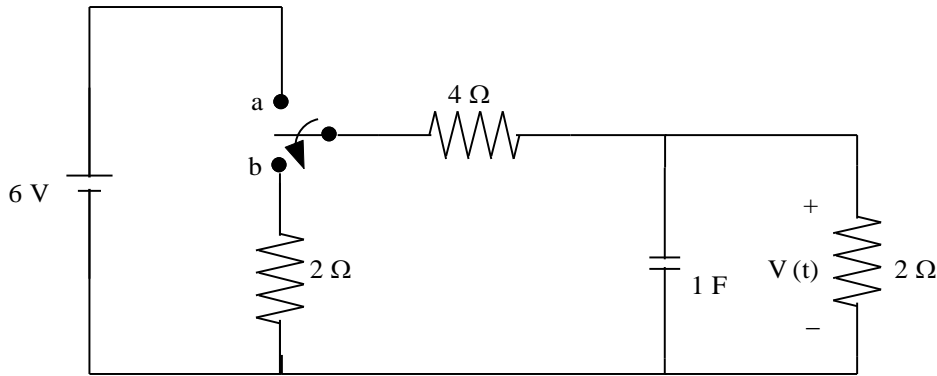


Fig 5A

- 5B** Find the laplace transform of the trapezoidal pulse shown in Fig 5B. **(10+10)**

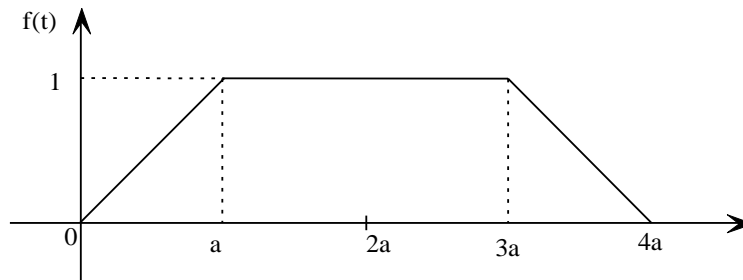


Fig 5B

- 6A** determine the voltage transfer functions  $\frac{V_2}{V_1}$  for the network (Fig 6A)

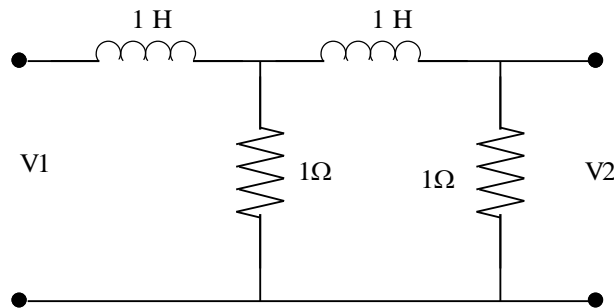


Fig 6A

- 6B.** In the network shown in Fig 6B, the switch is closed at  $t=0$ , the steady state having been reached at  $t=0$ . Determine the current through the inductor of 3H. **(10+10)**

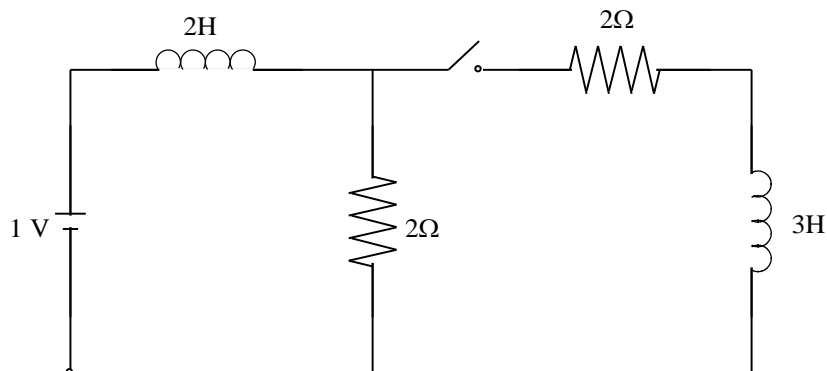


Fig 6B

- 7A.** In the network shown in Fig 7A, the switch is moved from a to b at  $t=0$ , determine  $V_c(t)$ .

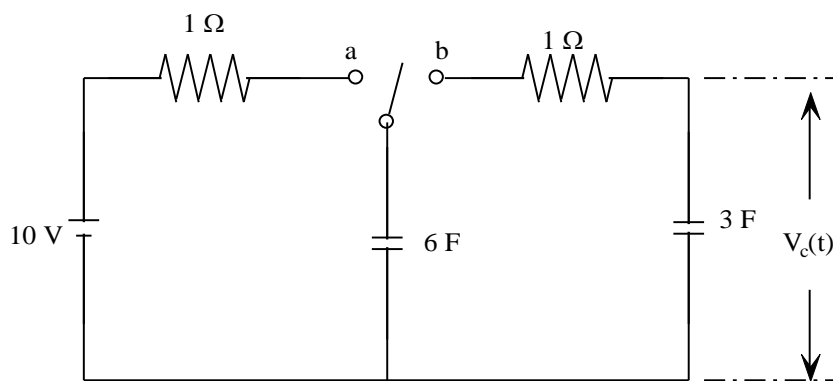


Fig 7A

- 7B.** Find the current response of a series R-L circuit excited by  $V=V_m \sin \omega t$ . **(10+10)**
- 8A.** A series RLC circuit with  $R=3\ \Omega$ ,  $L=1\text{ H}$  and  $C=0.5\text{ F}$  is connected to a step voltage of 10 V. Assuming zero initial conditions find the current for  $t > 0$ .
- 8B.** Find the current response of a series R-L circuit with  $R=10\ \Omega$  and  $L=5\text{ H}$ , when the voltage applied  $V(t)=10 \sin 5t$ . **(10+10)**

