



Reg.No.									
---------	--	--	--	--	--	--	--	--	--

## INTERNATIONAL CENTRE FOR APPLIED SCIENCES

(Manipal University)

### IV SEMESTER B.S. DEGREE EXAMINATION – APRIL/ MAY 2017

SUBJECT: ELECTRONIC DEVICES AND COMPUTER INTERFACING (CS241)

(BRANCH: CS & CE)

Thursday, 27 April 2017

**Time: 3 Hours**

**Max. Marks: 100**

- ✓ Answer ANY FIVE full Questions.
- ✓ Missing data, if any, may be suitably assumed

1A. Ideal diodes are used in a bridge rectifier with a source of  $230 \sin 314t$ . Draw the circuit diagram of it. If the load resistance is  $1k\Omega$  and turns ratio of transformer is 10:1, determine:

- i) DC output voltage
- ii) RMS output voltage
- iii) Pulse frequency at the output
- iv) PIV of the diodes required for safe operation
- v) If a Capacitor filter is connected across  $R_L$ , C required for a ripple factor less than 0.001.

1B For a Zener regulator circuit the following specifications are given. Input voltage  $V_{in} = (50 \pm 2) V$ , output voltage  $V_0 = 10V$ ,  $R_S = 500\Omega$ , minimum Zener current = 0.5mA and maximum power dissipation of Zener diode  $P_{max} = 500mW$ . Find the range of  $R_L$  for which regulation can be achieved. Also draw the circuit diagram of the regulator.

**(10+10)**

2A Given a sinusoidal signal  $V_{in} = 10 \sin \omega t$  is applied to double clipper which clips the input waveform at a voltage of -1V and -3V. Draw the clipper circuit, input/ output waveforms and transfer characteristics. Mention the diode status in all operating regions. Assume ideal diodes.

2B With a neat block diagram explain the working of successive approximation ADC. Consider a 4 bit ADC with  $V_{ref} = 0.5 V$ . Give the conversion table and illustrate with clock how 0.40V is converted to its digital equivalent.

**(10+10)**

3A A Silicon diode carries a current of 20mA when it is forward biased with 0.7V at  $27^\circ C$ . Determine:

- i) Reverse saturation current.
- ii) Dynamic forward resistance
- iii) Bias voltage required to get a current of 80 mA.

3B Draw the circuit diagram of an OPAMP integrator and noninverting amplifier. Derive the expression for output voltage for both circuits.

**(10+10)**

4A With a neat circuit diagram and plots explain the input and output characteristics of a NPN common base transistor.

4B The following parameters are given for a fixed bias circuit with Si transistor.  $I_{CQ} = 5mA$ ,  $\beta = 70$ ,  $R_C = 2 k\Omega$  and  $V_{CC} = 15 V$ . Find  $R_B$  and  $V_{CEQ}$ . Plot the load line and locate the Q point on it. Draw the circuit diagram.

**(10+10)**

- 5A Draw the VI characteristics of a TRIAC and explain the same.
- 5B With a neat circuit diagram, expression and relevant waveforms explain the working of a Monostable multivibrator using 555 timer.

**(10+10)**

- 6A With a neat circuit diagram and relevant expressions explain the working of RC phase shift oscillator circuit. Also discuss the Barkhausen Criterion required for oscillations.
- 6B Draw the circuit diagram of an OPAMP comparator circuit and explain its working with relevant expression. If voltage applied to inverting and noninverting terminal terminals of an OPAMP is as given below plot the output voltage with respect to input voltage. Given  $V_{CC} = 15V$

Inverting terminal voltage	Noninverting terminal voltage
5V	$10 \sin \omega t$
$10 \sin \omega t$	-2V

**(10+10)**

- 7A Draw the circuit diagram of a self-bias circuit. Determine the expressions required to find the operating point. Mention the effect of variation of  $V_{CC}$ ,  $I_B$  and  $R_C$  on the load line.
- 7B With a neat circuit diagram, relevant waveforms and expressions explain the working of a square wave generator.

**(10+10)**

- 8A Explain the construction and VI characteristics of an n-channel enhancement-type MOS FET.

- 8B Write short note on

- i. LED
- ii. Clamper circuit
- iii. Transistor switch
- iv. DIAC

**(10+10)**

